
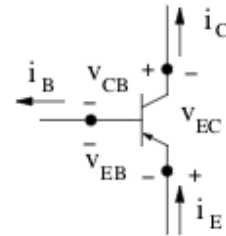


# BJT Large and Small Signal Models

- This document contains large and small signal models for the BJT transistor in the active region.
- I made sure to include models that model the Early Effect.

## Summary of BJT Large-Signal Models:

	NPN	PNP
<b>Cut-off:</b>		
BE reverse biased	$i_B = 0,$ $i_C = 0$	$i_B = 0$ $i_C = 0$
<b>Active Linear:</b>		
BE forward biased	$i_B = \frac{I_S}{\beta} e^{v_{BE}/nV_T}$	$i_B = \frac{I_S}{\beta} e^{v_{EB}/nV_T}$
CE reverse biased	$i_C = I_S e^{v_{BE}/nV_T} \left(1 + \frac{v_{CE}}{V_A}\right)$	$i_C = I_S e^{v_{EB}/nV_T} \left(1 + \frac{v_{EC}}{V_A}\right)$
<b>Saturation:</b>		
BE forward biased	$i_B = \frac{I_S}{\beta} e^{v_{BE}/nV_T}$	$i_B = \frac{I_S}{\beta} e^{v_{EB}/nV_T}$
CE forward biased	$i_C < \beta i_B, v_{CE} = 0.1 - 0.3 \text{ V}$	$i_C < \beta i_B, v_{EC} = 0.1 - 0.3 \text{ V}$

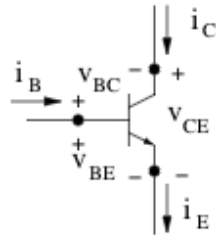

$$i_C + i_B = i_E$$


$$i_C = \beta i_B \left(1 + \frac{v_{CE}}{V_A}\right)$$

## 5.8.7 MODELING THE EARLY EFFECT

The dependence of the collector current on collector-emitter voltage is easily included in the simplified mathematical model for the forward-active region of the BJT by modifying Eqs. (5.23) as follows:

$$\begin{aligned}i_C &= I_S \left[ \exp \left( \frac{v_{BE}}{V_T} \right) \right] \left[ 1 + \frac{v_{CE}}{V_A} \right] \\ \beta_F &= \beta_{FO} \left[ 1 + \frac{v_{CE}}{V_A} \right] \\ i_B &= \frac{I_S}{\beta_{FO}} \left[ \exp \left( \frac{v_{BE}}{V_T} \right) \right]\end{aligned}\tag{5.43}$$

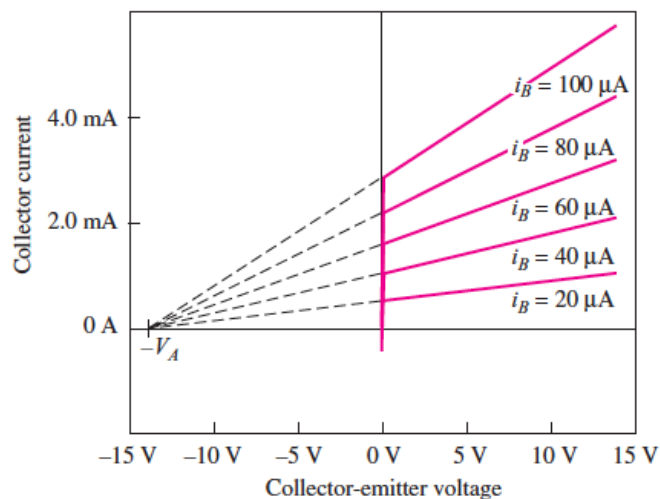$\beta_{FO}$  represents the value of  $\beta_F$  extrapolated to  $V_{CE} = 0$ . In these expressions, the collector current and current gain now have the same dependence on  $v_{CE}$ , but the base current remains independent of  $v_{CE}$ . This is consistent with Fig. 5.28, in which the separation of the constant-base-current curves in the forward-active region increases as  $v_{CE}$  increases, indicating that the current gain  $\beta_F$  is increasing with  $v_{CE}$ .


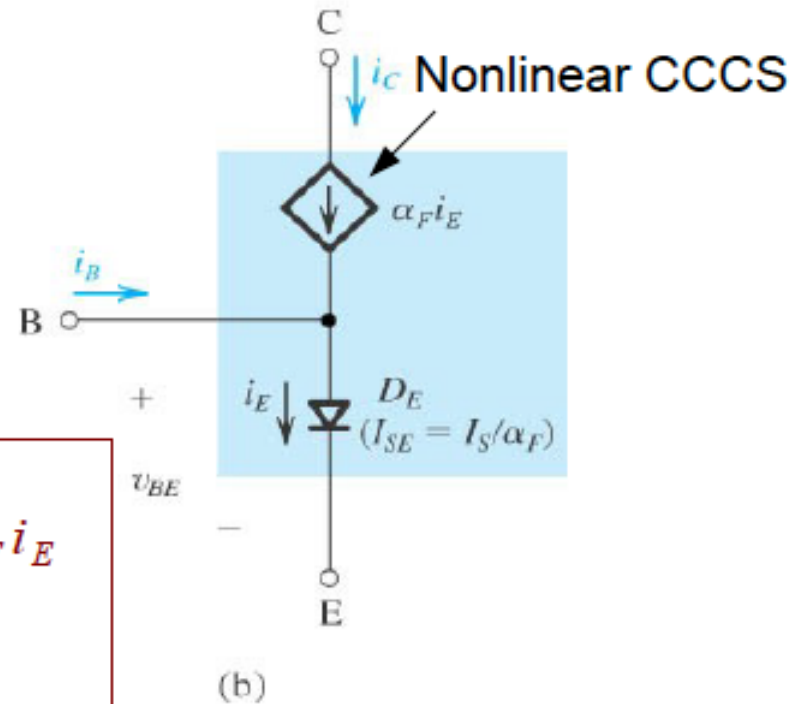


**Figure 5.28** Transistor output characteristics identifying the Early voltage  $V_A$ .
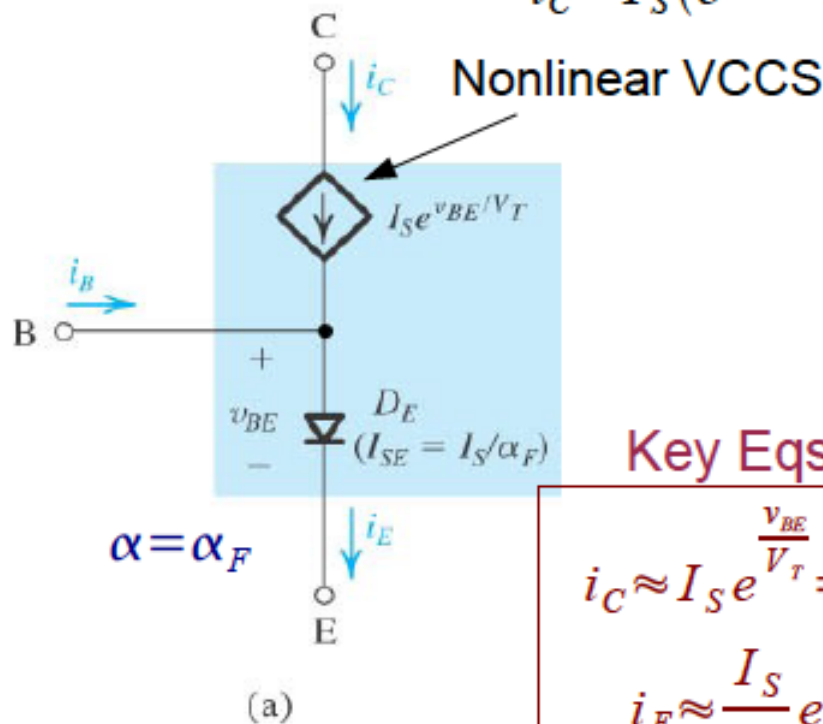
# Ignoring Early Voltage

Two equivalent large signal circuit models for the **forward-active mode NPN BJT**:

$$i_C = I_S \left( e^{\frac{v_{BE}}{V_T}} - 1 \right) \approx I_S e^{\frac{v_{BE}}{V_T}}$$



Key Eqs.

$$i_C \approx I_S e^{\frac{v_{BE}}{V_T}} = \alpha_F i_E$$


$$i_E \approx \frac{I_S}{\alpha_F} e^{\frac{v_{BE}}{V_T}}$$

# Ignoring Early Voltage
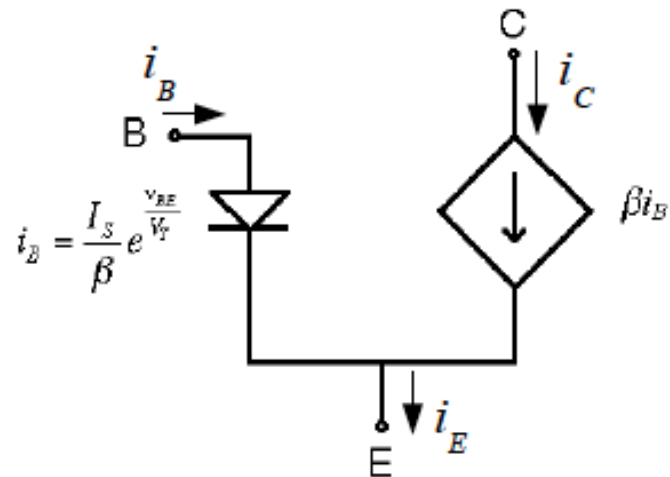
## Yet another NPN BJT large signal model

$$i_C = \beta i_B \approx I_S e^{\frac{v_{BE}}{V_T}} \Rightarrow i_B \approx \frac{I_S}{\beta} e^{\frac{v_{BE}}{V_T}}$$


This “looks like” a diode between base and emitter and the equivalent circuit becomes:




Note that in this model, the diode current is represented in terms of the *base current*. In the previous ones, it was represented in terms of the *emitter current*.

# Equivalent Circuit Models


## Ignoring Early Voltage

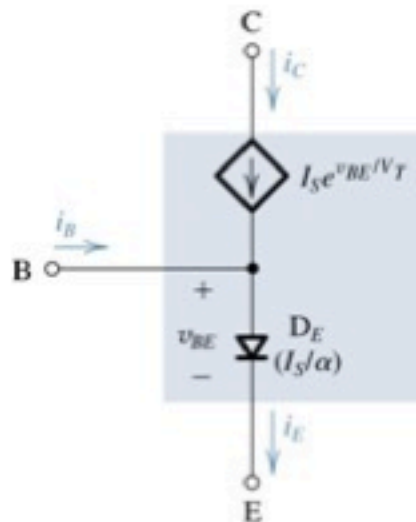


(a)

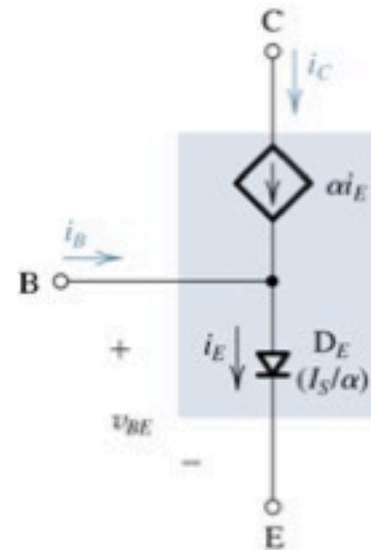

(b)

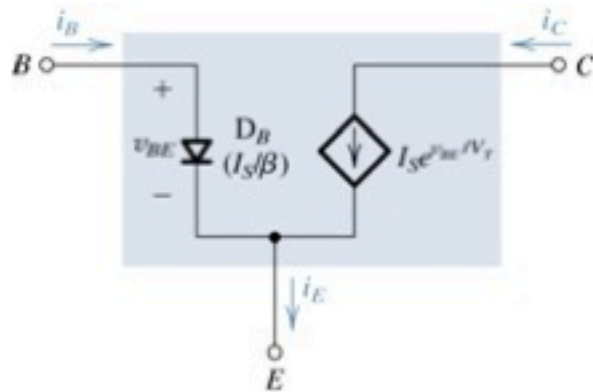


(c)

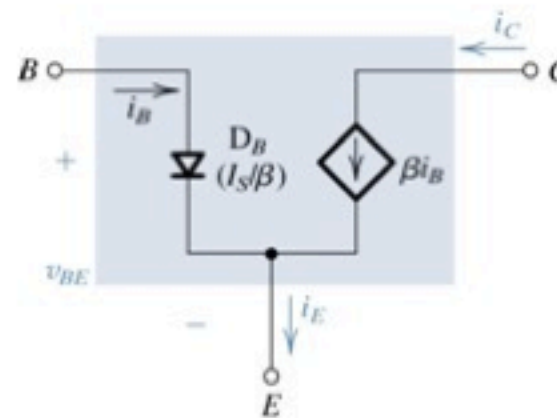

(d)





Large-signal equivalent-circuit models of the *npn* BJT operating in the active mode.

# Ignoring Early Voltage

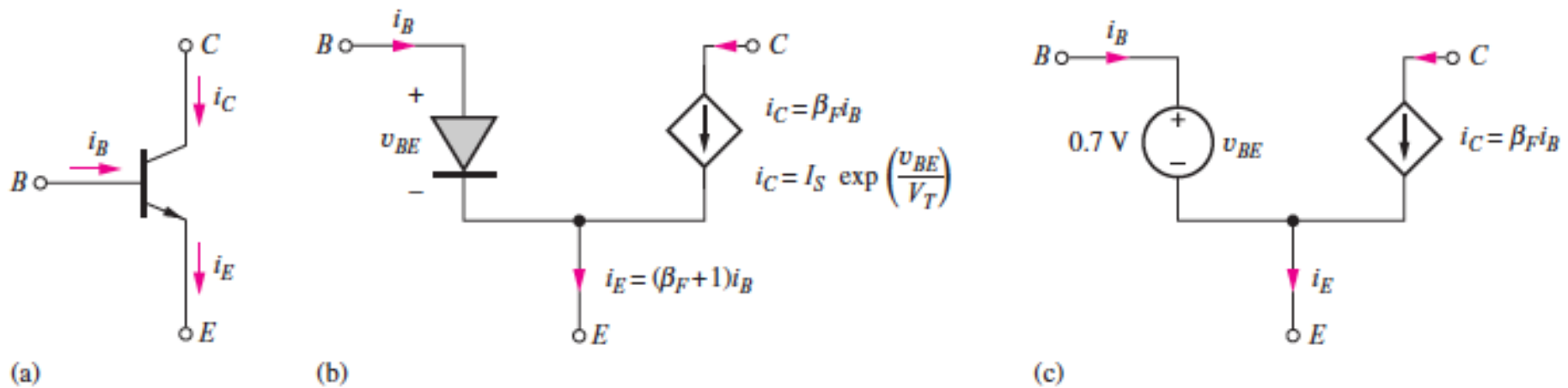

**Figure 5.17** (a) *npn* transistor. (b) Simplified model for the forward-active region. (c) Further simplification for the forward-active region using the CVD model for the diode.
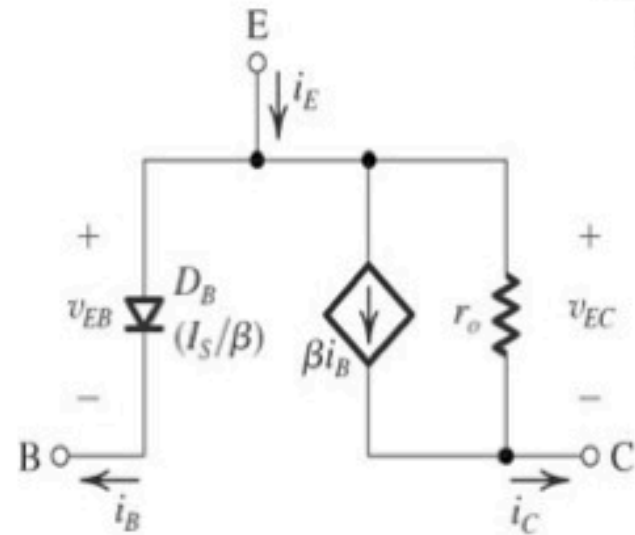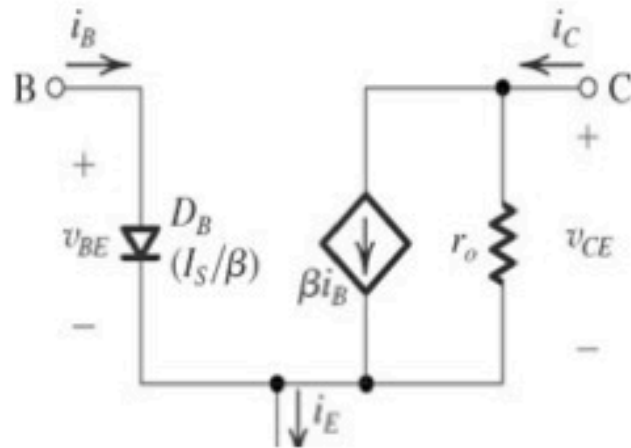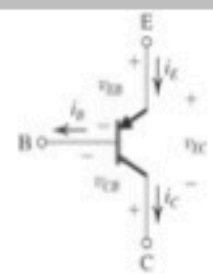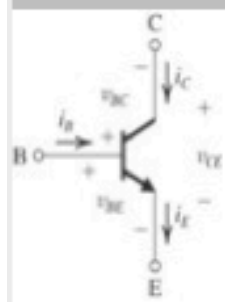
## Table 5.3 Symbols & Large Signal Model



Large-Signal Equivalent-Circuit Model (Including the Early Effect)

$$i_B = \left(\frac{I_S}{\beta}\right) e^{v_{BE}/V_T}$$

$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A}\right)$$

$$r_o = V_A / (I_S e^{v_{BE}/V_T})$$


$$i_B = \left(\frac{I_S}{\beta}\right) e^{v_{EB}/V_T}$$

$$i_C = I_S e^{v_{EB}/V_T} \left(1 + \frac{v_{EC}}{|V_A|}\right)$$


$$r_o = |V_A| / (I_S e^{v_{EB}/V_T})$$
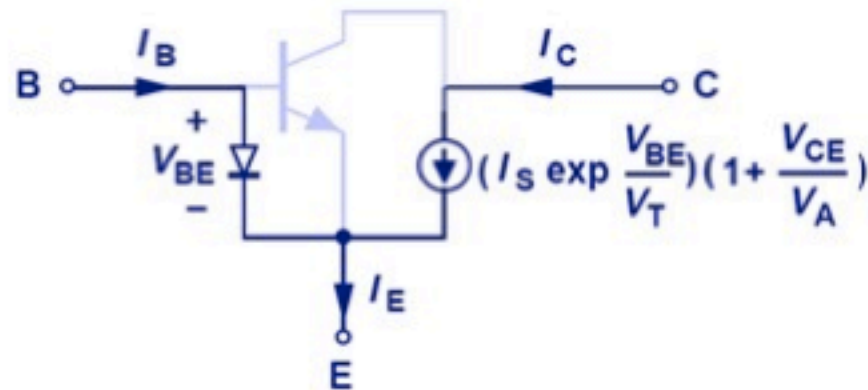
# Large-Signal *vs.* Small-Signal Models

- The large-signal model is used to determine the DC operating point ( $V_{BE}$ ,  $V_{CE}$ ,  $I_B$ ,  $I_C$ ) of the BJT.




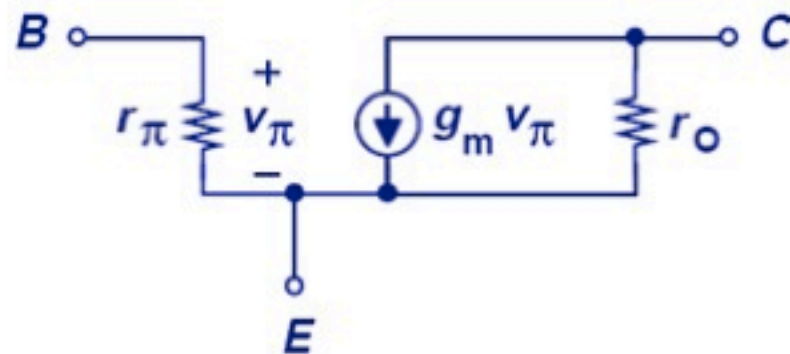- The small-signal model is used to determine how the output responds to an input signal.


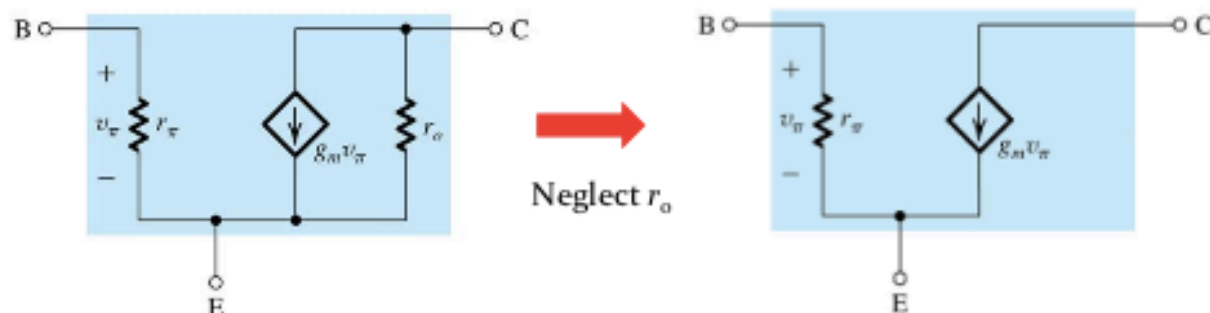
## BJT small-signal models

- ❑ Two models are exchangeable and does not affect the analysis result
- ❑ The hybrid- $\pi$  model
  - Typically used as the emitter is grounded




Model Parameters in Terms of DC Bias Currents

$$g_m = \frac{I_C}{V_T} \quad r_e = \frac{V_T}{I_E} = \alpha \frac{V_T}{I_C}$$

$$r_x = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C} \quad r_o = \frac{|V_A|}{I_C}$$

- ❑ The T model

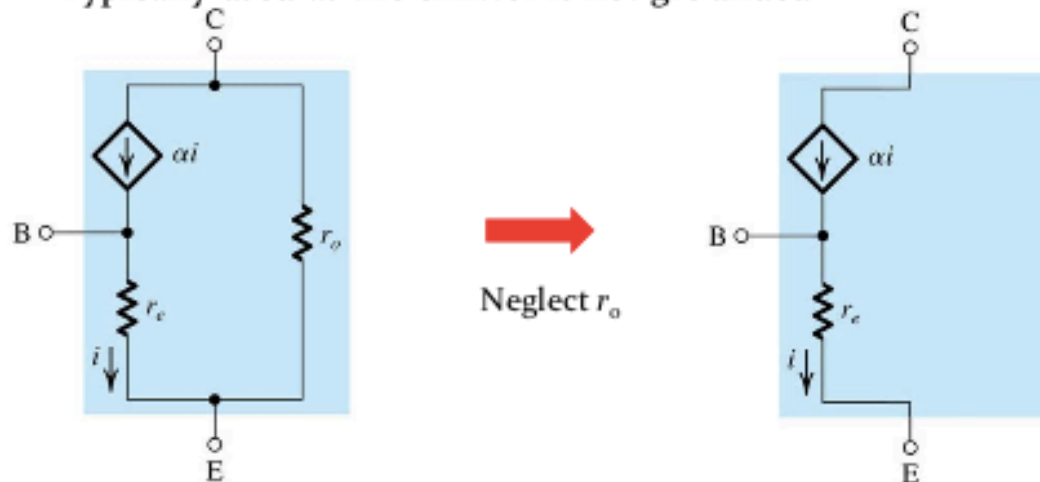- Typically used as the emitter is not grounded



In Terms of  $g_m$

$$r_e = \frac{\alpha}{g_m} \quad r_x = \frac{\beta}{g_m}$$

In Terms of  $r_e$

$$g_m = \frac{\alpha}{r_e} \quad r_x = (\beta + 1)r_e$$

Relationships between  $\alpha$  and  $\beta$

$$\beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{\beta}{\beta + 1}$$

## Output Resistance

$r_o$  is output resistance seen from collector terminal

$$i_C = I_S e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$
$$r_o = \left[ \frac{\partial i_C}{\partial v_{CE}} \Big|_{v_{BE} = \text{constant}} \right]^{-1}$$
$$r_o = \frac{V_A + V_{CE}}{I_C}$$

Alternatively, neglecting the Early effect on the collector current, we define

$$I_C = I_S e^{v_{BE}/V_T}$$

The output resistance then becomes

$$r_o = \frac{V_A}{I_C}$$