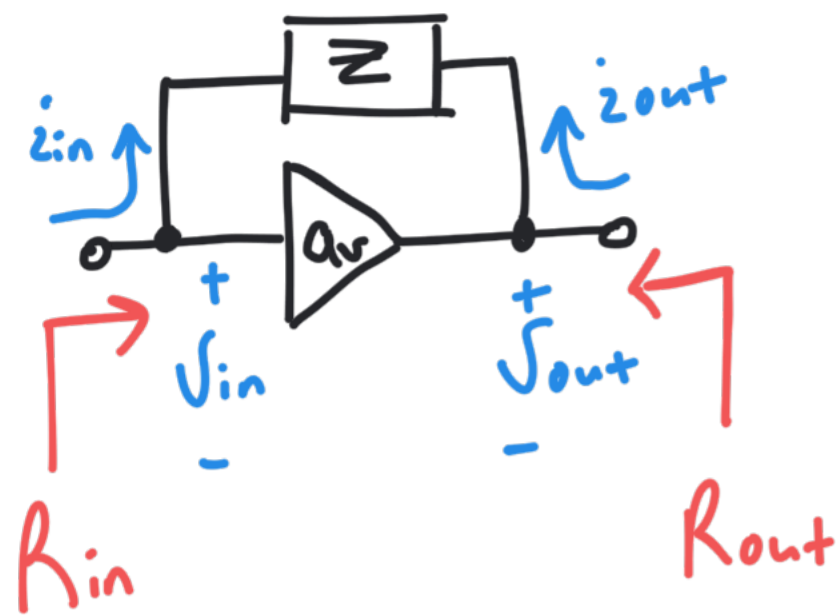


Quick review: Miller Time!



$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{V_{in} - V_{out}} = \frac{Z V_{in}}{V_{in} - V_{out}}$$

Input Impedance

$$Z_{in} = \frac{Z V_{in}}{V_{in} - V_{out}}$$

$$Z_{in} = \frac{Z}{1 - a_v}$$

for negative feedback: $a_v = -|a_v|$

$$Z_{in} = \frac{Z}{1 + |a_v|}$$

Output Impedance


$$R_{out} = \frac{V_{out}}{i_{out}} = \frac{V_{out}}{\frac{V_{out} - V_{in}}{Z}} = \frac{Z a_v}{a_v - 1}$$


← so, $Z_{out} = \frac{Z a_v}{a_v - 1}$

we see that Z_{in} can be drastically reduced

for negative feedback: $a_v = -|a_v|$

$$Z_{out} = \frac{Z |a_v|}{|a_v| + 1}$$

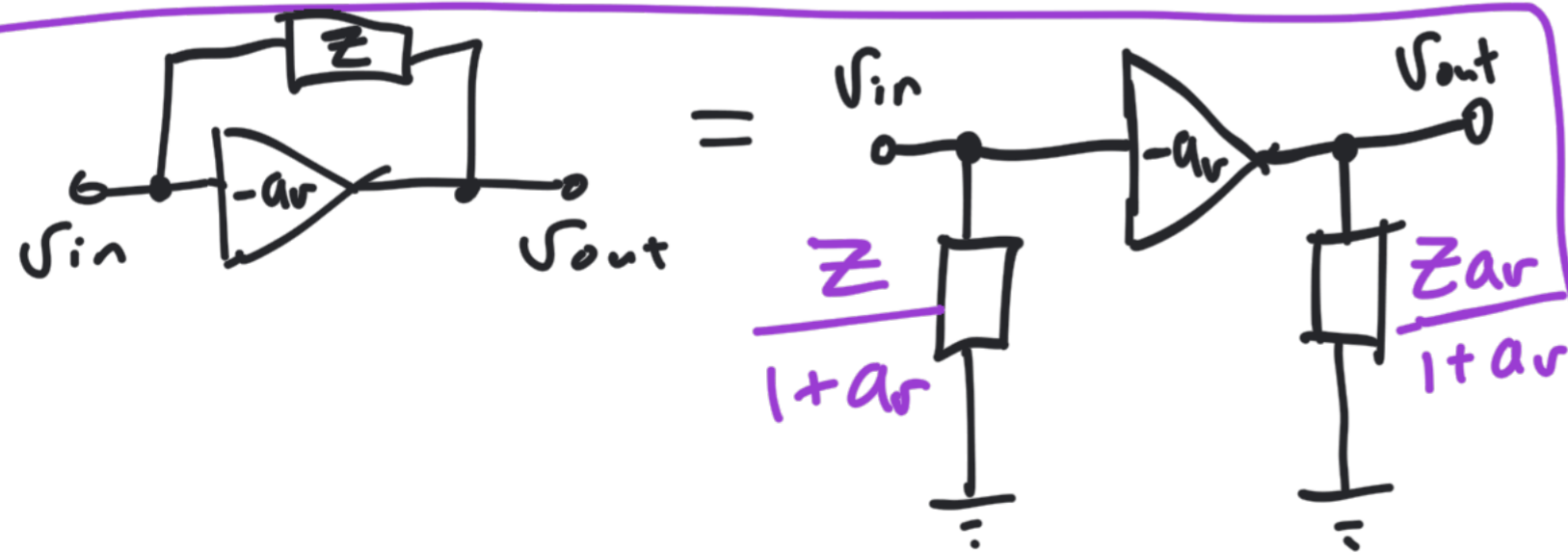

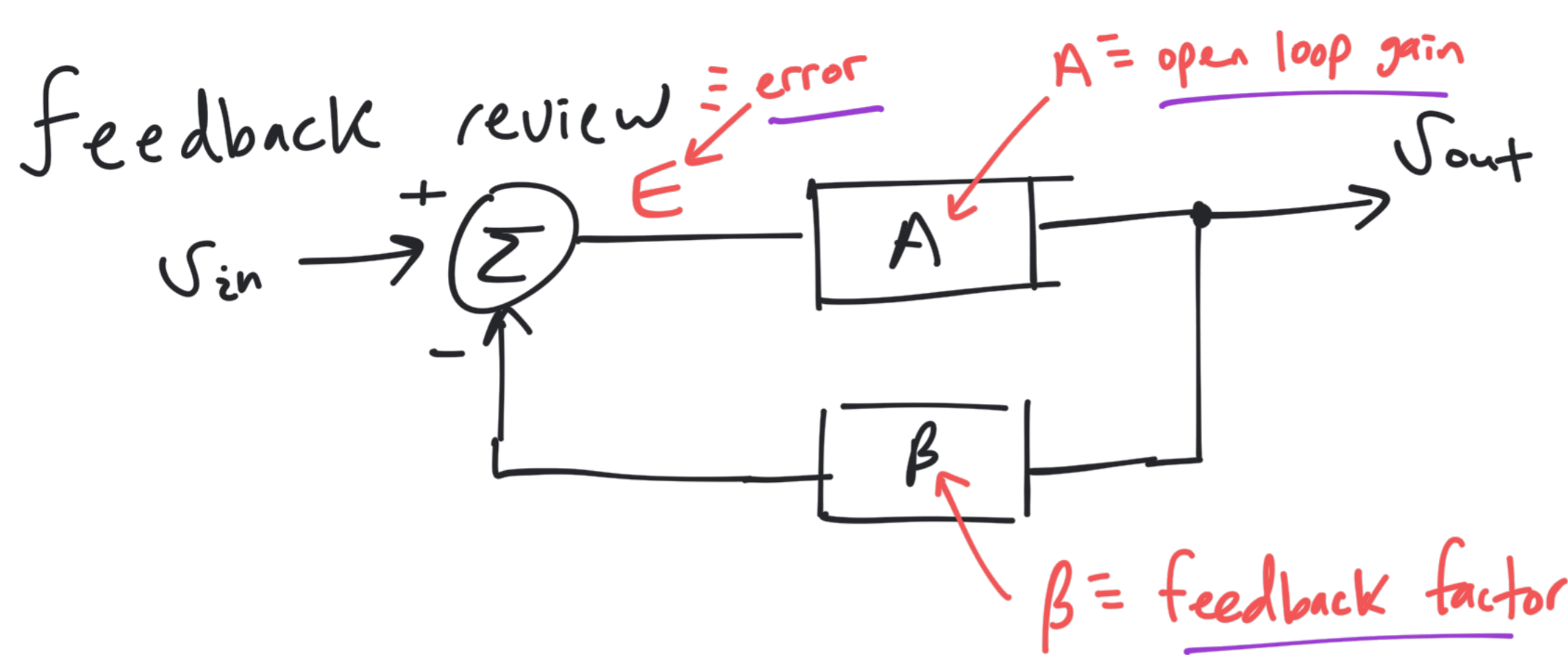

Derivation

$$E = V_{in} - V_{out}\beta$$

$$E = V_{out}/A$$


$$\therefore \frac{V_{out}}{A} = V_{in} - V_{out}\beta$$

$$V_{out} = AV_{in} - V_{out}A\beta$$

$$V_{out}(1 - A\beta) = AV_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 - A\beta}$$

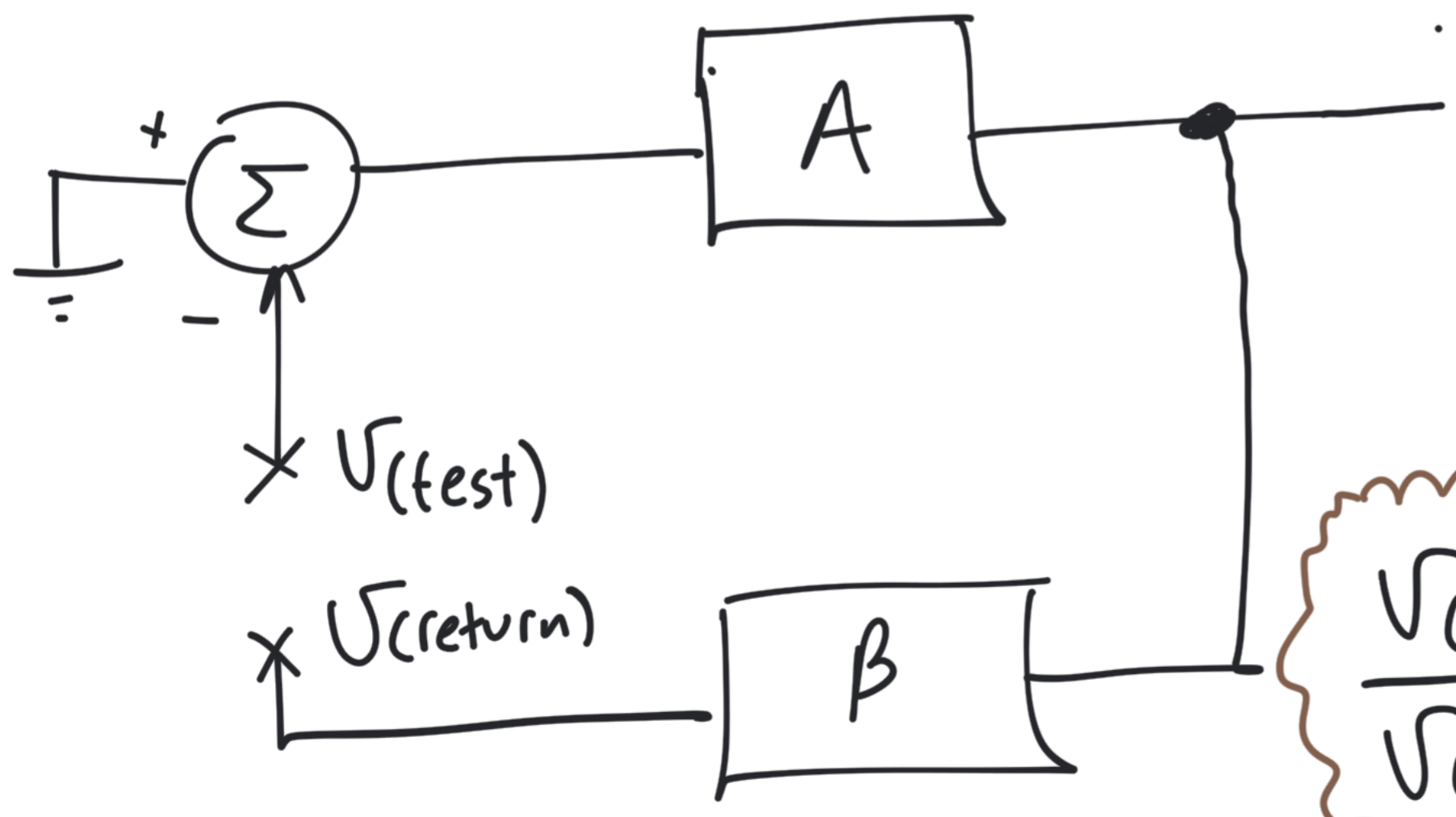Break feedback loop to measure/calculate loop gain:



$\frac{V_{out}}{V_{in}} \equiv$ closed loop gain

sometimes called "signal gain"

$A\beta \equiv$ loop gain

$$\frac{V(\text{return})}{V(\text{test})} = -A\beta$$

Bode Stability Criterion (see "A note on stability analysis using Bode Plots" by Hahn et al.)

A closed loop system is stable if the open-loop system is stable and frequency response of $A\beta$ has amplitude $|A\beta| < 1$ at all frequencies corresponding to: $\phi = \pm (180^\circ + n360^\circ)$



$$\phi = \angle A\beta$$

Technically, this is a sufficient condition for stability, but not a necessary condition. It is possible for a system to have multiple phase crossover frequencies (some w/ amplitudes larger than unity) and still be stable...

I think this is because $A\beta$ is monotonically decreasing at crossover point.

However, for op amp circuits most texts I see say: instability occurs when $|A\beta| \geq 1$ for $\angle A\beta = \phi = 180^\circ$.

So, to design an oscillator you want $A\beta = 1$ (Barkhausen criterion)


So, loop gain $A\beta$ determines stability.

What happens when $|A\beta| \rightarrow 1$ and $\angle A\beta \rightarrow 180^\circ$?

- V_{out} starts going to ∞ !
- When V_{out} approaches power supply rail, active devices in amplifier change gain... This causes A to change and forces $|A\beta| < 1$ or (I guess) $\angle A\beta \neq 180^\circ$ at $|A\beta| = 1$.
- Thus the trajectory of infinite voltage eventually stops!

At this stage one of three things can occur:

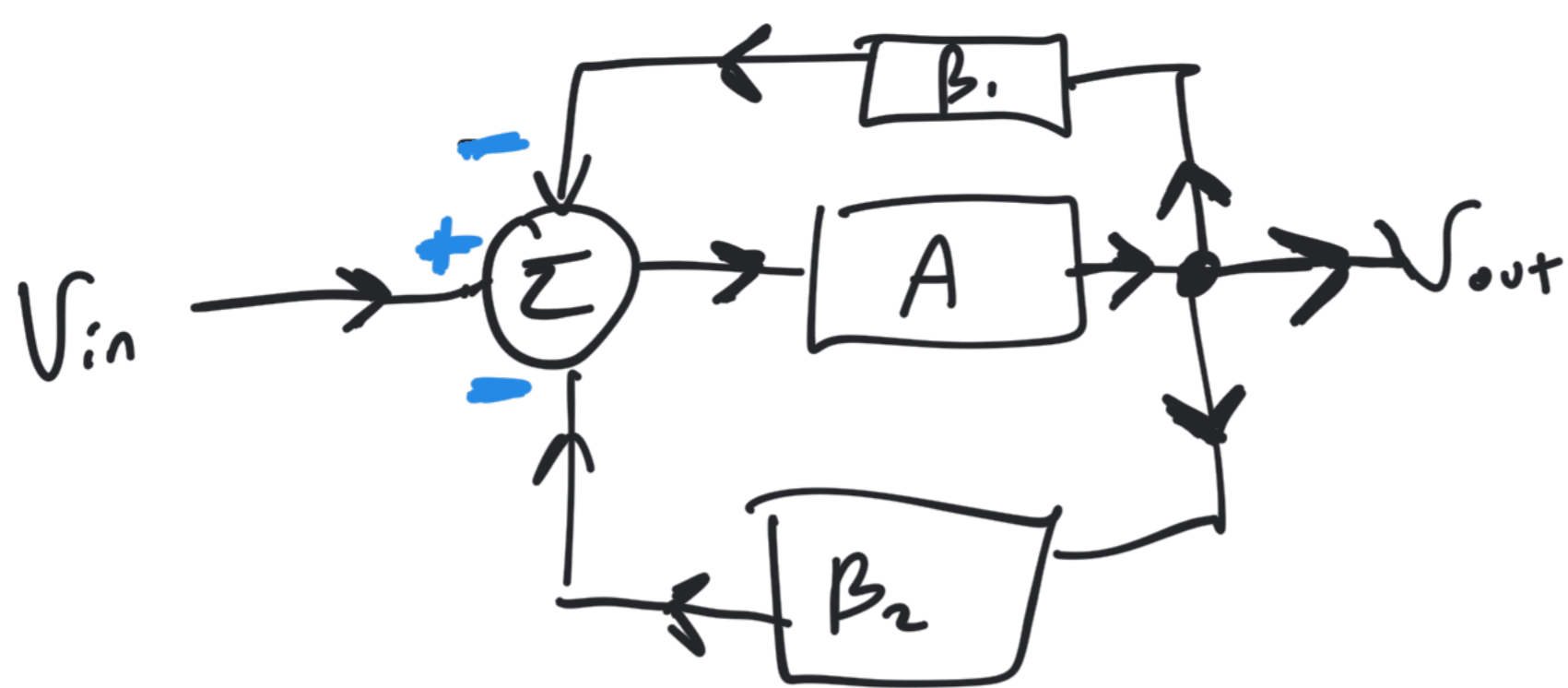1. Nonlinearity in saturation or cutoff causes system to become stable and lockup at current power rail.
2. System saturates (or cutoffs) for a long time before it becomes linear and heads for opposite power rail.
This results in highly distorted oscillations (usually quasi-square waves).
These oscillations are called relaxation oscillators.
3. System stays linear and reverses direction, leading for opposite power rail. This produces a sin-wave oscillator.



two feed back paths

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 - A(\beta_1 + \beta_2)}$$

system oscillates if

$$A(\beta_1 + \beta_2) = 1$$


$$\beta_1 + \beta_2 = \frac{1}{A}$$

$$\beta_1 + \beta_2 = 0 \quad (\text{Assume } A \gg 1)$$


$$\beta_1 = -\beta_2$$

← positive and negative feedback sort of cancel out.

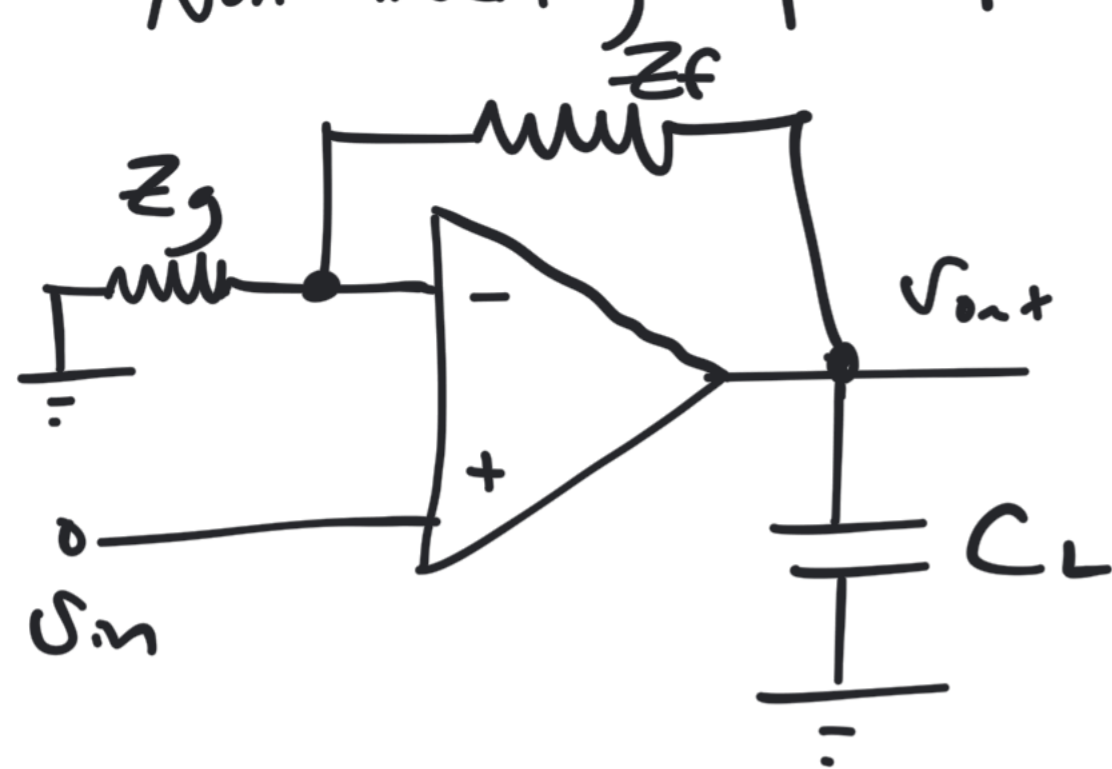
Non-inverting op amp : capacitively loaded



Equivalent Circuit

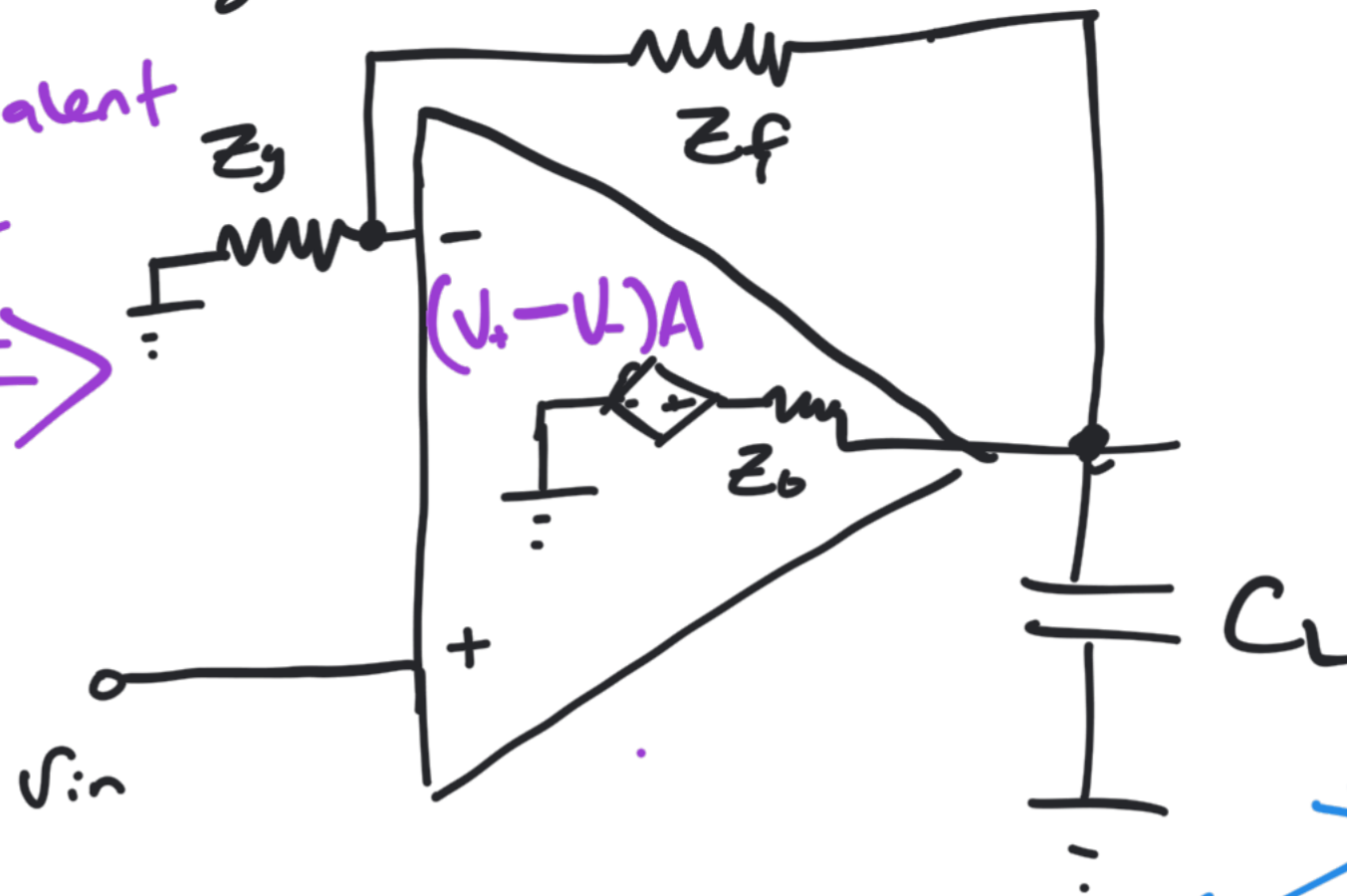


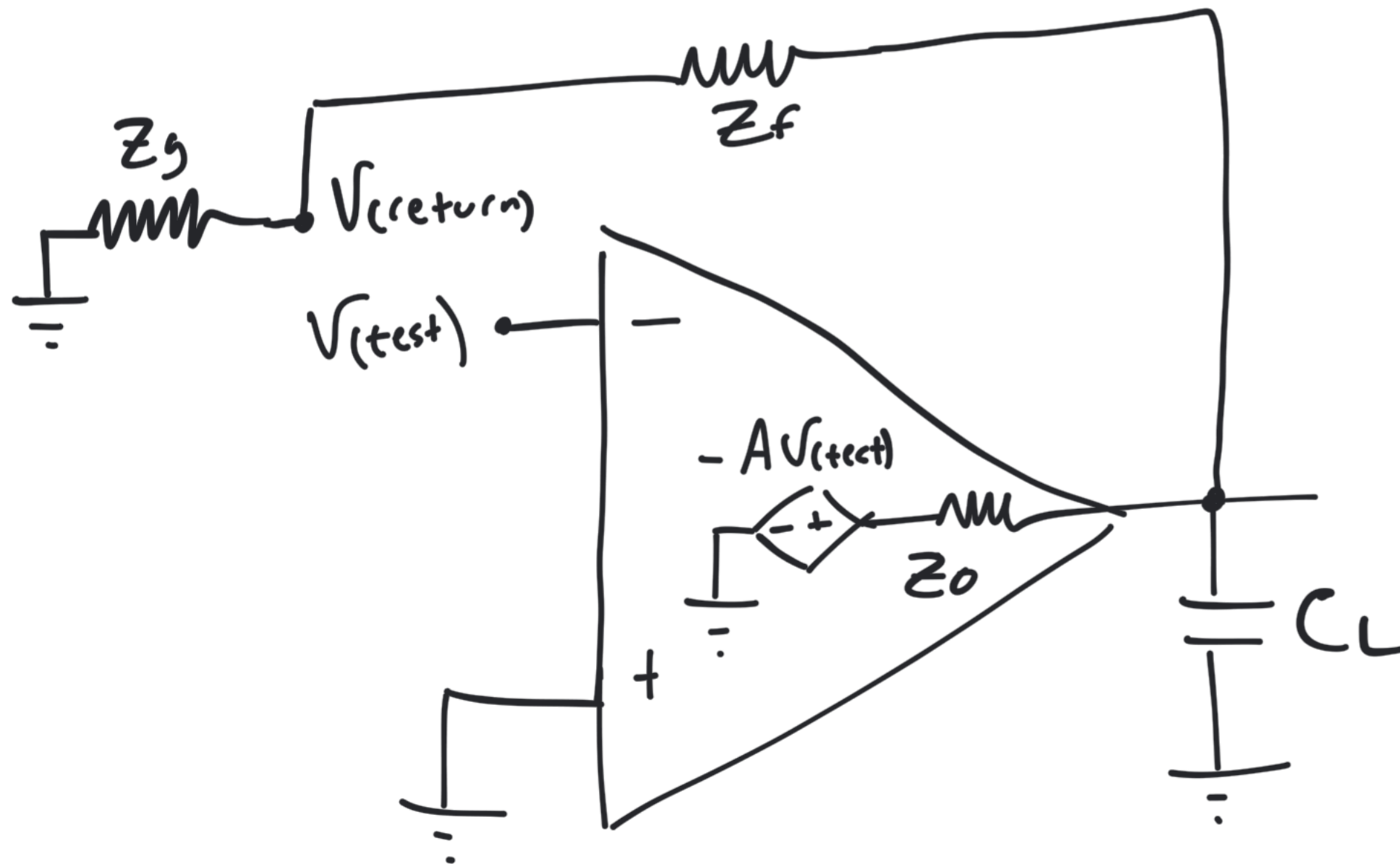To find $A\beta$... break the connection...



$$A\beta = \frac{V_{(return)}}{V_{(test)}}$$


Eg. circuit:

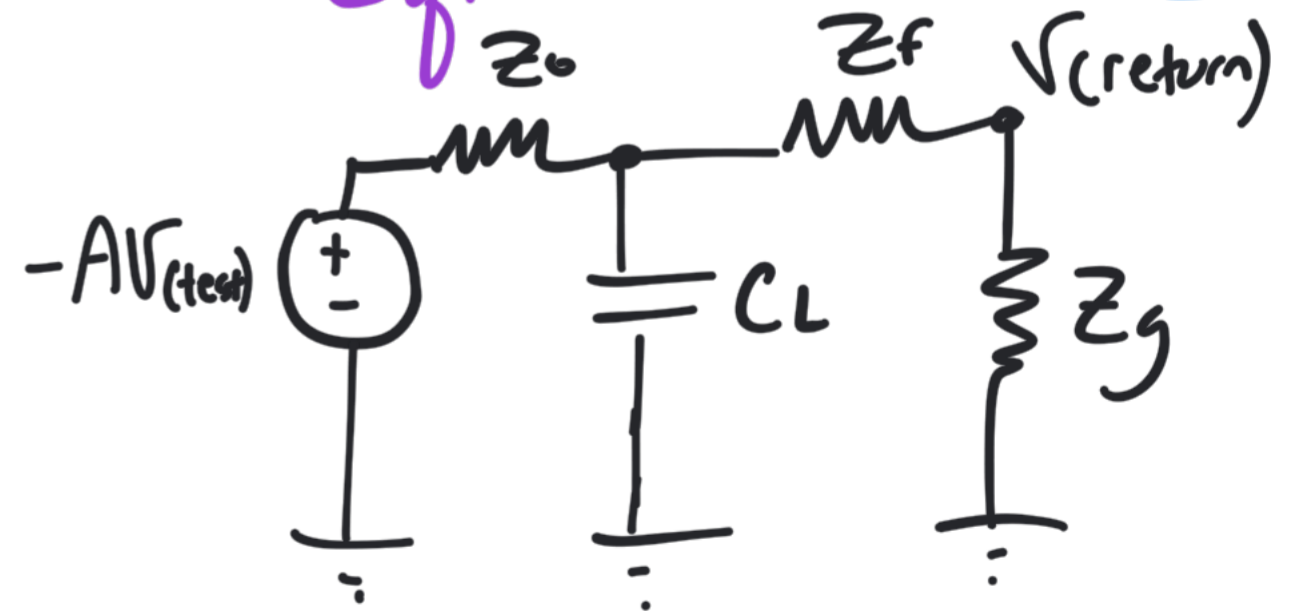

This is all exact same analysis for inverting op amp config!



Last circuit

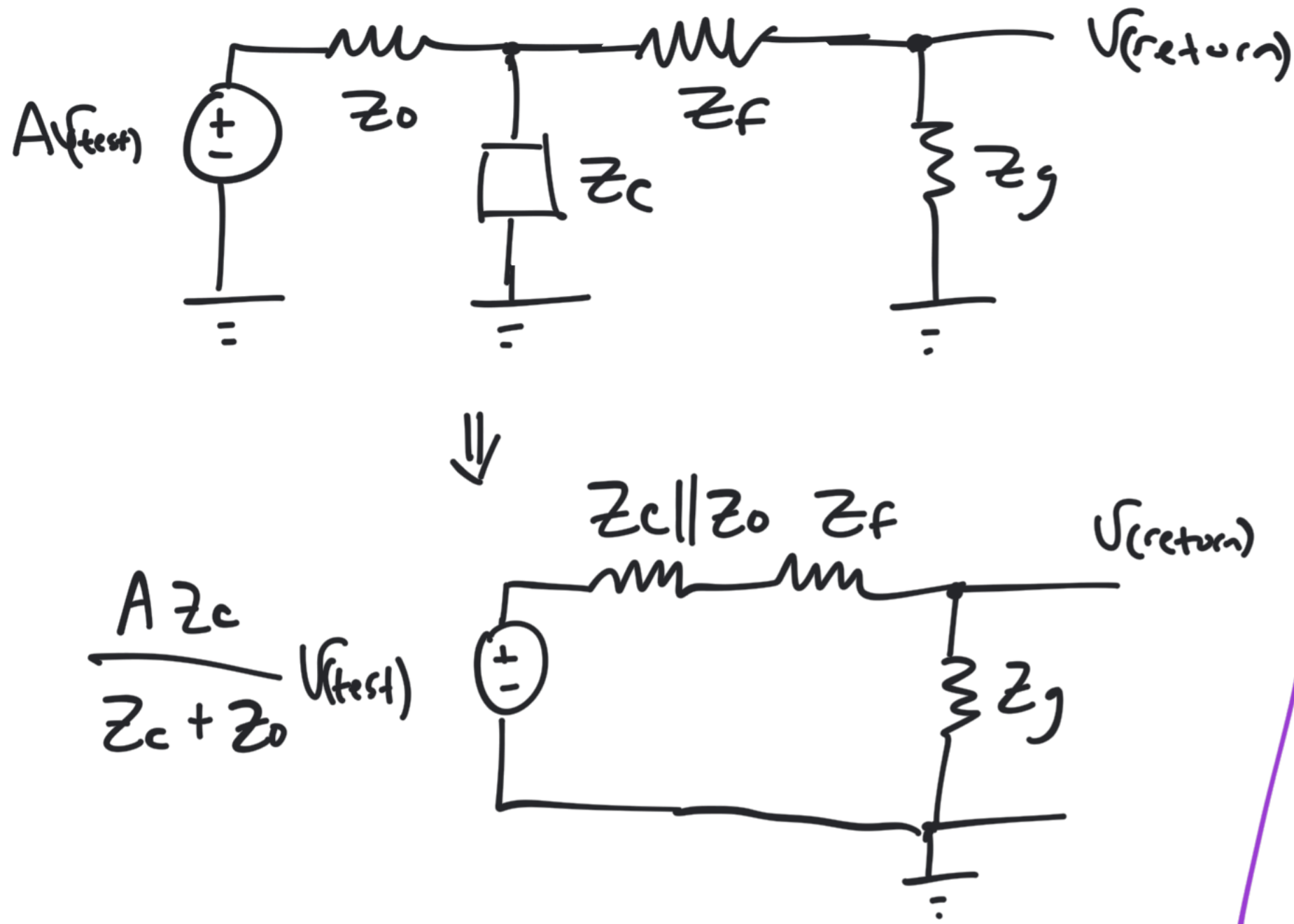

Assume $Z_f + Z_g \gg Z_c \parallel Z_0$

$$A\beta = \frac{A Z_c Z_g}{(Z_c + Z_0)(Z_f + Z_g)}$$

$$A\beta = \left(\frac{A Z_g}{Z_f + Z_g} \right) \left(\frac{Z_c}{Z_c + Z_0} \right)$$

$$Z_c = \frac{1}{s C_L} \text{ substitute}$$

$$A\beta = \left(\frac{A Z_g}{Z_f + Z_g} \right) \frac{1}{1 + s C_L Z_0}$$


real pole at $\frac{1}{C_L Z_0}$

Additional - phase shift!
negative

can cause instabilities!

$$\frac{V_{(return)}}{V_{(test)}} = A\beta = \frac{A Z_c}{Z_c + Z_0} \frac{Z_g}{Z_c \parallel Z_0 + Z_f + Z_g}$$

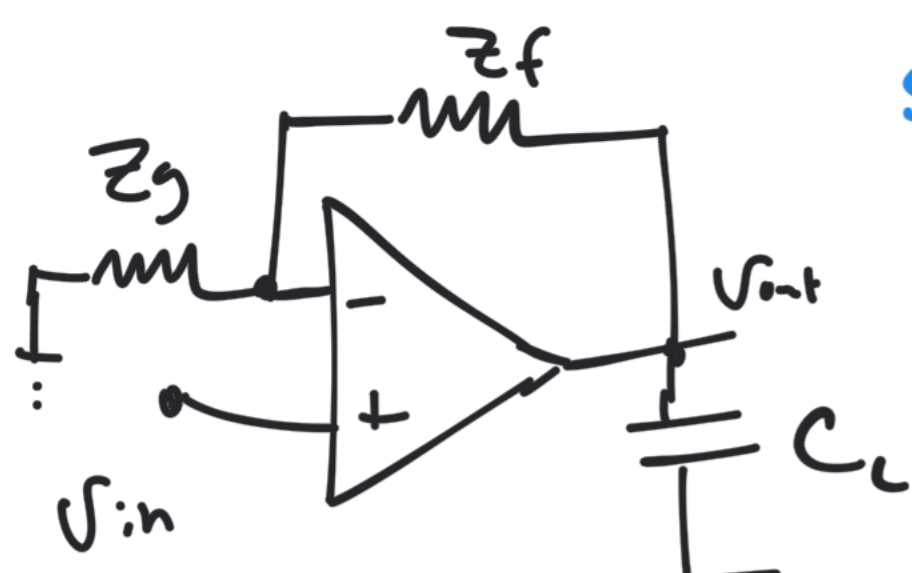
So, C_L (in conjunction w/ non-zero Z_o) slows down output response which adds ^{more} phase lag to the loop...
 Already loop has phase lag due to poles of open-loop gain A ... more phase lag means more chance of going unstable...



DC: $\frac{V_{out}}{V_{in}} = 1 + \frac{Z_f}{Z_g}$
 (ideal)

Remedy 1

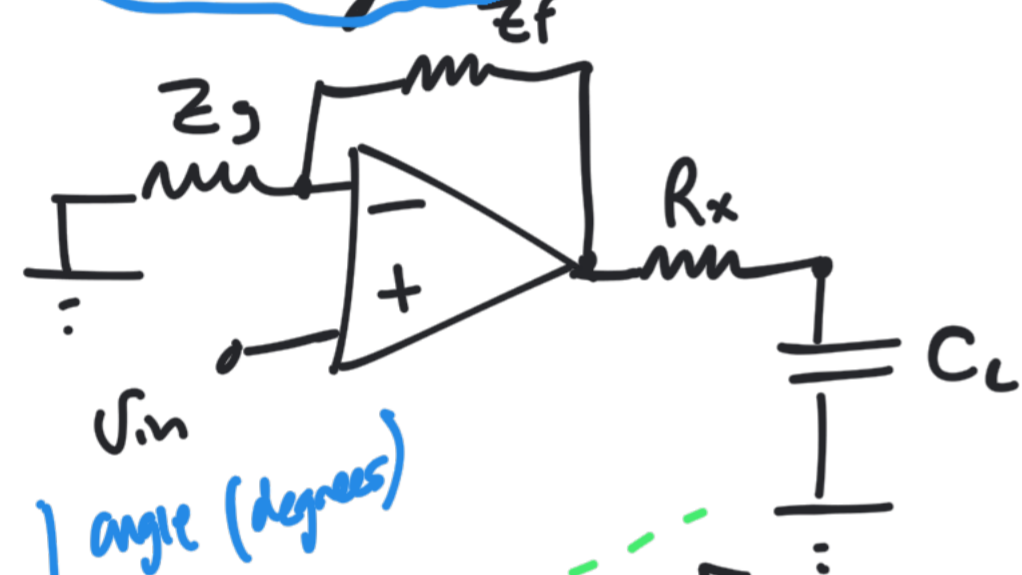see "Ask the Applications Engineer. 25" by Grayson King





$$A\beta = \left(\frac{A Z_g}{Z_g + Z_f} \right) \frac{R_x + \frac{1}{s C_L}}{R_x + \frac{1}{s C_L} + Z_o}$$

$$= \frac{A Z_g}{Z_g + Z_f}$$


$$\frac{s R_x C_L + 1}{(Z_o + R_x) s C_L + 1}$$

Bode plot

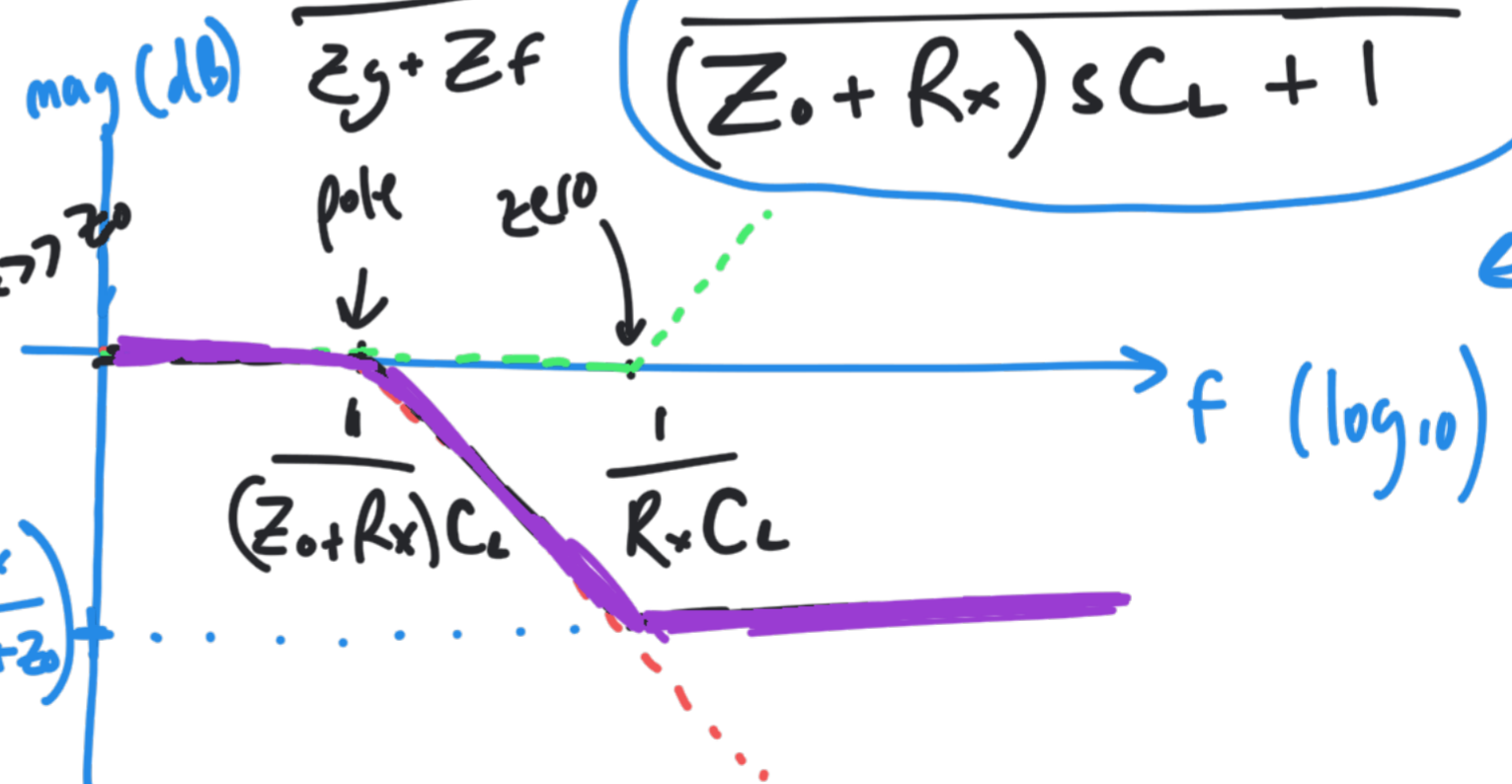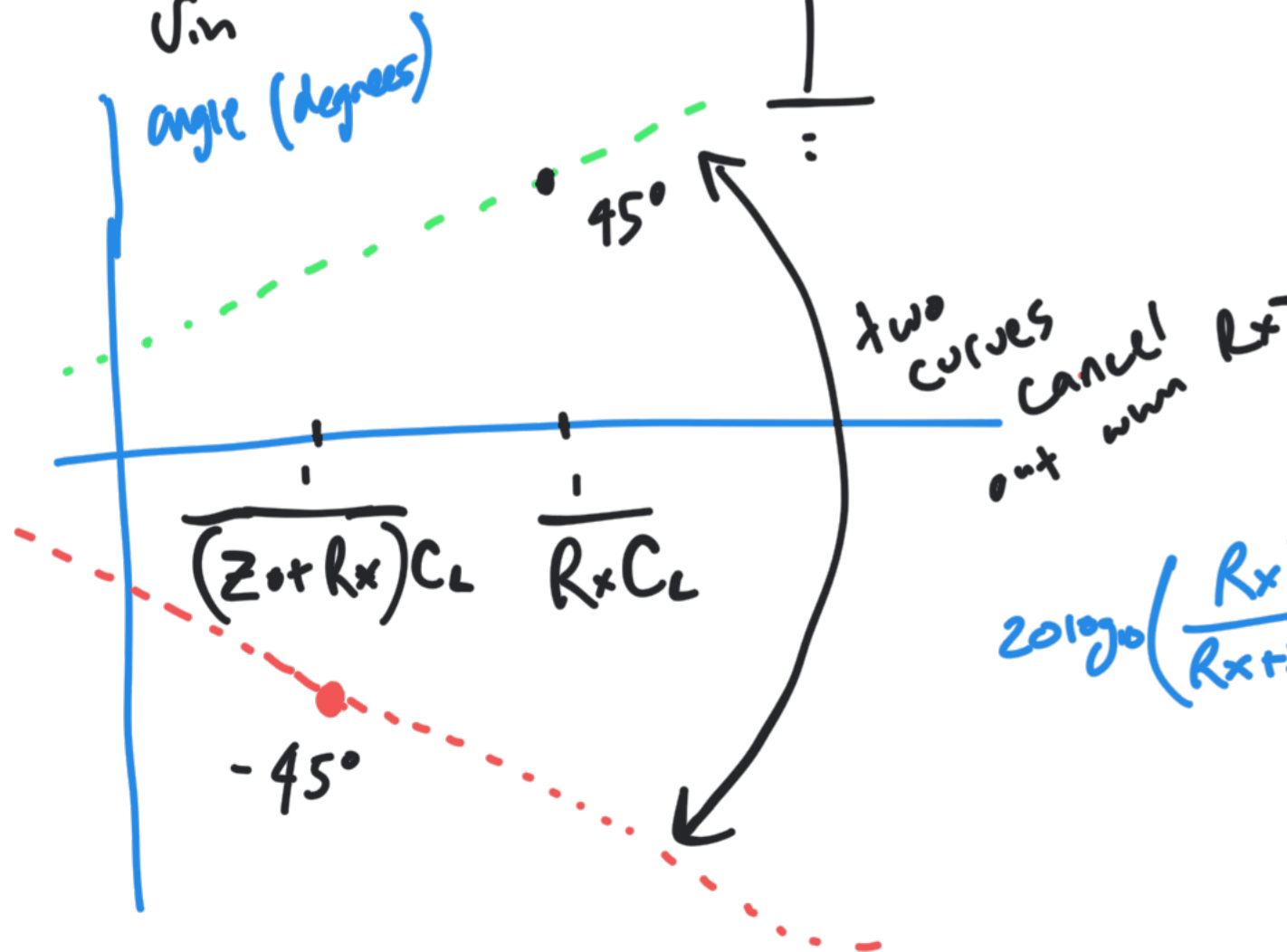

Advantages: one part solution
 Disadvantages: output impedance seen by load increases. This can decrease signal gain due to resistor divider action.



Remedy 1 cont.

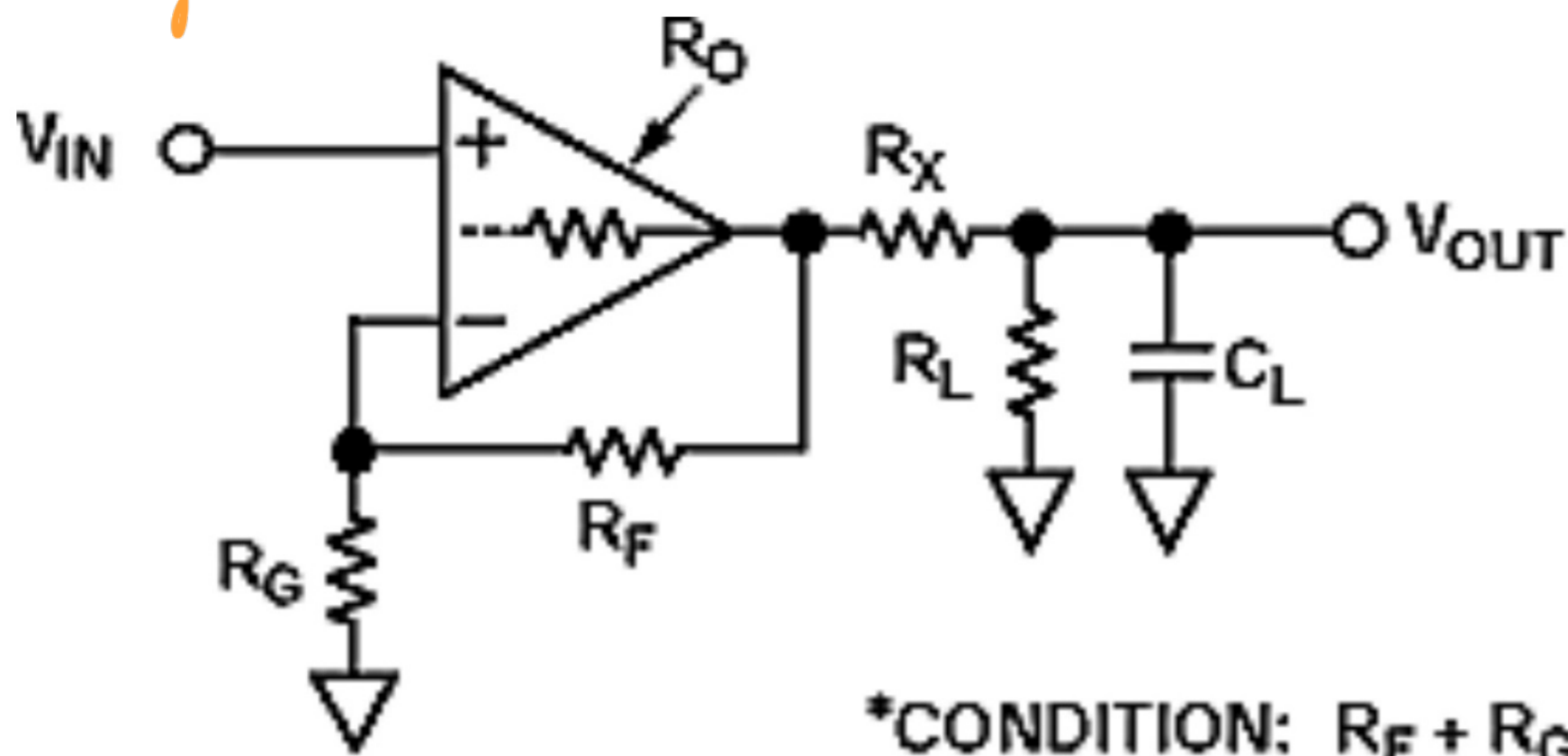

$$*f_z = \frac{1}{2p[(R_O + R_X) \parallel R_L]C_L}$$

$$= \frac{1}{2pR_O + R_X) C_L} + \frac{1}{2pR_L C_L}$$


*CONDITION: $R_F + R_G \gg R_O$

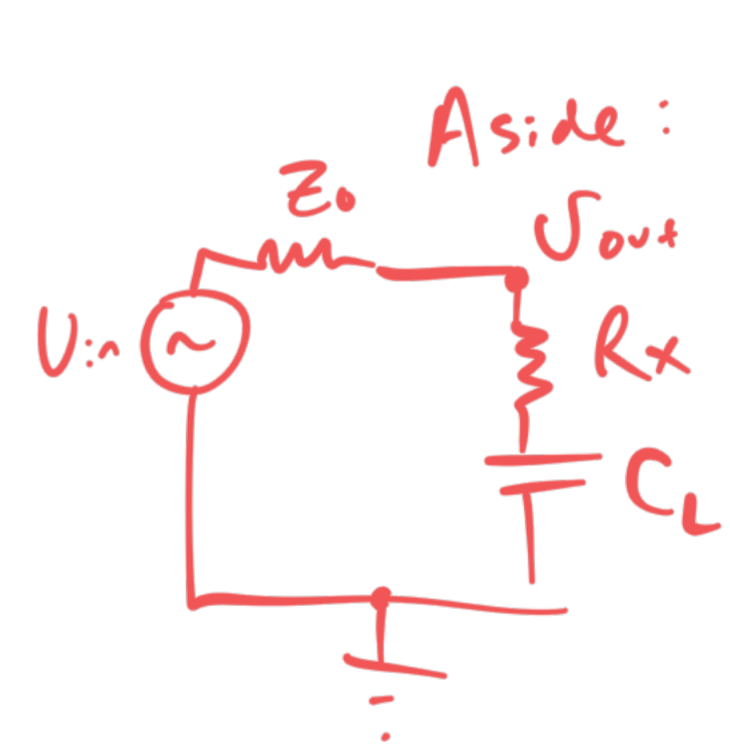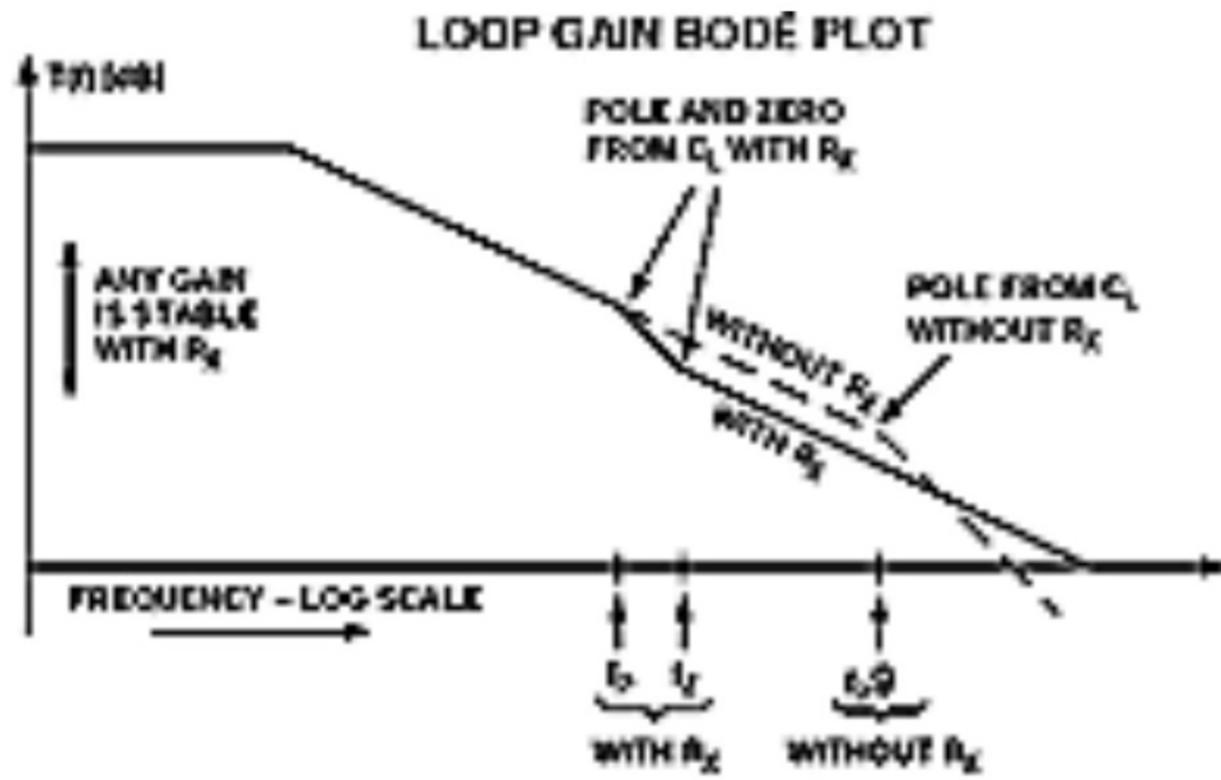

Aside:

$$V_{out} = V_{in} \left(\frac{R_X + \frac{1}{sC_L}}{R_X + \frac{1}{sC_L} + Z_o} \right)$$
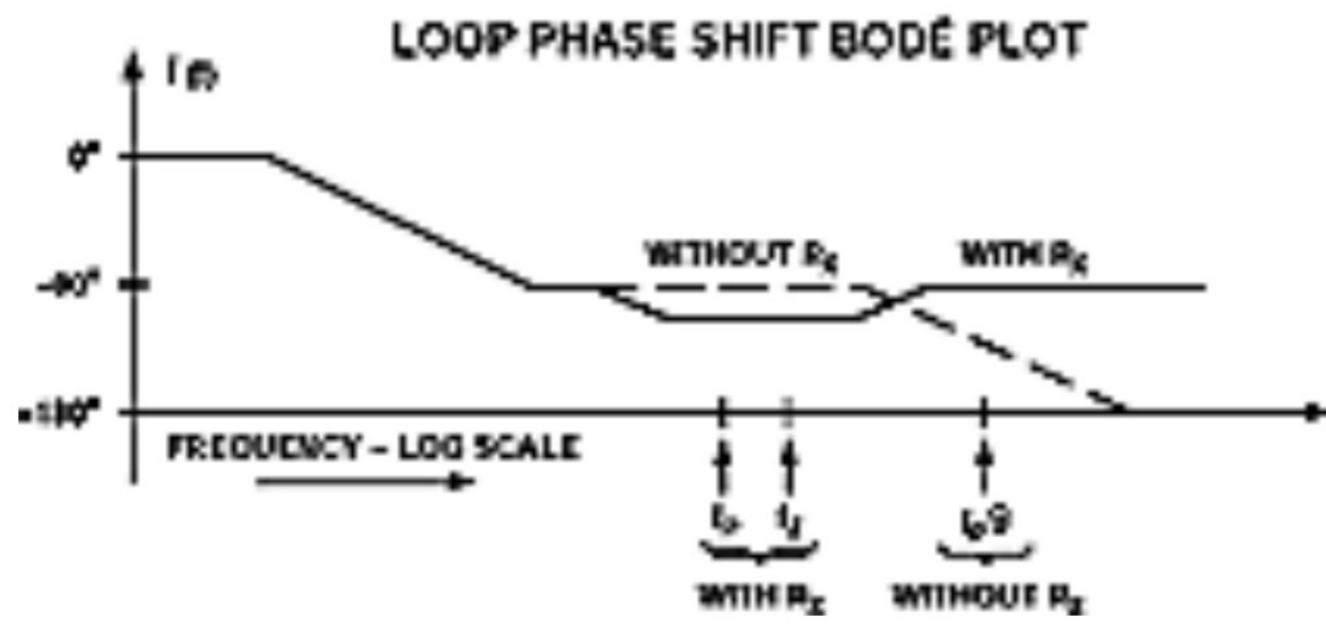
$$\frac{V_{out}}{V_{in}} = \frac{1 + sC_L R_X}{1 + sC_L (R_X + Z_o)}$$




Remedy 2 Increase closed loop gain (i.e. signal gain)

Simplest method!

$$A\beta = \frac{AZ_g}{Z_g + Z_f} \cdot \frac{1}{1 + sC_L Z_o}$$

decrease this factor!

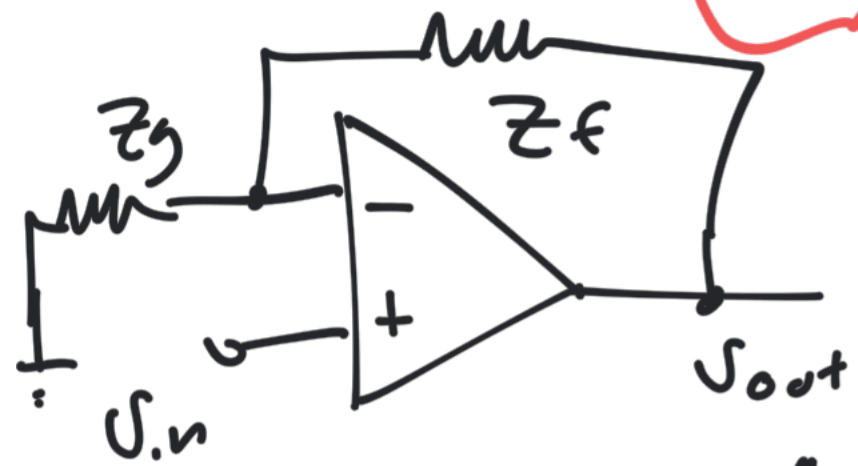

$$\frac{1}{\beta} = \frac{Z_g + Z_f}{Z_g}$$

signal gain = $\frac{A}{1 + A\beta} \approx 1 + \frac{Z_f}{Z_g}$ for large $A\beta \gg 1$

decrease $\beta \rightarrow$ increase $\frac{1}{\beta} \rightarrow$ increase signal gain \rightarrow decrease loop gain $A\beta$
 (stability increases!)


Advantages: very simple

Disadvantages: You may have to deal w/ a bunch of unwanted gain... power waste!

Remedy 3


Noise gain manipulation

original:

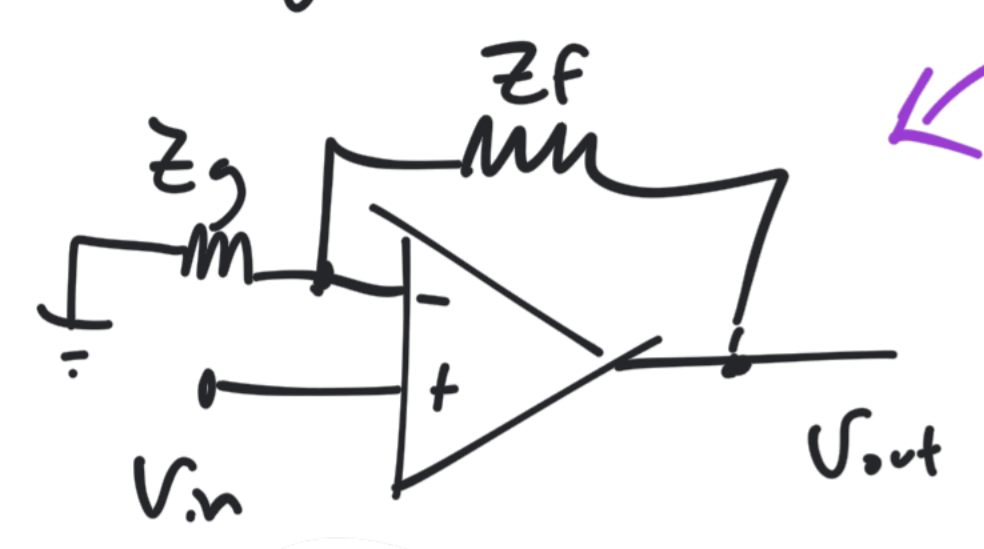

same signal gain: $1 + \frac{Z_f}{Z_g}$ ← ideal of amp

⇒

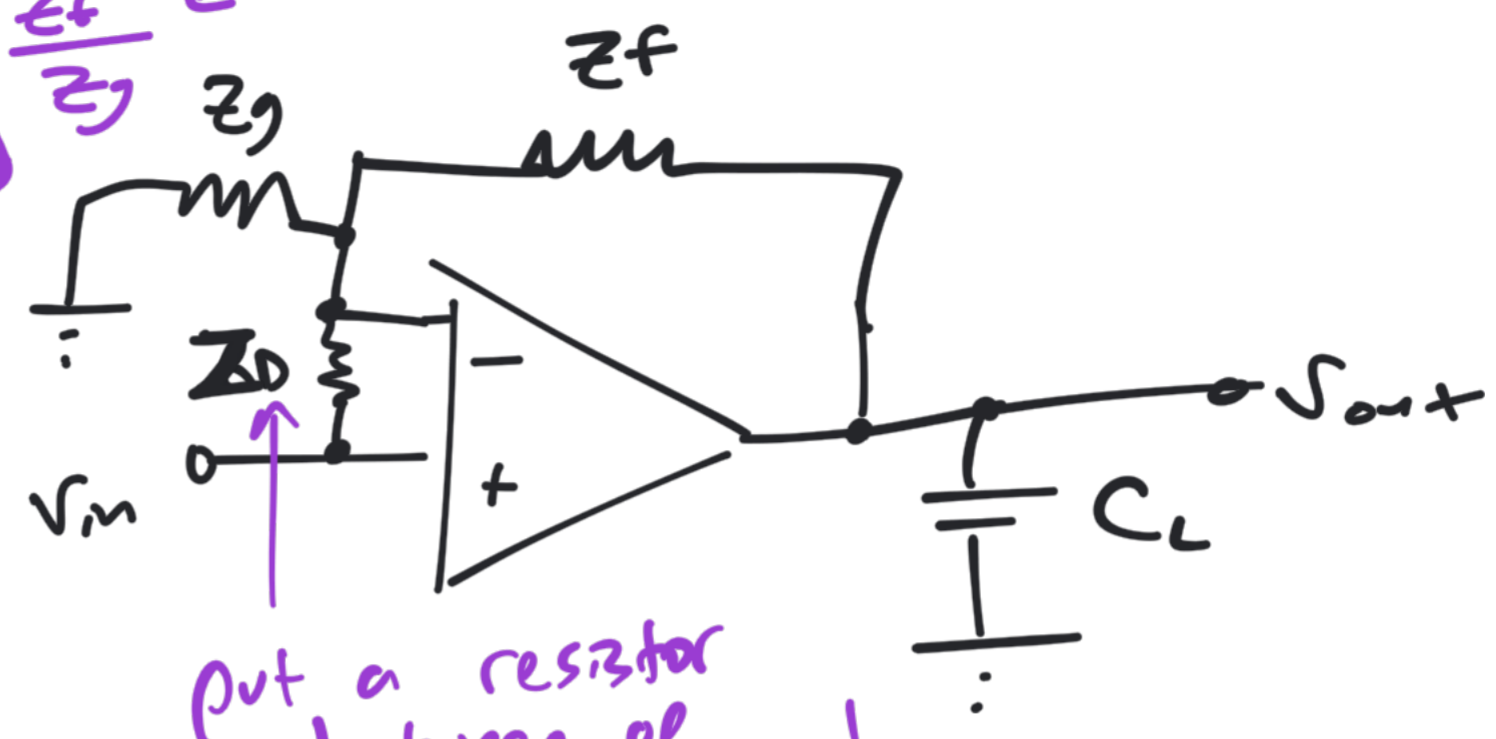

put a resistor between amp inputs!

In this case:

$$A\beta = A \frac{Z_g \parallel Z_0}{Z_g \parallel Z_0 + Z_f} \frac{1}{1 + sC_L Z_0}$$


Advantages: Does not change signal gain.

Disadvantages: Increases noise...

I'm guessing this also "messes with" input impedance (i.e. lowers it)

Remedy 4

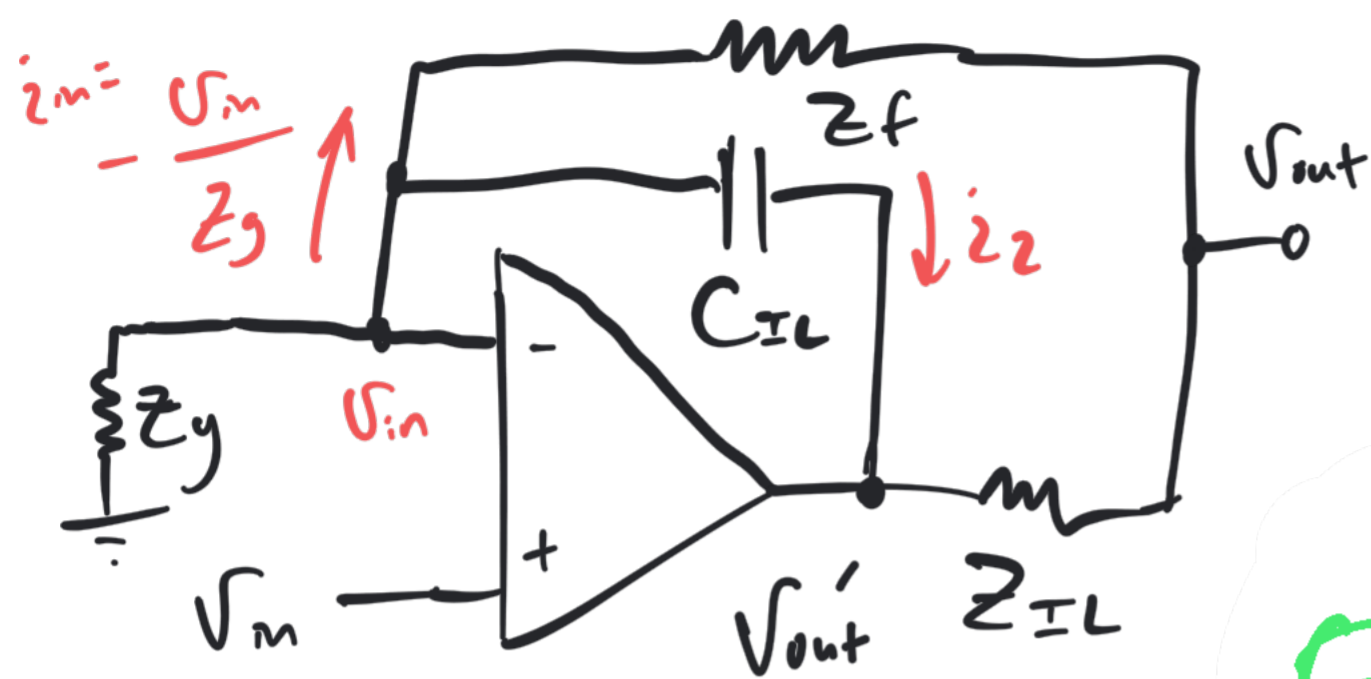
Split feedback (sometimes called "in-the-loop" compensation method)
 See "Ask the application engineer-32"



ideal op amp:

$$\textcircled{1} \dot{i}_1 = \dot{i}_m \left(\frac{\frac{1}{sC_{IL}}}{\frac{1}{sC_{IL}} + Z_f + Z_{IL}} \right)$$

recall:

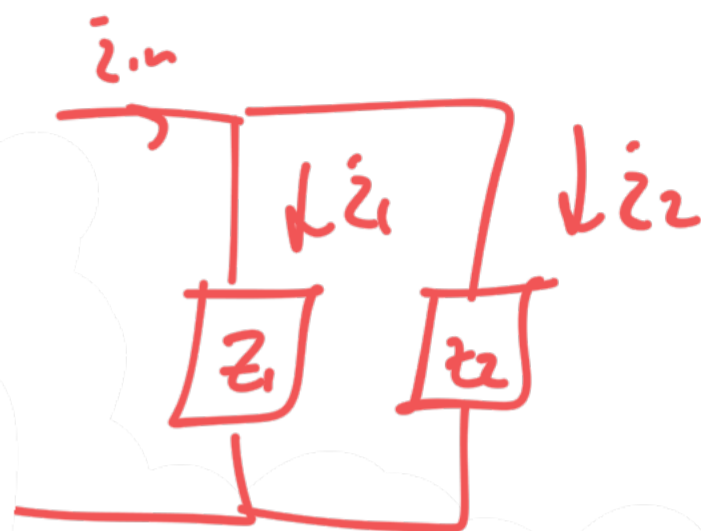

$$i_1 = i_m \frac{Z_2}{Z_1 + Z_2}$$

First, find closed loop gain:


$$\therefore \frac{V_m - V_{out}}{Z_f} = -\frac{V_m}{Z_g} \left(\frac{1}{1 + sC_{IL}(Z_f + Z_{IL})} \right)$$

$$V_{out} = V_m + \frac{Z_f}{Z_g} V_m \left(\frac{1}{1 + sC_{IL}(Z_f + Z_{IL})} \right)$$

$$\frac{V_{out}}{V_m} = 1 + \frac{Z_f}{Z_g} \left(\frac{1}{1 + sC_{IL}(Z_f + Z_{IL})} \right)$$

if $Z_f \gg Z_{IL}$ then closed loop BW
 $= \frac{1}{2\pi C_f Z_f}$

Remedy 4
cont.

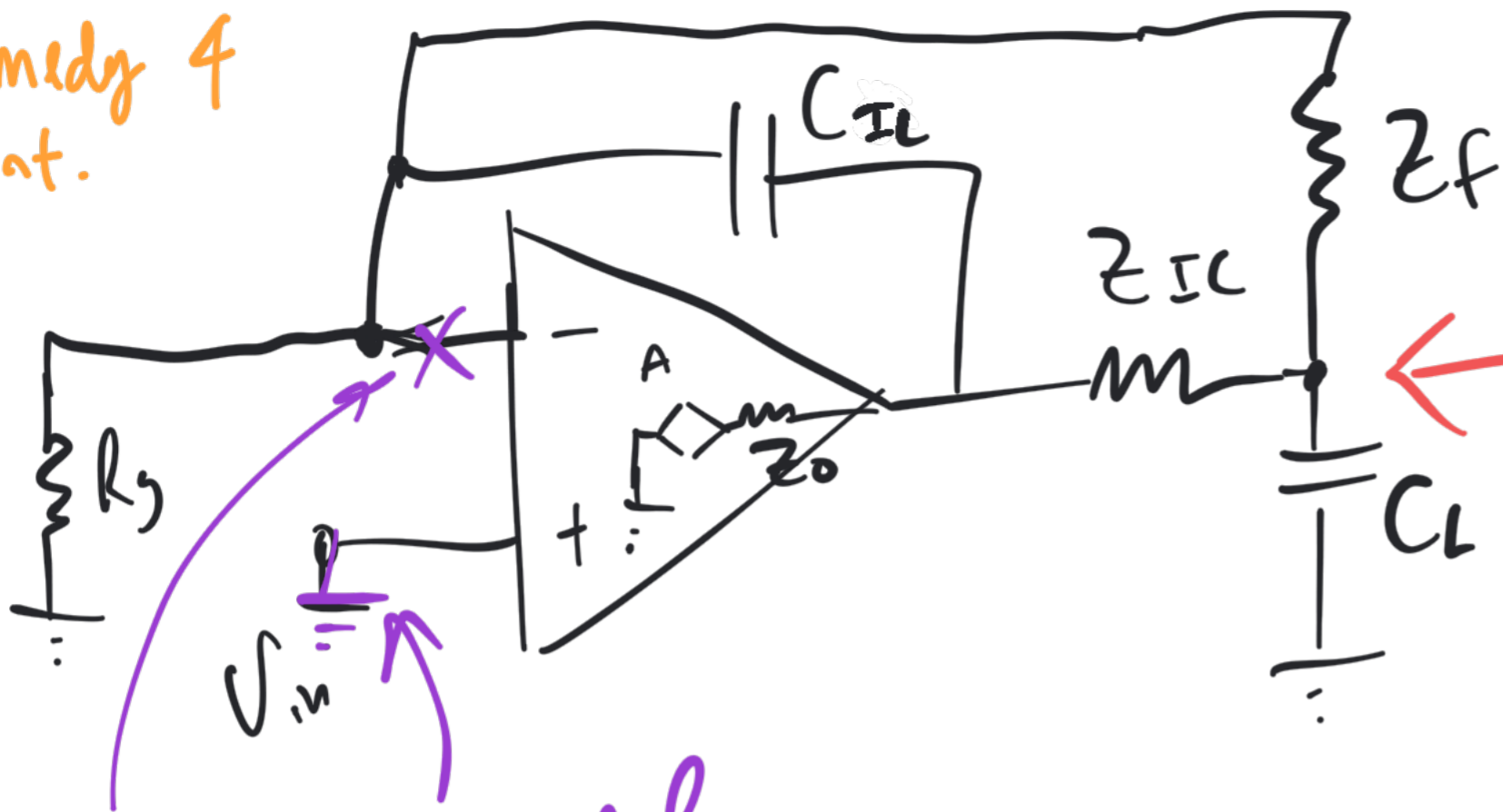

at low frequencies:

$C_{IL} \approx \text{open}$


$Z_{in} \approx 0$

since Z_{IL} is

in the loop!

(this is desired)...


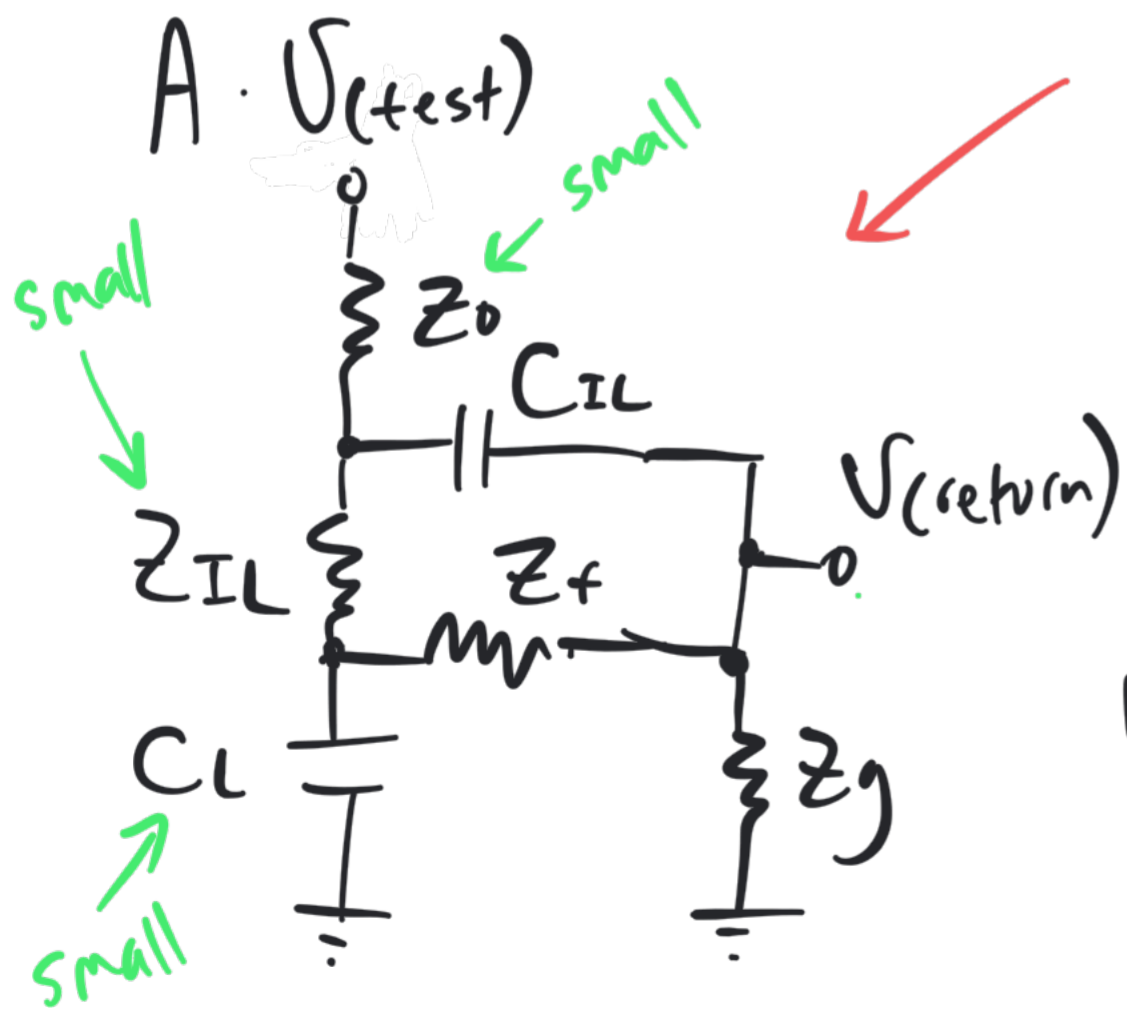
Calculate $A\beta$:
Break the loop!
and set $V_{in} = 0V$



Two caps separated by resistors means we have two poles! (pole-splitting)


C_L & $C_{IL} = \text{open (low f)}$
 short (high f)

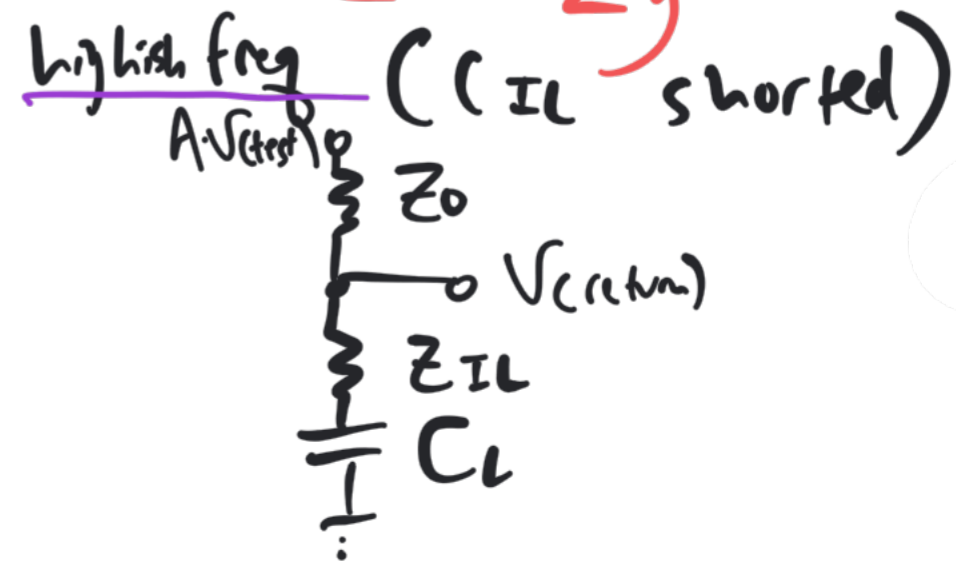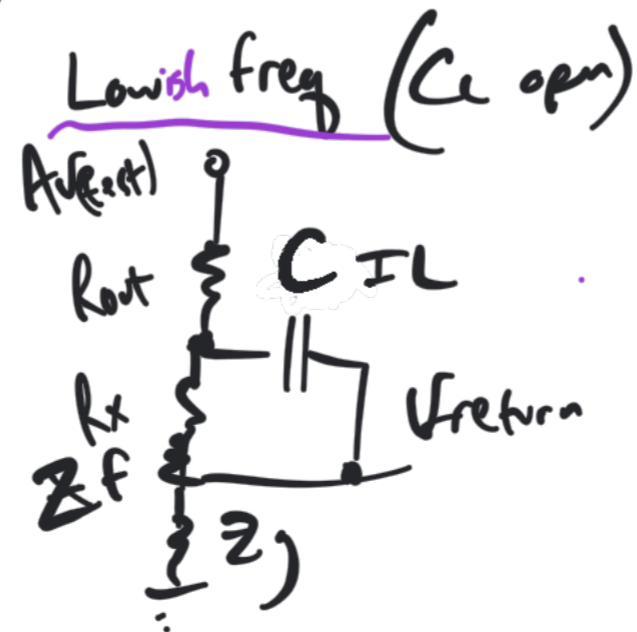design: $C_{IL} \gg C_L$
 $Z_{IL} \ll Z_f$
 $Z_o \ll Z_g$



can find sets of 2 poles and 2 zeros equal to cancel them out!

Remedy 4 cont.

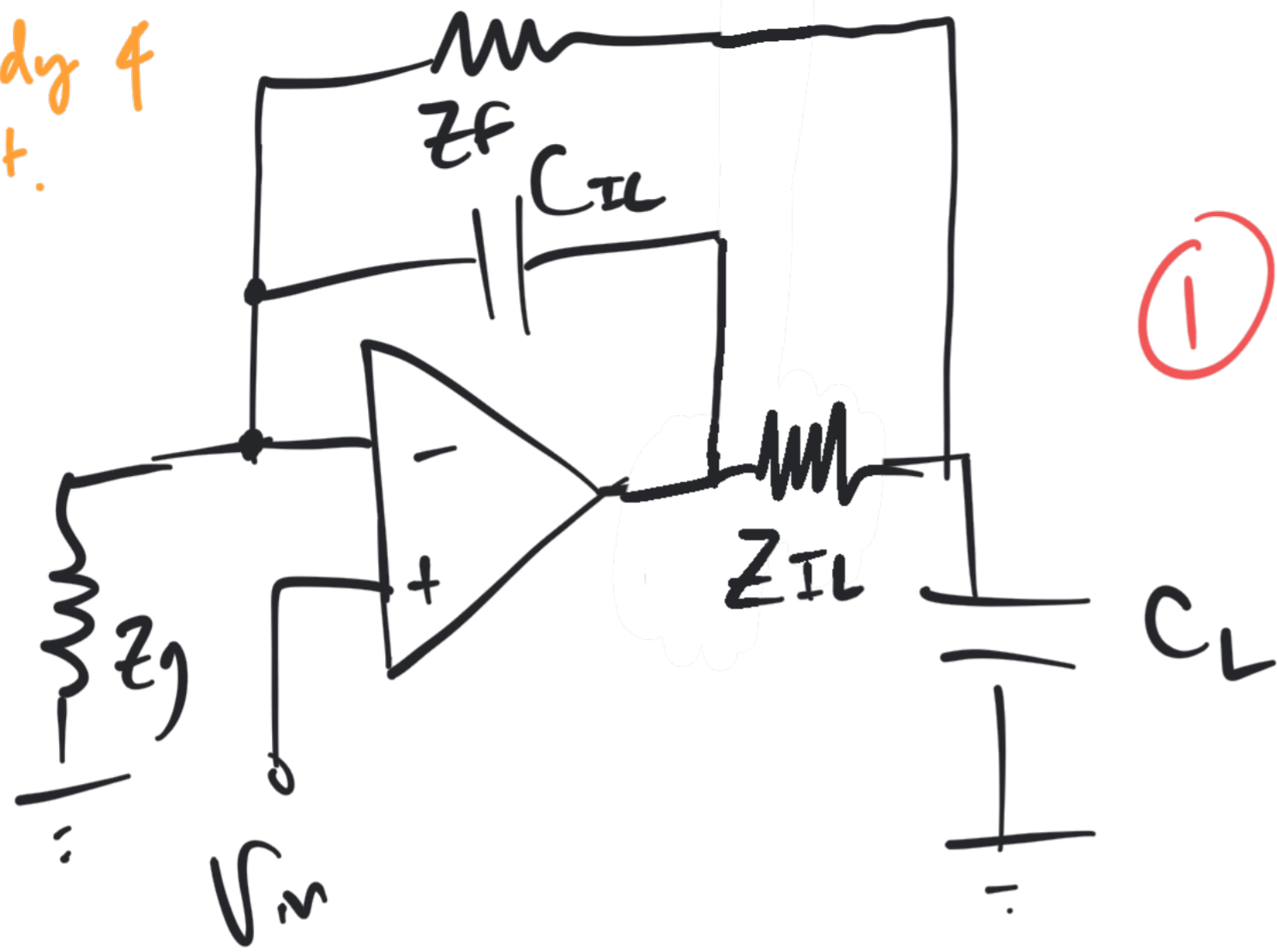


Another way to look @ problem

① At low frequencies:

$C_{IL} \approx \text{open}$
 $C_L \approx \text{open}$

← don't need to worry about

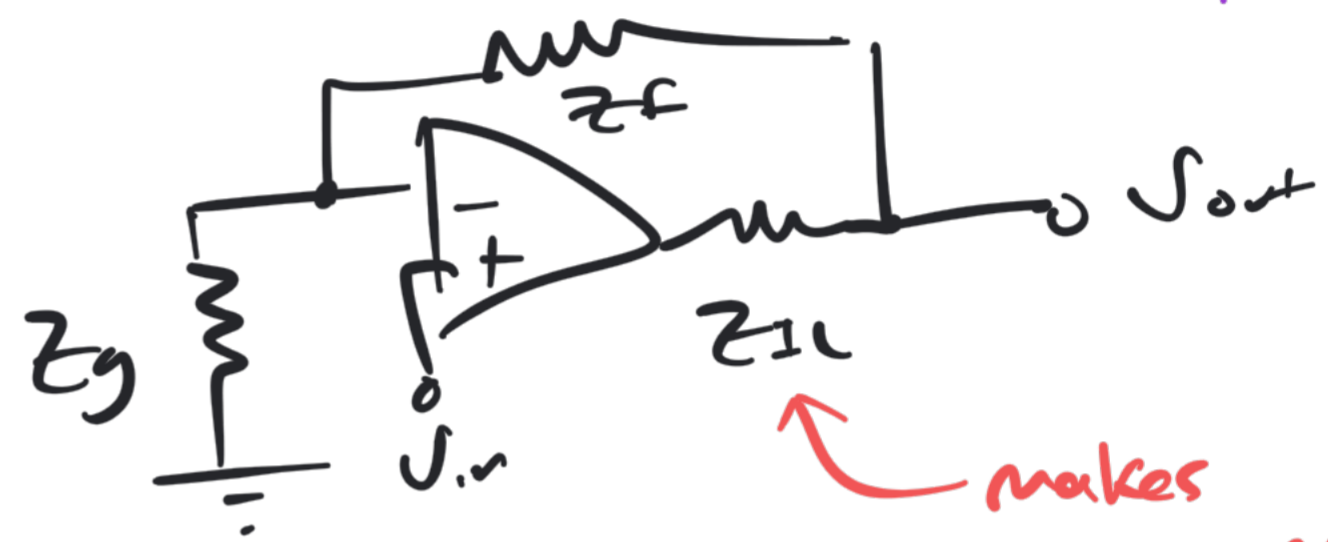


(i.e. phase shift due to $Z_{IL}C_L$ is small)

no difference (since it's in the loop!)

← still not a big deal...

i.e. phase shift due to $(\frac{Z_{IL}}{Z_o})C_L$ is still small

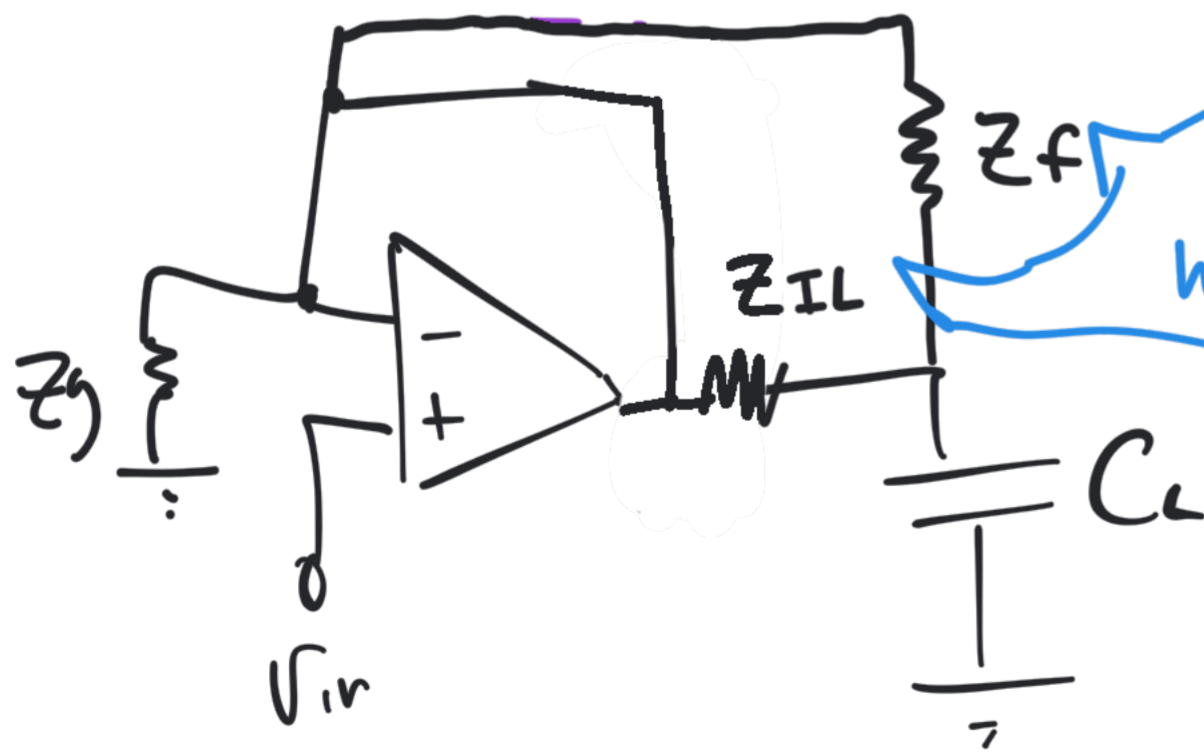
② At mid-frequencies: $C_{IL} \approx \text{short}$
 $C_L \approx \text{open-ish}$



hi, we are here to stop you from creating oscillations!

Ah, shucks!


(possible) remedy 5

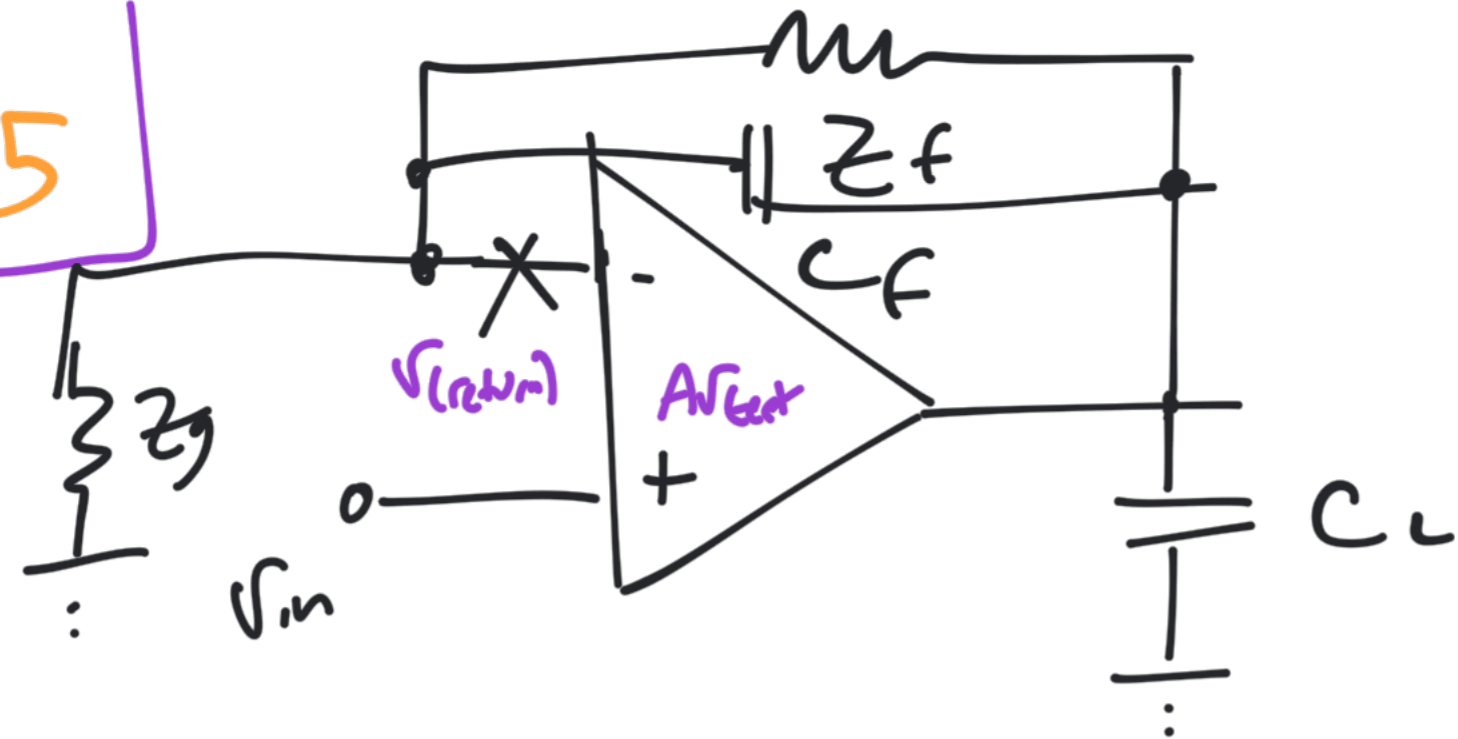

$A\beta$ calculation:

$$V_{(return)} = A V_{(test)} \cdot \frac{C_L \parallel (C_f \parallel Z_f + Z_g)}{C_L \parallel (C_f \parallel Z_f + Z_g) + Z_o}$$
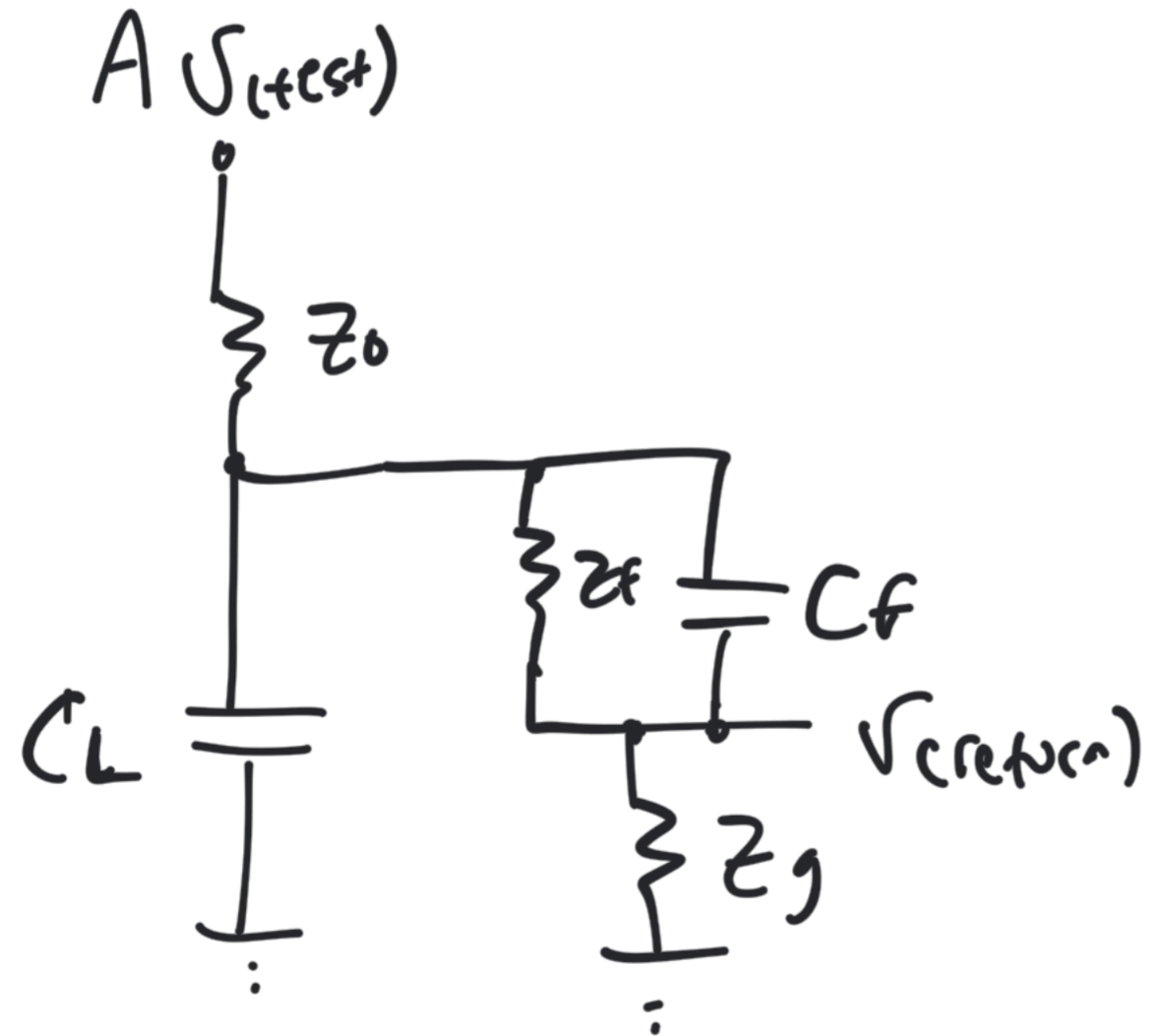
$$\frac{C_L \parallel (C_f \parallel Z_f + Z_g)}{Z_g + Z_f \parallel C_f}$$




To much algebra for me...
 if I use previous approx:
 pole: $\frac{1}{2\pi Z_o C_L}$, $\frac{1}{2\pi (Z_f \parallel Z_g) C_f}$ *make large*
 zeros: ∞ , $\frac{1}{2\pi Z_f C_f}$ *cancel out pole maybe?*
larger freq
smaller freq


Bad

input capacitance:

← also causes instabilities

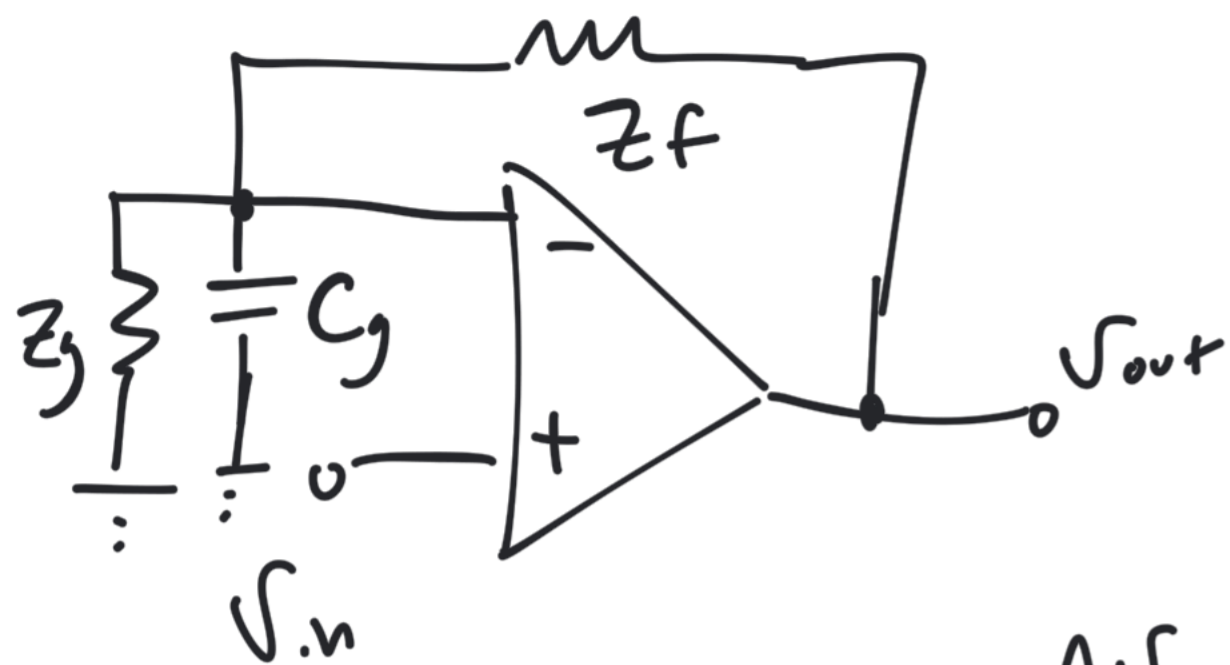

find $A\beta$:

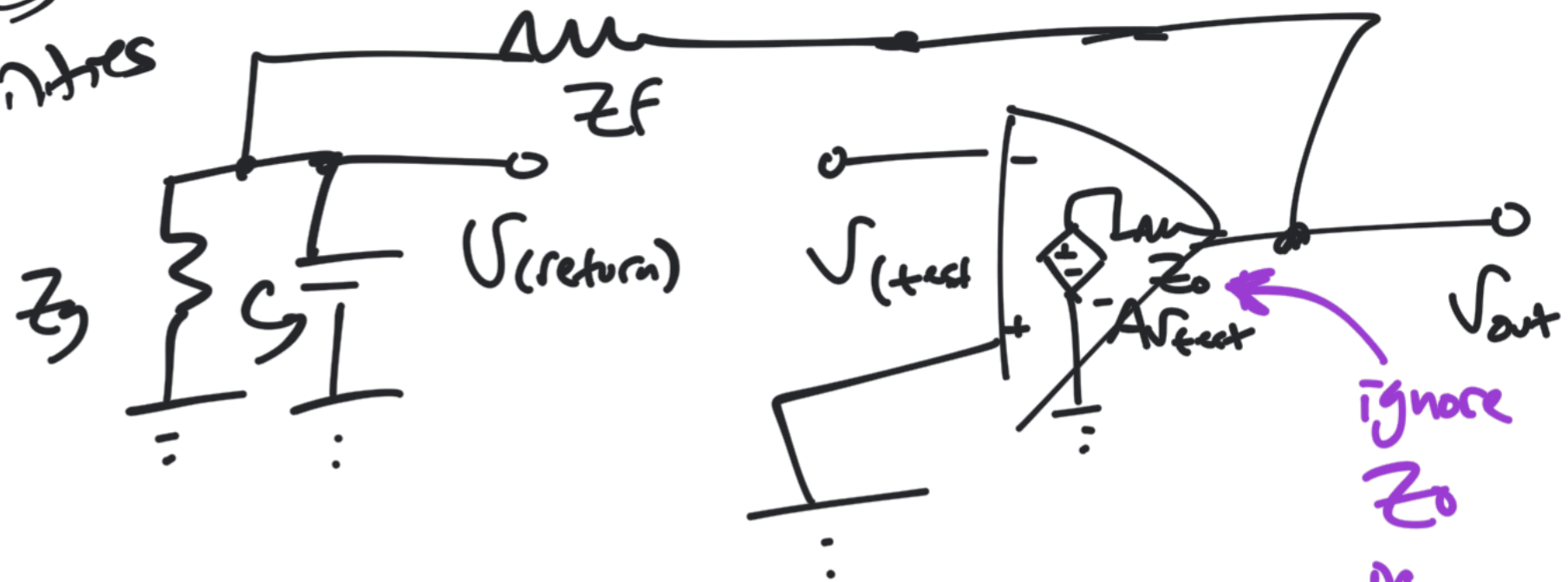

$A V_{test}$

Z_f

V_{return}

R_g

C_g

\vdots

$$\frac{V_{return}}{V_{test}} = A \frac{Z_g}{Z_g + Z_f}$$

$$= A \frac{R_g}{R_g + Z_f (1 + s C_g R_g)}$$

$$= A \frac{R_g}{(R_g + Z_f) + s C_g R_g Z_f}$$

$$= A \frac{R_g}{R_g + Z_f} \cdot \left(\frac{1}{1 + (R_g || R_f) s C_f} \right)$$


can add instability!

pole @ $(R_g || R_f) C_f$

$$\begin{aligned} Z_g & \parallel C_g \\ & \parallel R_g \\ & \parallel \frac{R_g}{s C_g} \\ & = R_g + \frac{1}{s C_g} \end{aligned}$$

$$\frac{R_g}{1 + s C_g R_g}$$

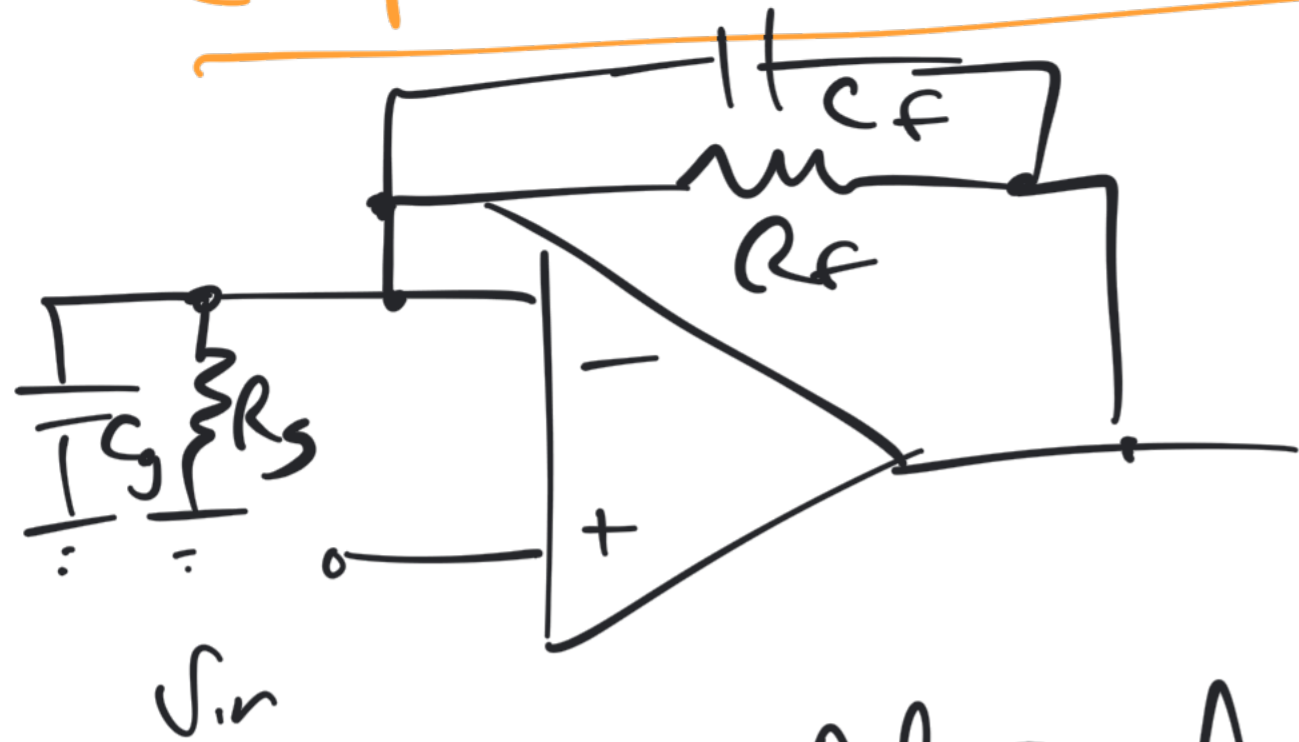Compensation method for input capacitance



$$Z_f = \frac{R_f}{sC_f R_f} = \frac{R_f}{sC_f R_f + 1}$$

$$Z_g = \frac{R_g}{sC_g R_g + 1}$$


From previous figure $\rightarrow A\beta = A \frac{Z_g}{Z_f + Z_g}$

$$= A \left(\frac{\frac{R_g}{sC_g R_g + 1}}{\frac{R_g}{sC_g R_g + 1} + \frac{R_f}{sC_f R_f + 1}} \right)$$

Let $R_g C_g = R_f C_f$: $A\beta = A \frac{R_g}{R_g + R_f}$

Cool!

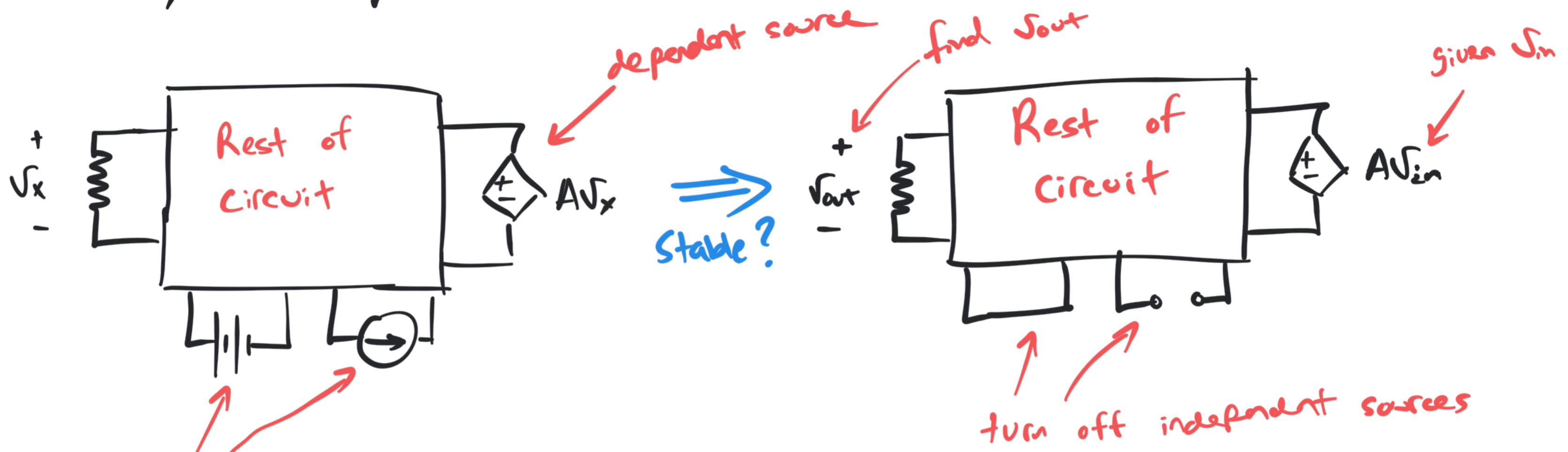Return ratio: another (related) way to determine stability ... works great for sources w/ one dependent source ...



independent sources

$$R = \text{Return ratio} = - \frac{V_{out}}{V_{in}}$$

circuit unstable if: $|R| \geq 1$
when

$$\angle R = 180^\circ + n360^\circ$$


NOTE: in general $R \neq \beta A$

Good paper: Demystifying Bilateral Feedback analysis
by Yun Chin

The general idea


Makes sense:

here $|R| \geq 1$
when $\angle R = 180^\circ$
... positive feedback
uncontrolled
regeneration!

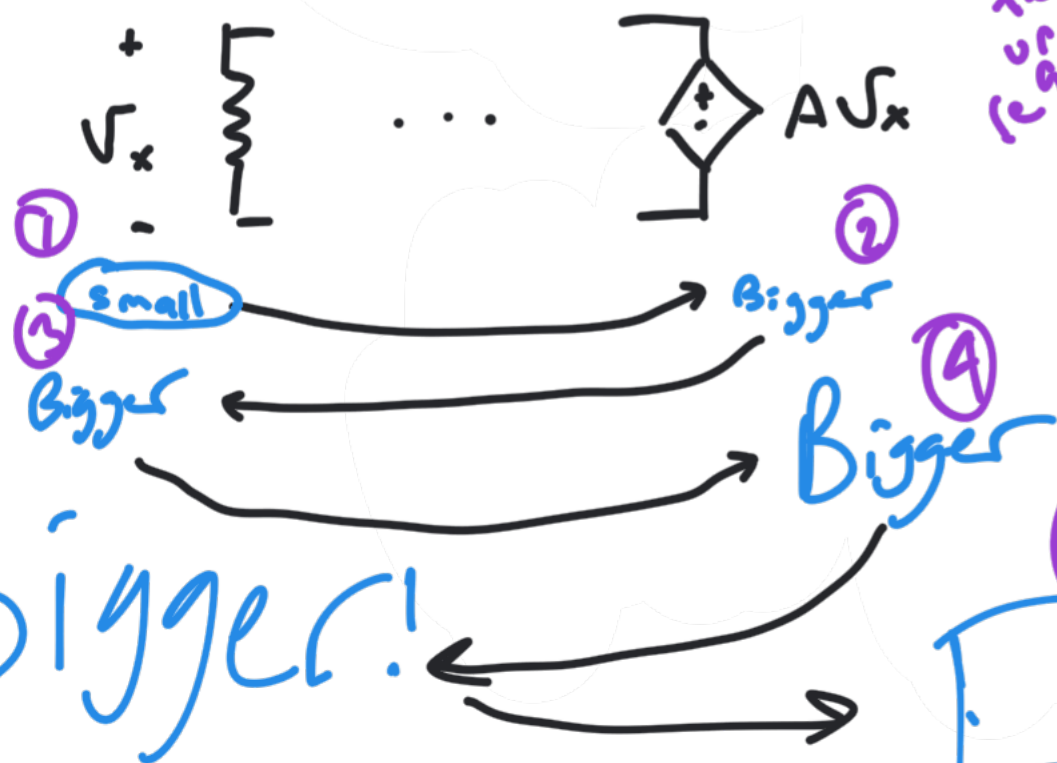


BIGGER

Exemple

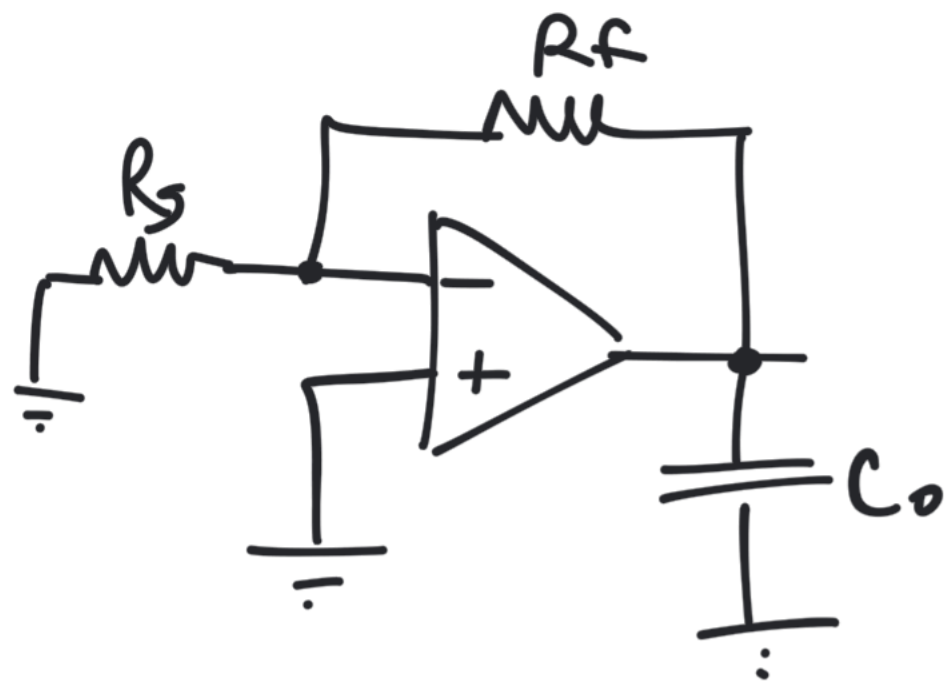

return ratio

Egon circuit

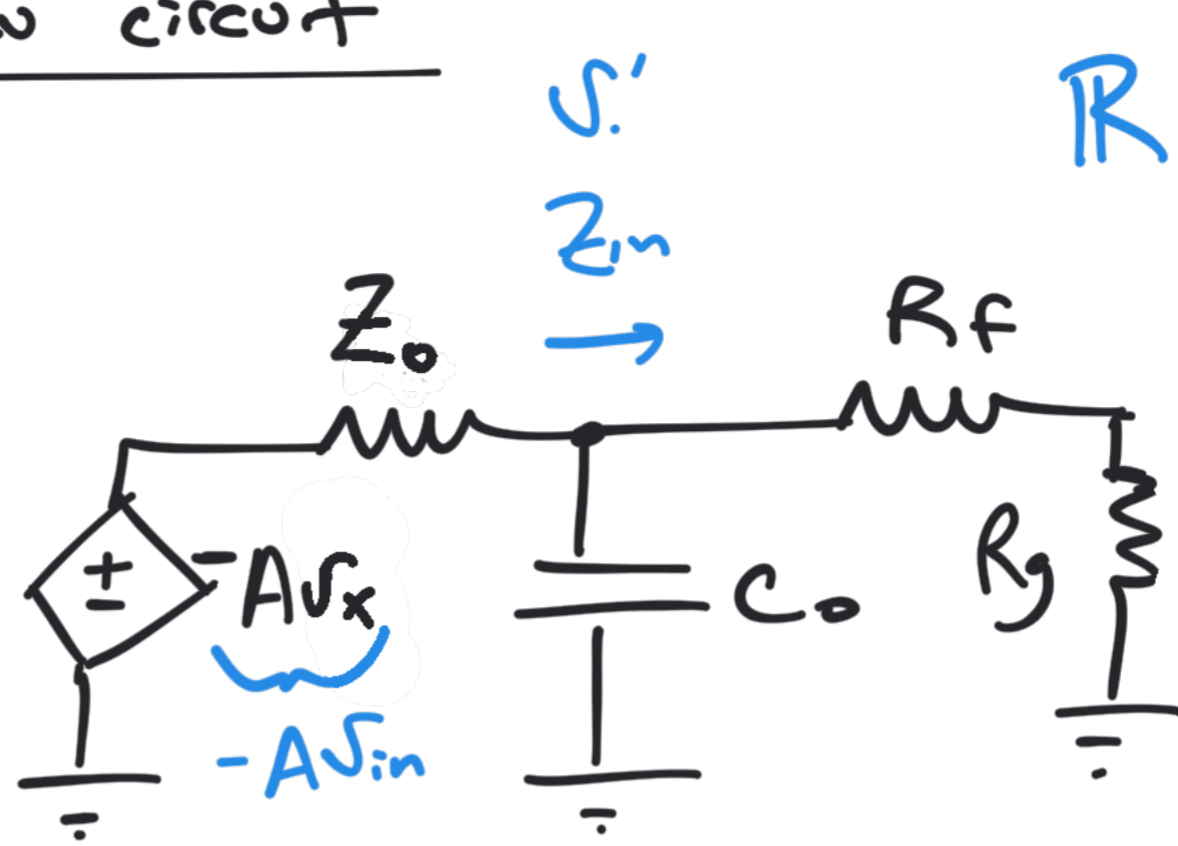

$$R = -\frac{V_{out}}{V_{in}}$$

unstable when:
 $|R| > 1$
 for $\angle R = 180^\circ + n360^\circ$

$$R = A \frac{R_g}{R_g + R_f} \frac{1}{1 + sC_o Z_o}$$

$$R = -\frac{V_{out}}{V_{in}}$$

$$Z_{in} = \frac{1}{sC_o} \parallel (R_f + R_g) = \frac{R_f + R_g}{1 + sC_o(R_f + R_g)}$$

$$V' = \frac{Z_{in}}{Z_{in} + Z_o} (-AV_{in})$$


$$= \frac{(R_f + R_g)}{(R_f + R_g) + Z_o + sC_o Z_o (R_f + R_g)} (-AV_{in})$$

$$\approx \frac{1}{1 + sC_o Z_o}$$

$$\frac{V_{out}}{V_{in}} = \frac{V' \left(\frac{R_g}{R_f + R_g} \right)}{V_{in}} = \frac{R_g}{R_f + R_g} \frac{-A}{1 + sC_o Z_o}$$


Stability analysis BJT transistor amplifiers

① original

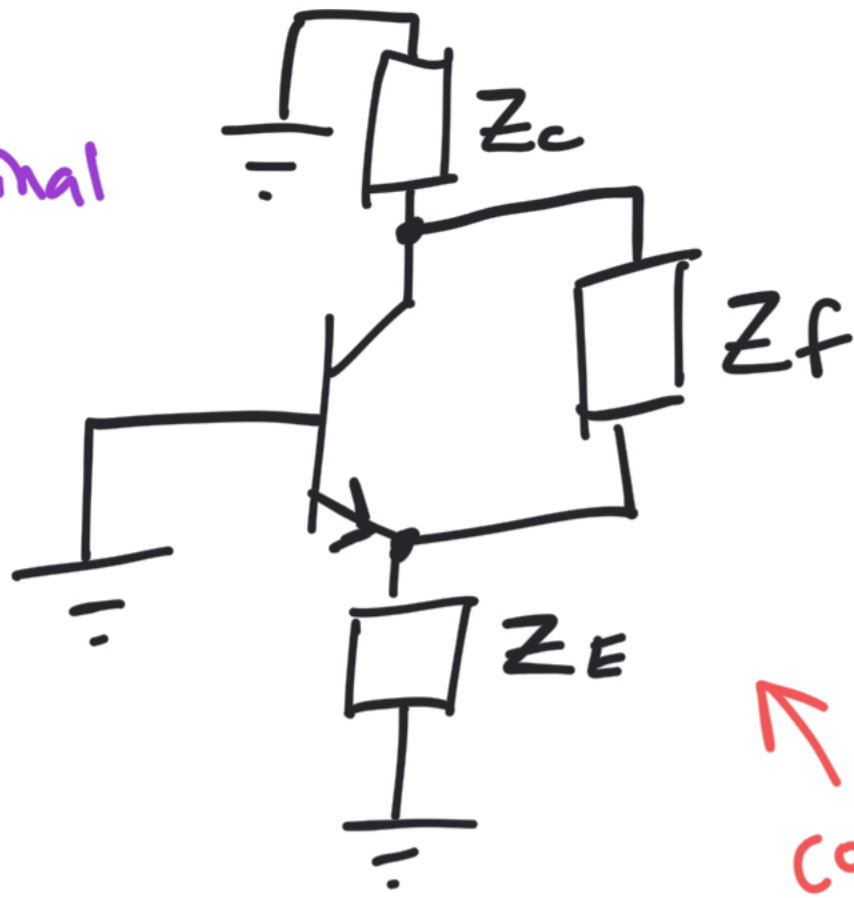


Small signal model

② small signal

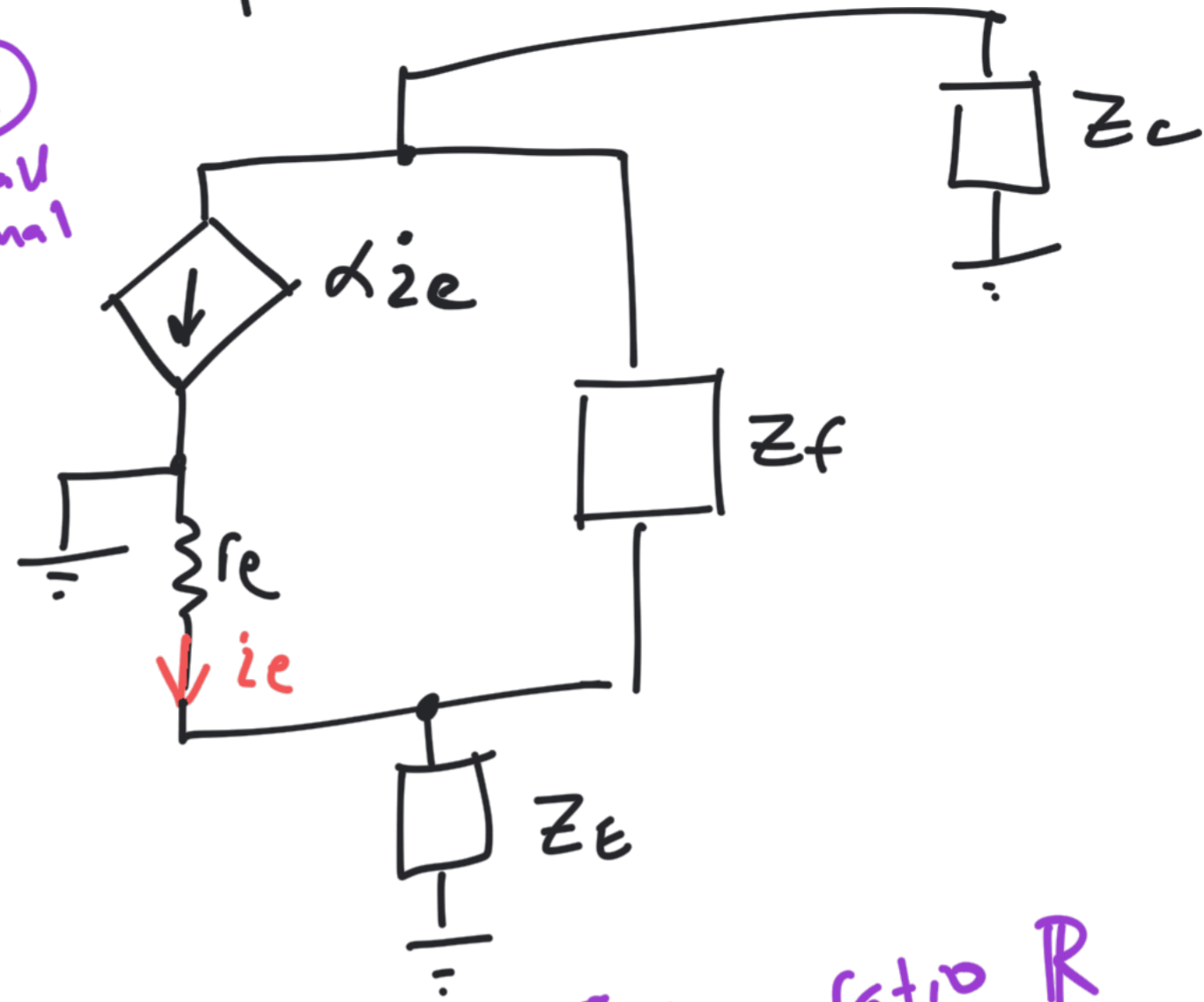


Common base configuration

③ re-draw small signal

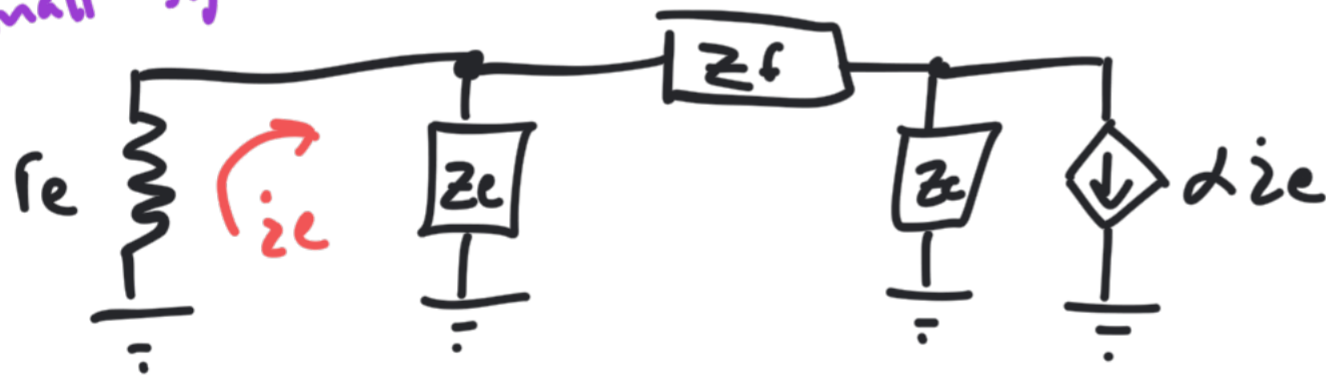

④ Find Return ratio R

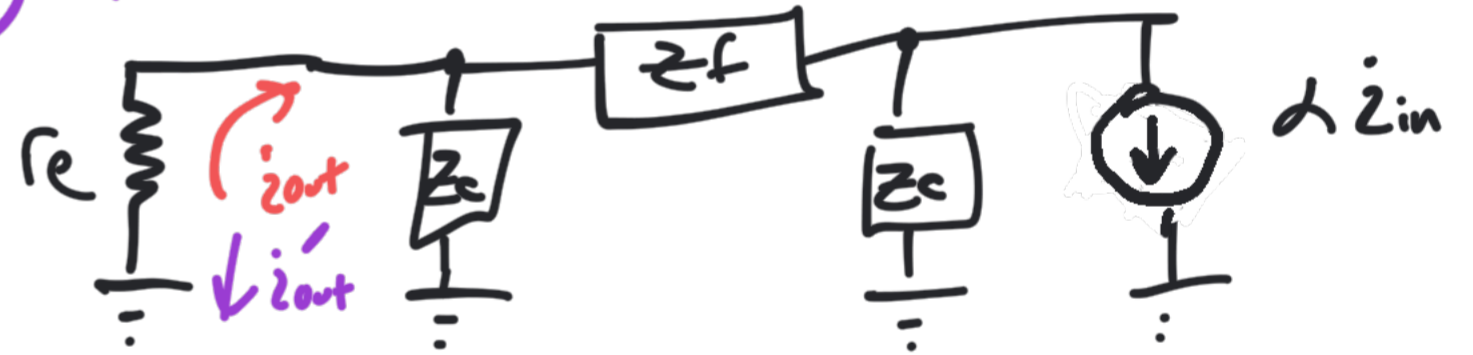

$$R = - \frac{i'_{out}}{i'_{in}} = \frac{i'_{out}}{i'_{in}}$$

circuit unstable


if $|R| > 1$

when $\angle R = 180^\circ + n360^\circ$


From previous slide:

①


Find Return ratio R

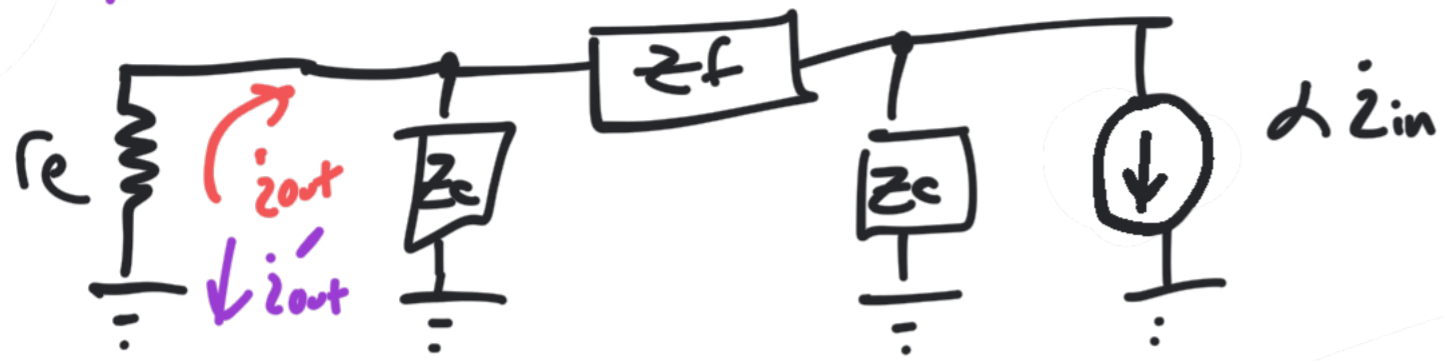

②

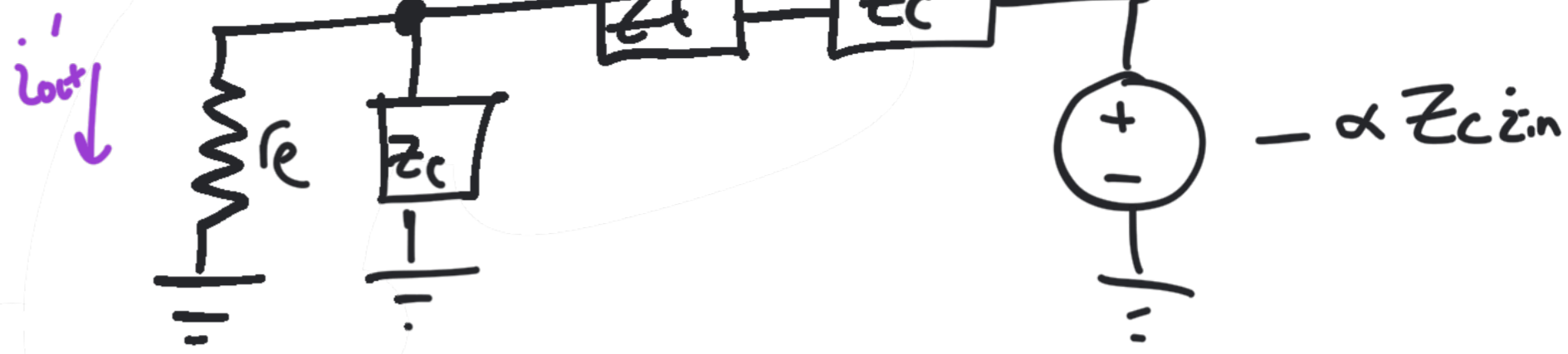

③

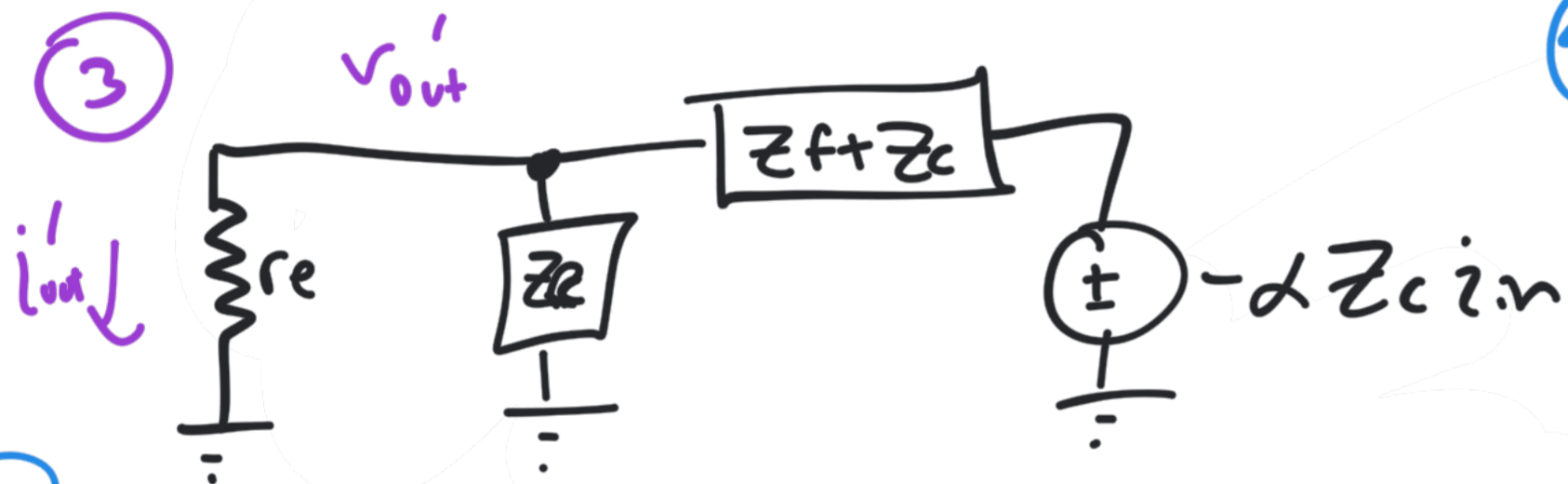

④

Voltage divider rule:

$$v'_{out} = \frac{r_e \parallel Z_c}{r_e \parallel Z_c + Z_f + Z_c} (-\alpha Z_c i_{in})$$

⑤

$$i'_{out} = \frac{v'_{out}}{r_e} = \frac{r_e \parallel Z_c}{r_e \parallel Z_c + Z_f + Z_c} \left(\frac{-\alpha Z_c i_{in}}{r_e} \right)$$

⑥

$$R = \frac{i'_{out}}{i_{in}} = \frac{r_e \parallel Z_c}{r_e \parallel Z_c + Z_f + Z_c} \left(\frac{-\alpha Z_c}{r_e} \right)$$

From previous slide

$$R = \frac{r_e \parallel Z_e}{r_e \parallel Z_e + Z_f + Z_c} \left(\frac{-\alpha Z_c}{r_e} \right)$$

$$\rightarrow R = \left(\frac{r_e Z_e}{r_e + Z_e} \right) \left(\frac{-\alpha Z_c}{r_e} \right) \left(\frac{1}{\frac{r_e Z_e}{r_e + Z_e} + Z_f + Z_c} \right)$$

Common base Colpitt's oscillator:

Let $Z_c = j\omega L_c$
 $Z_e = \frac{1}{j\omega C_e}$
 $Z_f = \frac{1}{j\omega C_f}$

$$R = \frac{-\alpha Z_c Z_e}{r_e Z_e + (Z_f + Z_c)(r_e + Z_e)}$$

General Equation


$$R = \frac{-\alpha Z_c Z_e}{r_e Z_e + Z_f r_e + Z_f Z_e + Z_c r_e + Z_c Z_e}$$

$$\rightarrow R = \frac{-\alpha \frac{L_c}{C_e}}{r_e \left(\frac{1}{j\omega C_e} + \frac{1}{j\omega C_f} + j\omega L_c \right) + \left(-\frac{1}{\omega^2 C_e C_f} + \frac{L_c}{C_e} \right)}$$

imaginary term

Resonance when imaginary term = 0
 $\rightarrow \omega_0 = \frac{1}{\sqrt{L_c \frac{C_e C_f}{C_e + C_f}}}$
 @ $\omega_0 \rightarrow R < -1$ for oscillator
 $\rightarrow \frac{C_e}{C_e + C_f} \geq 1 - \alpha$

Example

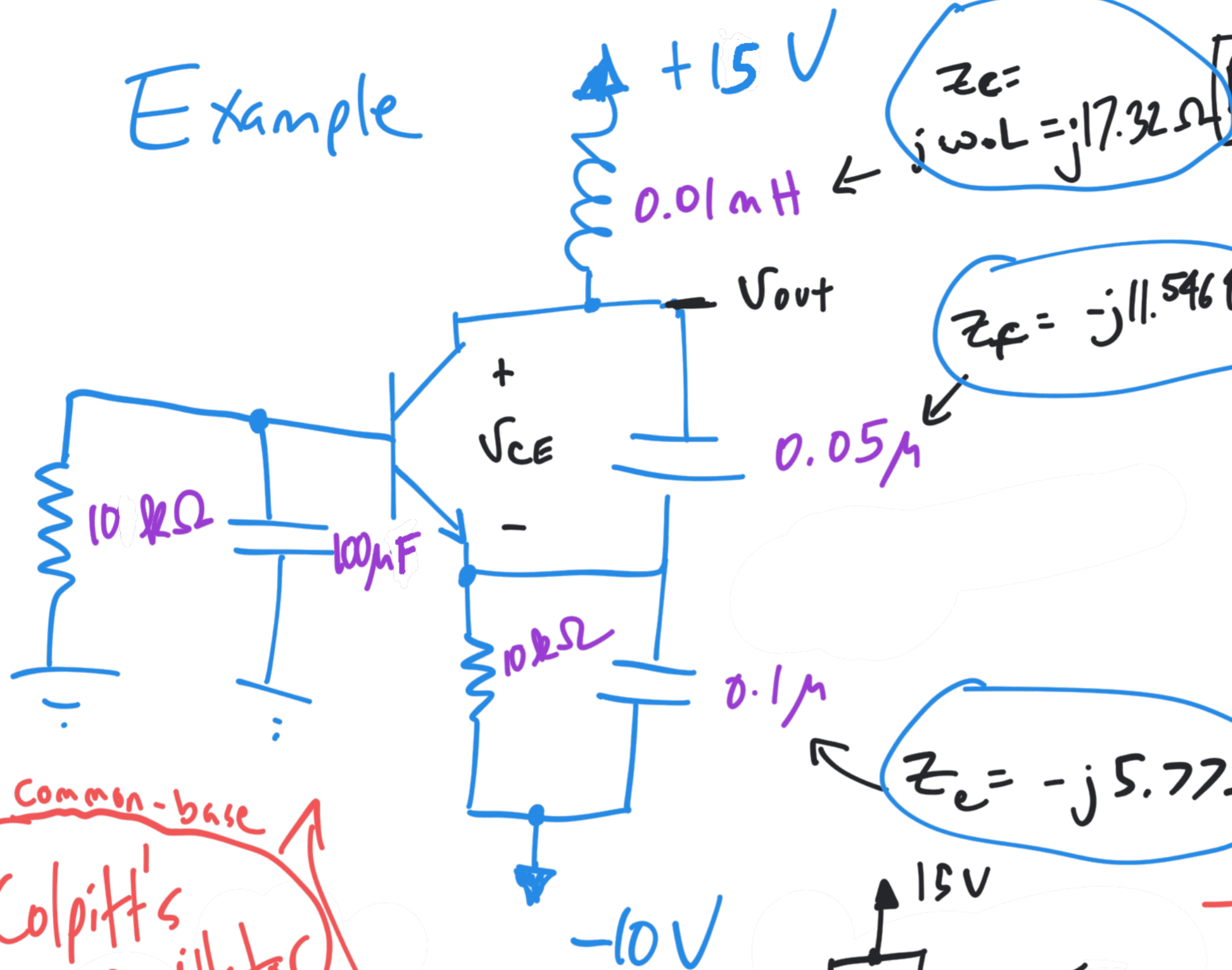

$z_c = j\omega L = j17.32\Omega$

Bias current:
 $I_E = \frac{10 - 0.7}{10k\Omega} = 0.93mA$

$z_f = -j11.546f\Omega$


$f_0 \approx 275kHz$

Check:
 $\frac{C_e}{C_e + C_f} = 0.667 \geq 1 - \alpha \approx 0.1$

$z_e = -j5.77\Omega$

Common-base
 Colpitt's oscillator

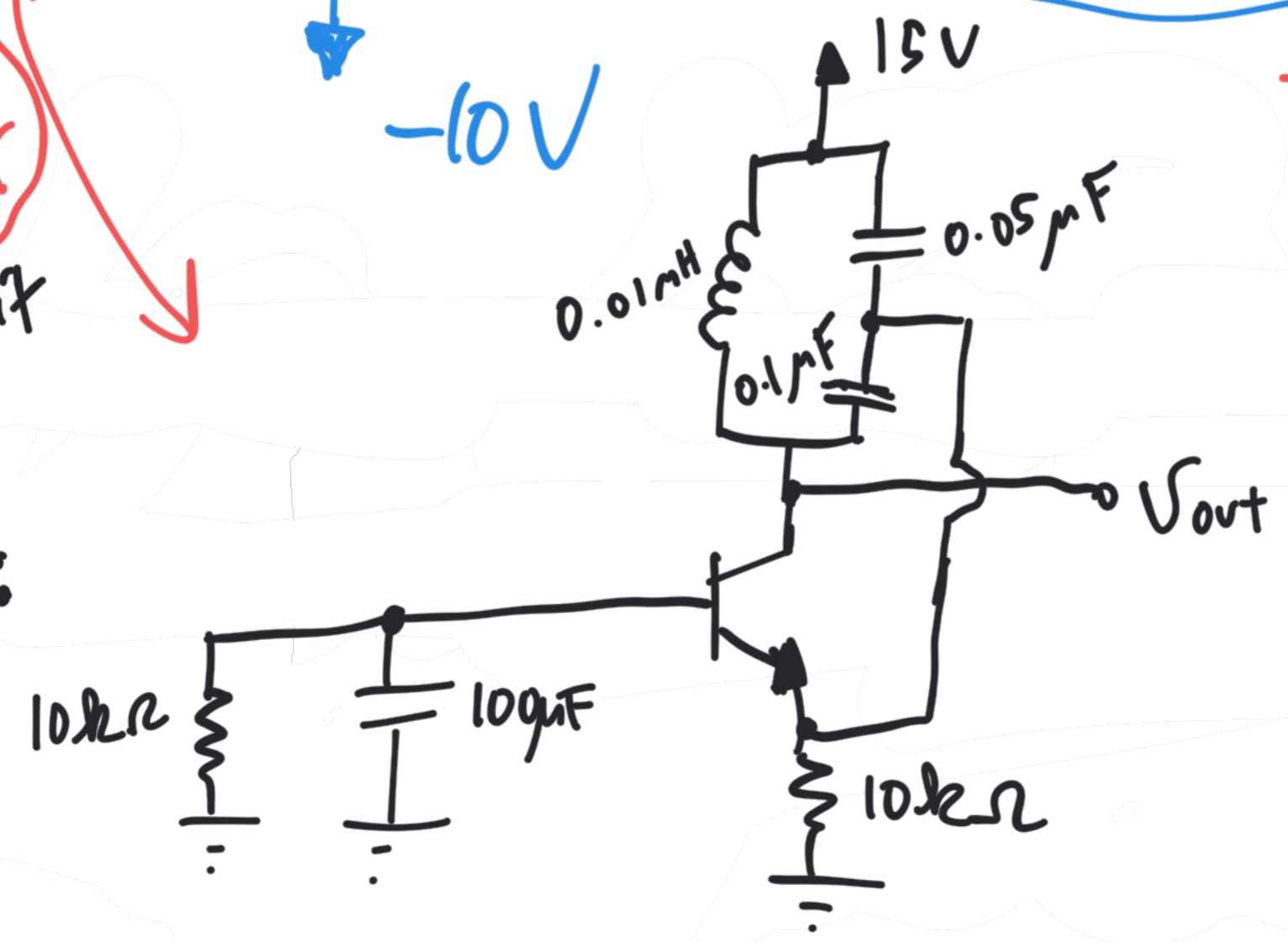
Another circuit w/
 small signal equivalent:



This was checked w/ LTspice.


Stability analysis BJT transistor amplifiers

① original

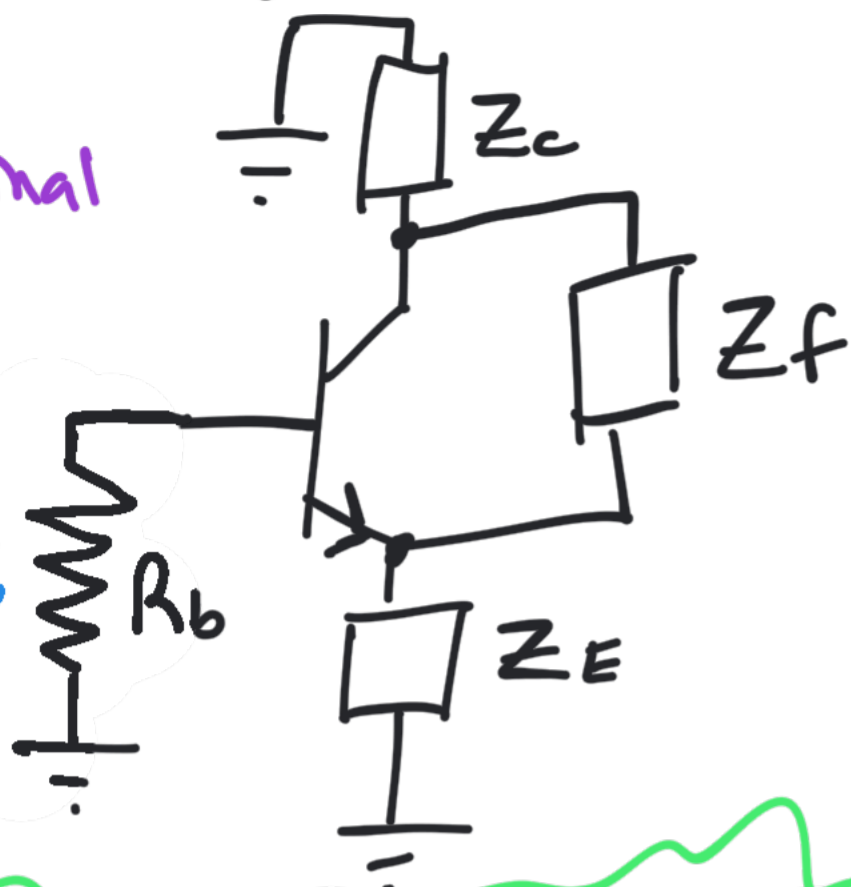

Small signal model


② small signal

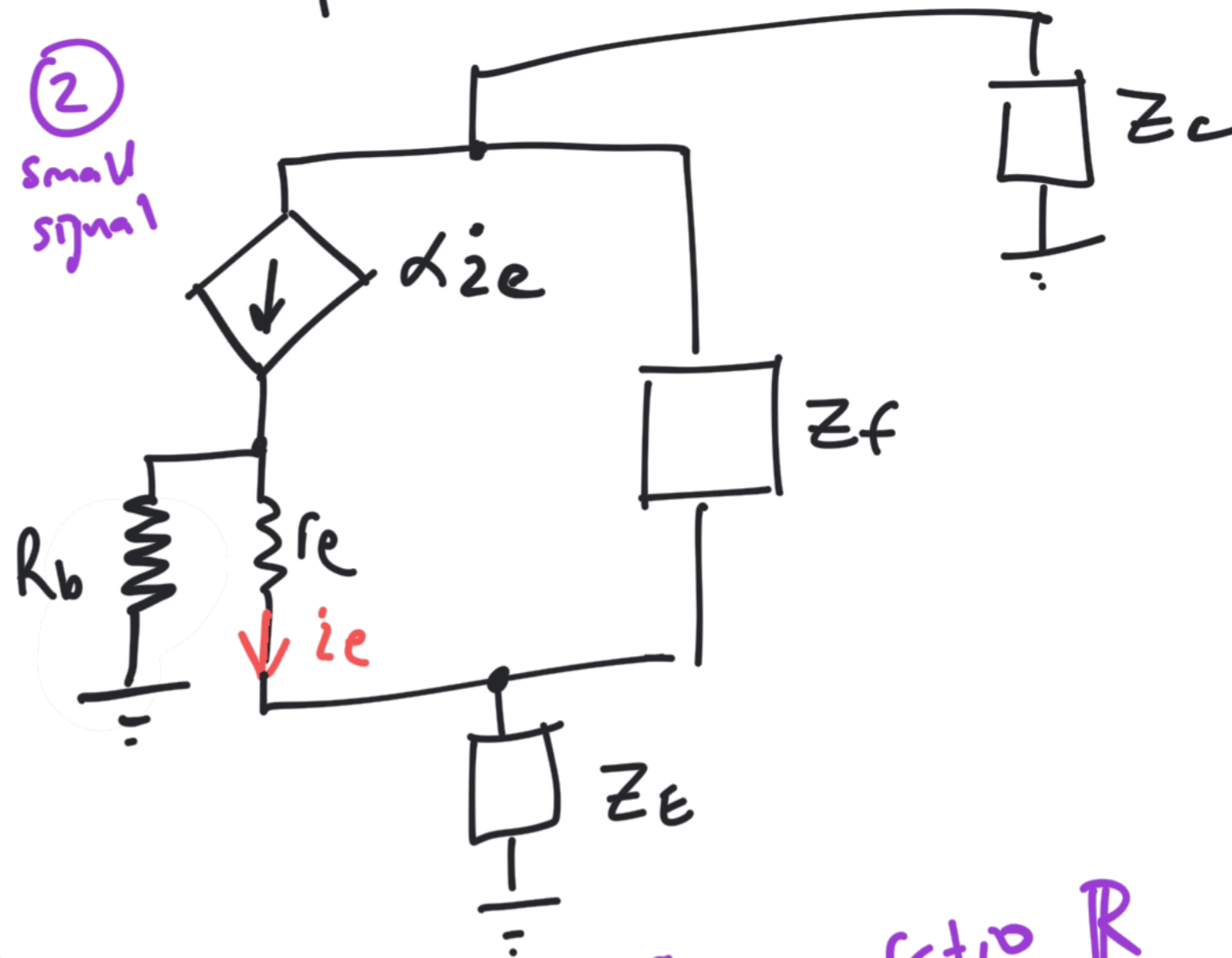


What does Rb do?

This is the new thing here!

③ re-draw small signal

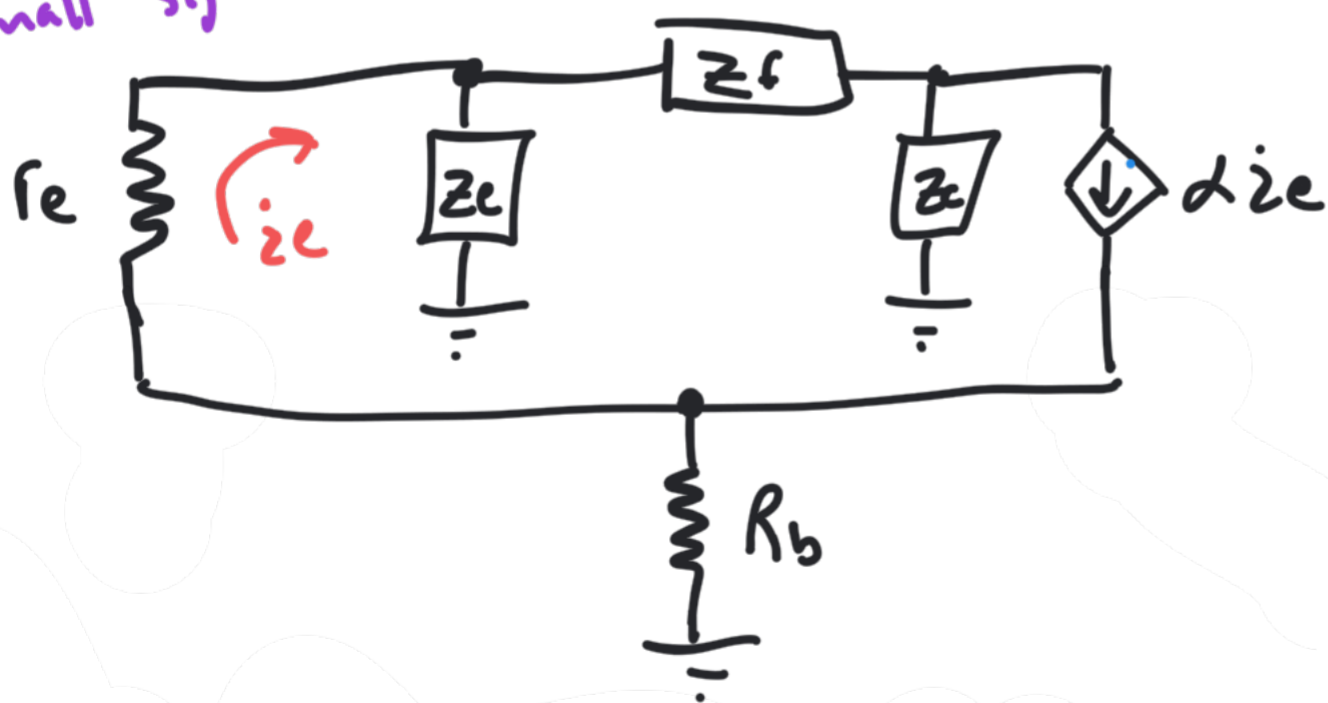

④ Find Return ratio R

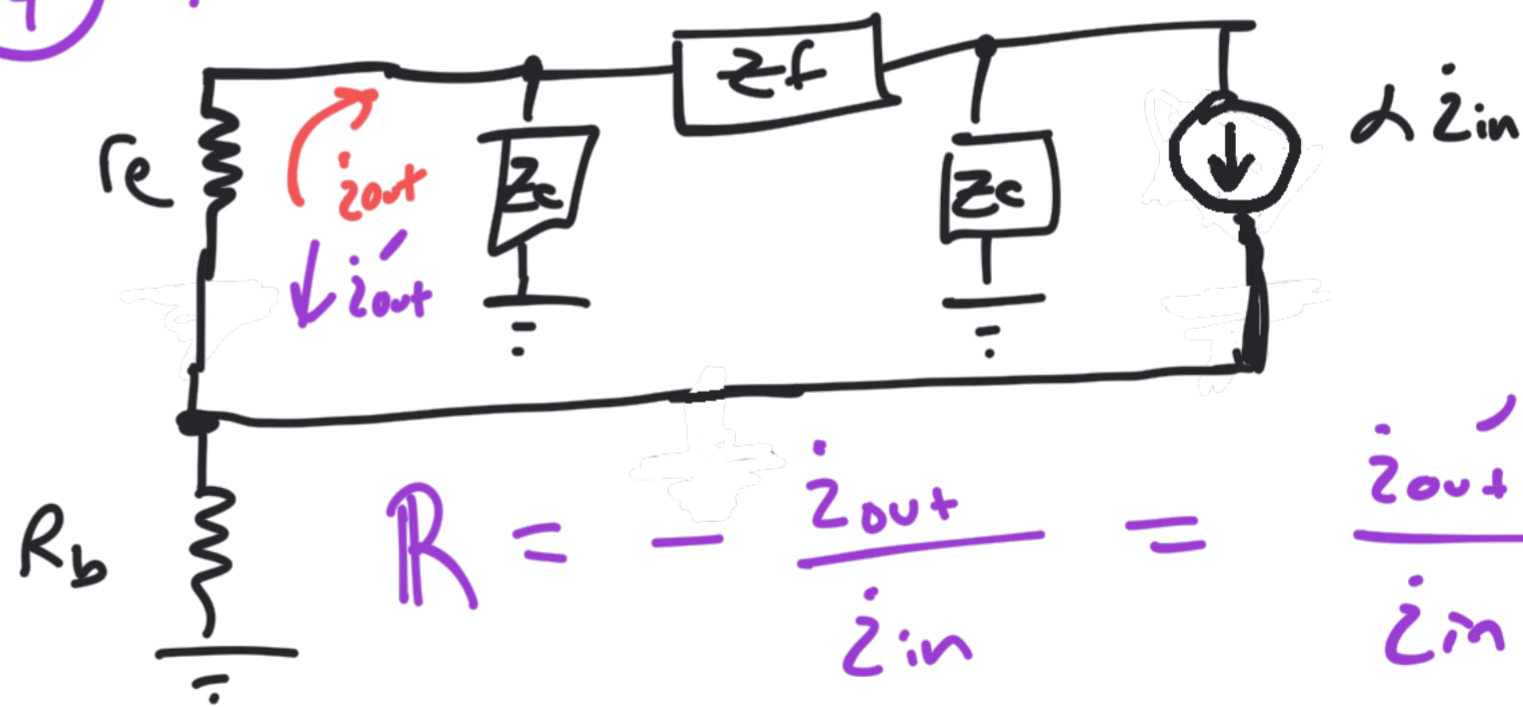



$$R = - \frac{i_{out}}{i_{in}} = \frac{i'_{out}}{i_{in}}$$

circuit unstable

if $|R| > 1$


when $\angle R = 180^\circ + n \cdot 360^\circ$

Find Return ratio R

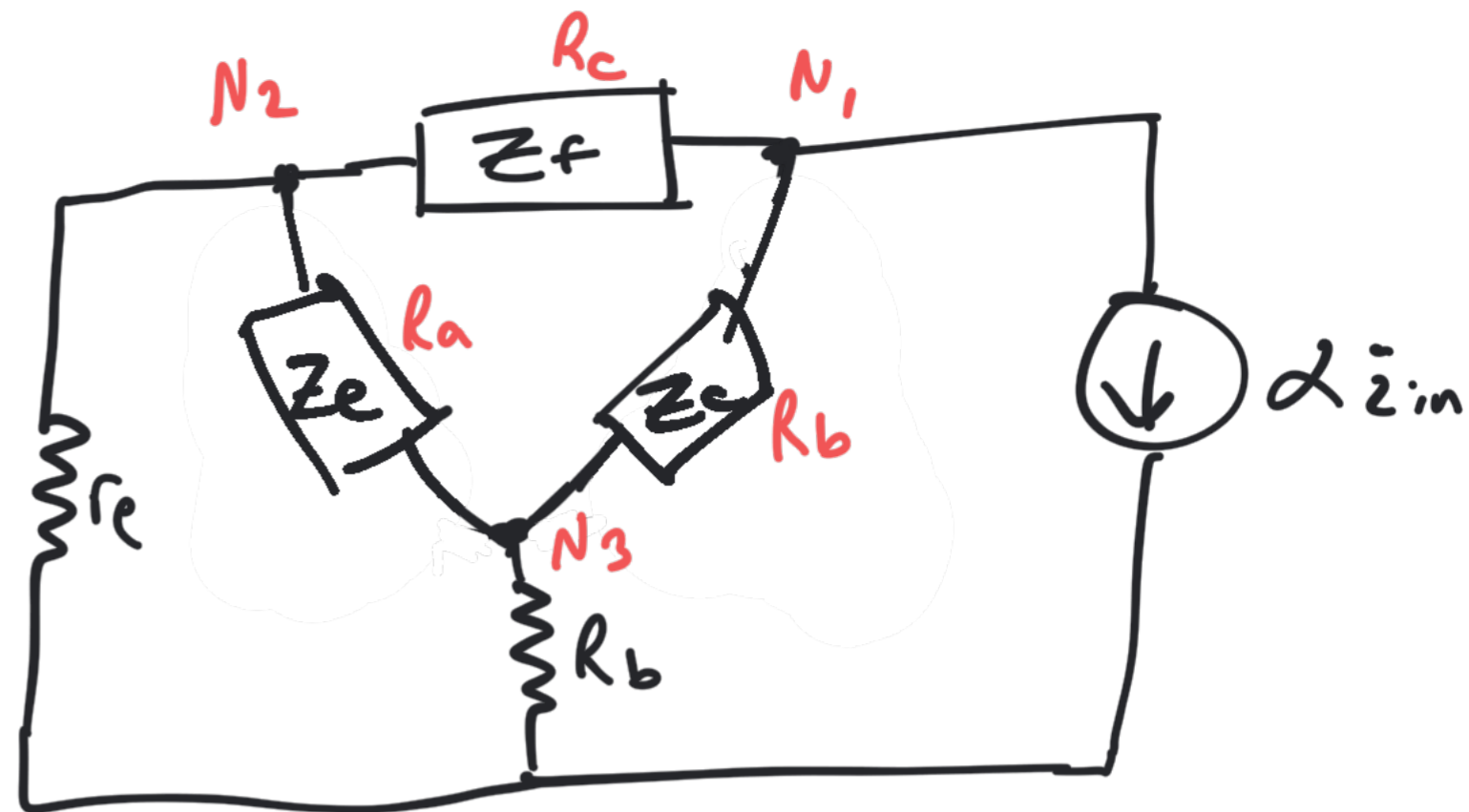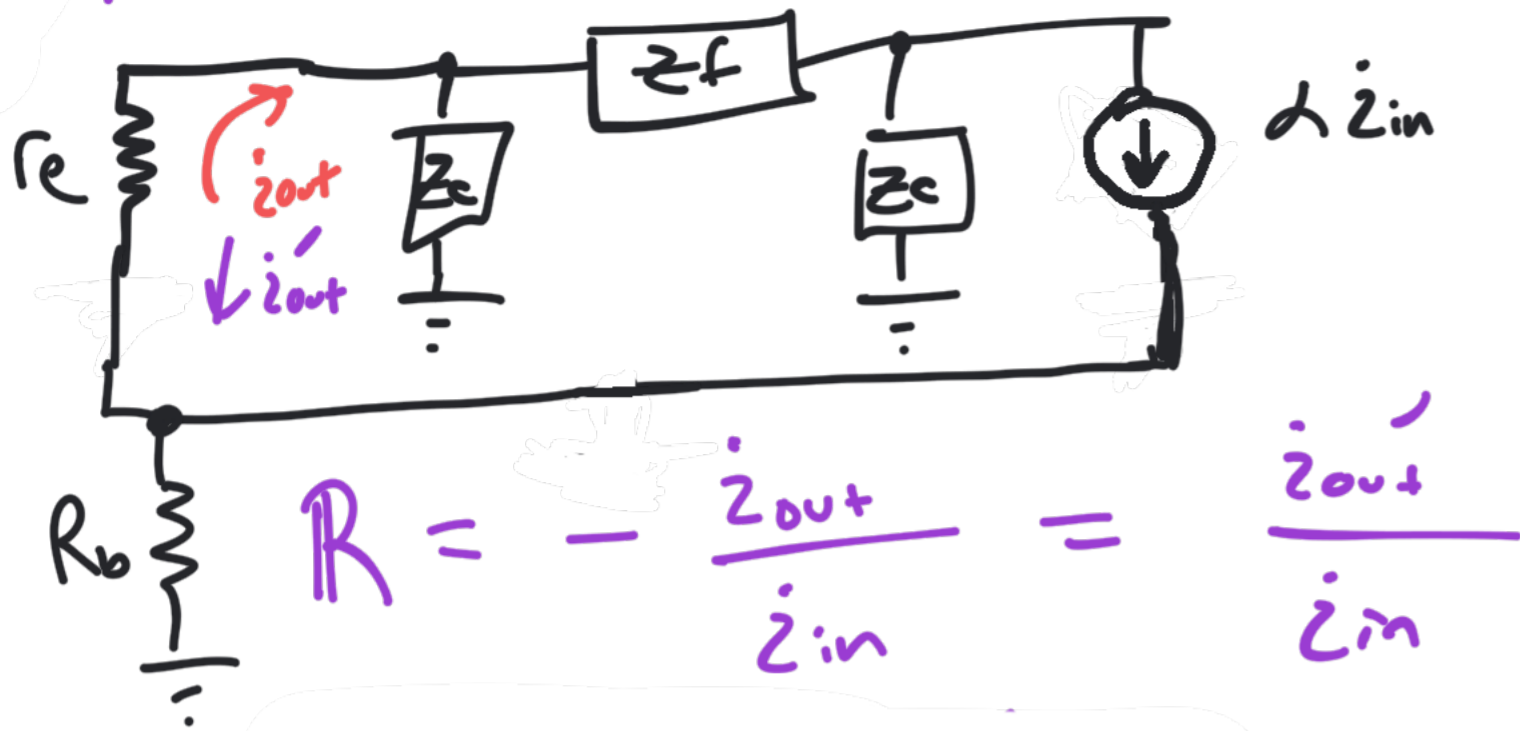


$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c} = \frac{Z_c Z_f}{Z_c + Z_f + Z_c}$$
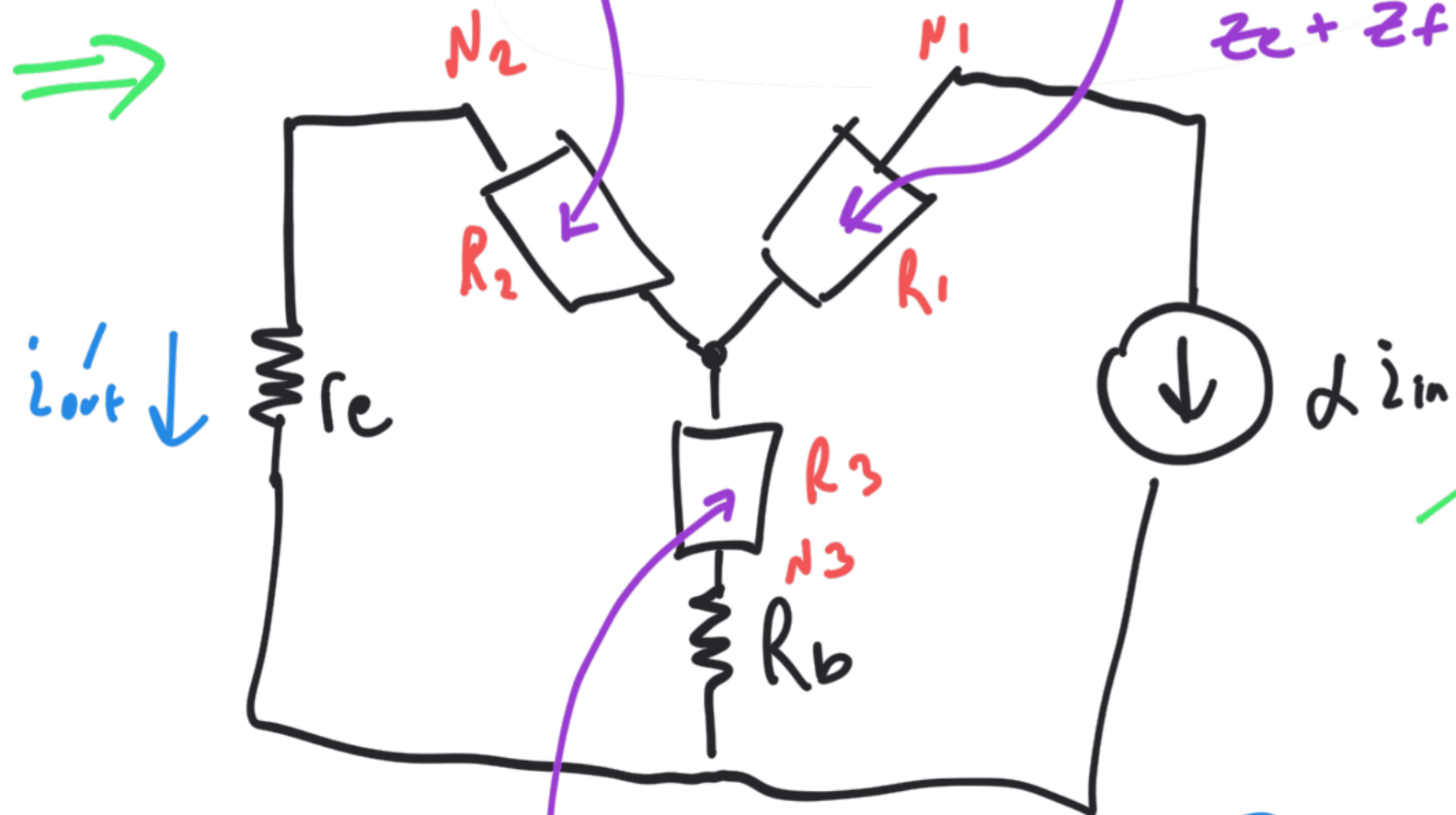
$$R_1 = \frac{Z_c Z_f}{Z_c + Z_f + Z_c}$$



$$R_3 = \frac{Z_c Z_c}{Z_c + Z_f + Z_c}$$

R

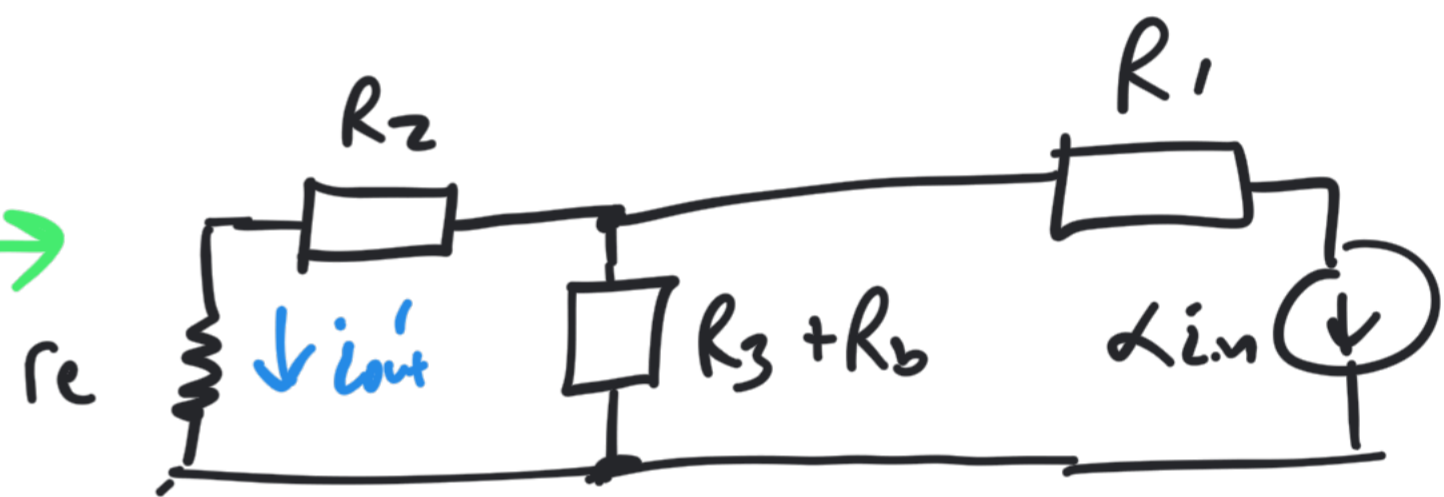

$$i_{out} = -\alpha i_{in} \left(\frac{R_3 + R_b}{R_2 + r_e + R_3 + R_b} \right)$$

$$\frac{i_{out}}{i_{in}} = -\alpha \left(\frac{R_3 + R_b}{R_2 + r_e + R_3 + R_b} \right)$$

$$R = -\alpha \left(\frac{Z_c Z_c + R_b (Z_c + Z_f + Z_c)}{Z_c Z_f + Z_c Z_c + (R_b + r_e) (Z_c + Z_f + Z_c)} \right)$$

$$R = -\alpha \left(\frac{Z_e Z_c + R_b (Z_e + Z_f + Z_c)}{Z_e Z_f + Z_e Z_c + (R_b + r_e)(Z_e + Z_f + Z_c)} \right)$$

Let $Z_e \rightarrow 0$ (short) : $R = \frac{-\alpha R_b}{R_b + r_e}$ (not going to oscillate) even if $R_b \rightarrow Z_b$

↑
Complex impedance

Let $Z_f \rightarrow \infty$ (open) : $R = \frac{-\alpha R_b}{Z_e + R_b + r_e}$ (Does not seem like this can oscillate... even if $R_b \rightarrow Z_b$)



↑
Complex impedance

Let $Z_c \rightarrow 0$ (short) : $R = \frac{-\alpha R_b (Z_e + Z_f)}{Z_e Z_f + (R_b + r_e)(Z_e + Z_f)}$

↖ No obvious way to oscillate either...


So, all in all it doesn't look like R_b does much to stability!

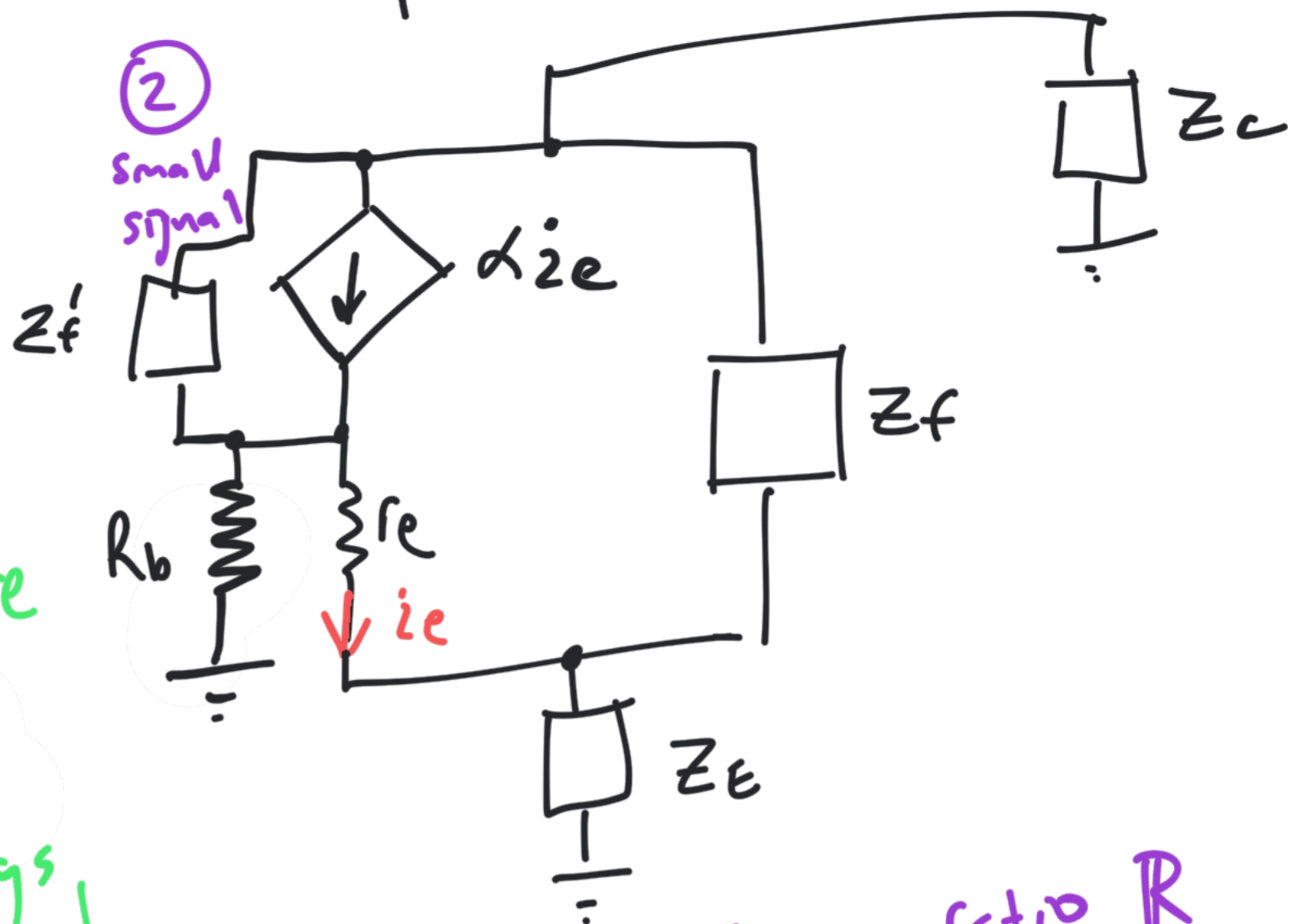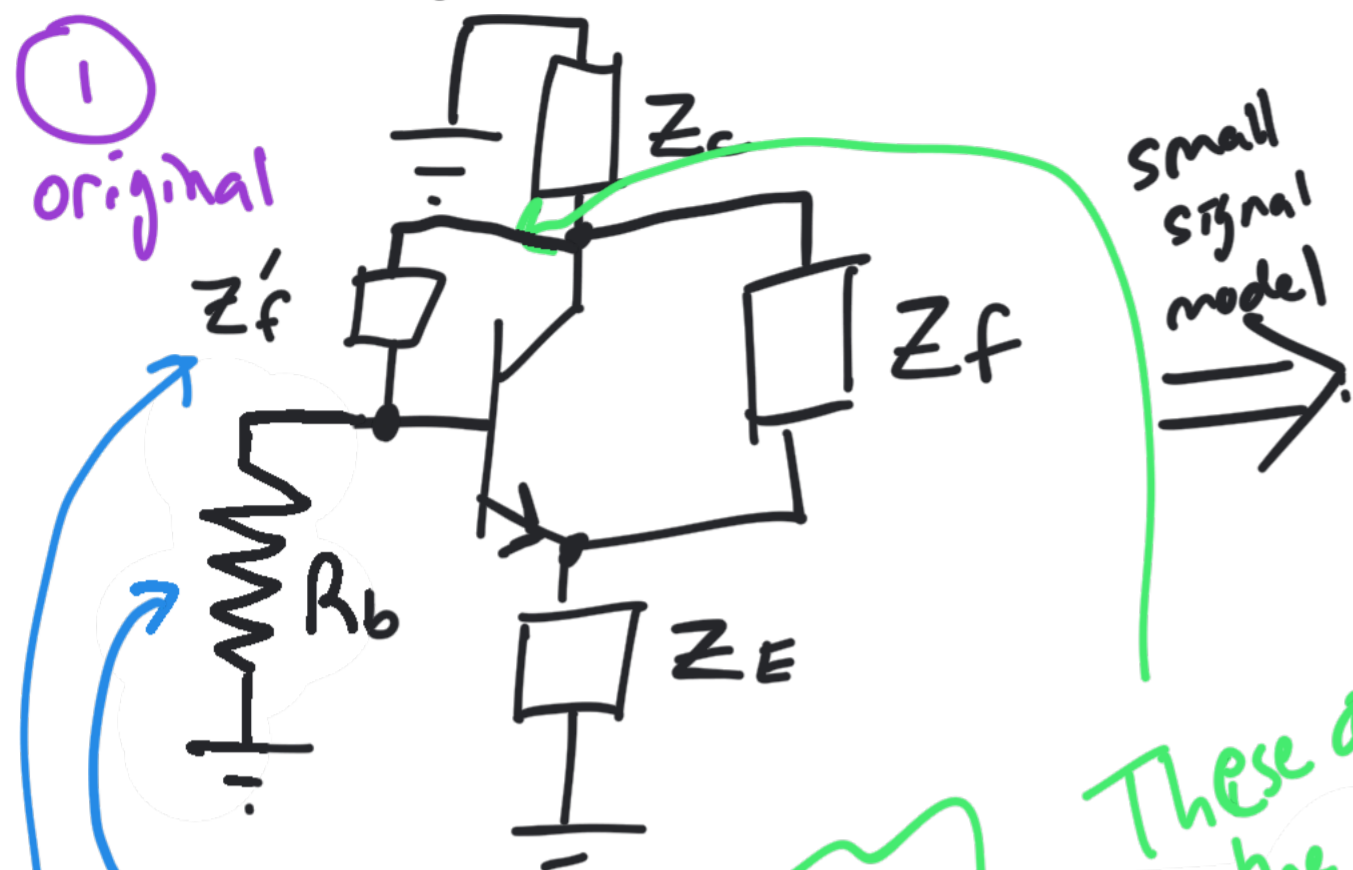Stability analysis BJT transistor amplifiers




What does R_b do?
 What does Z_f' do?
 These are the new things here!

③ re-draw small signal

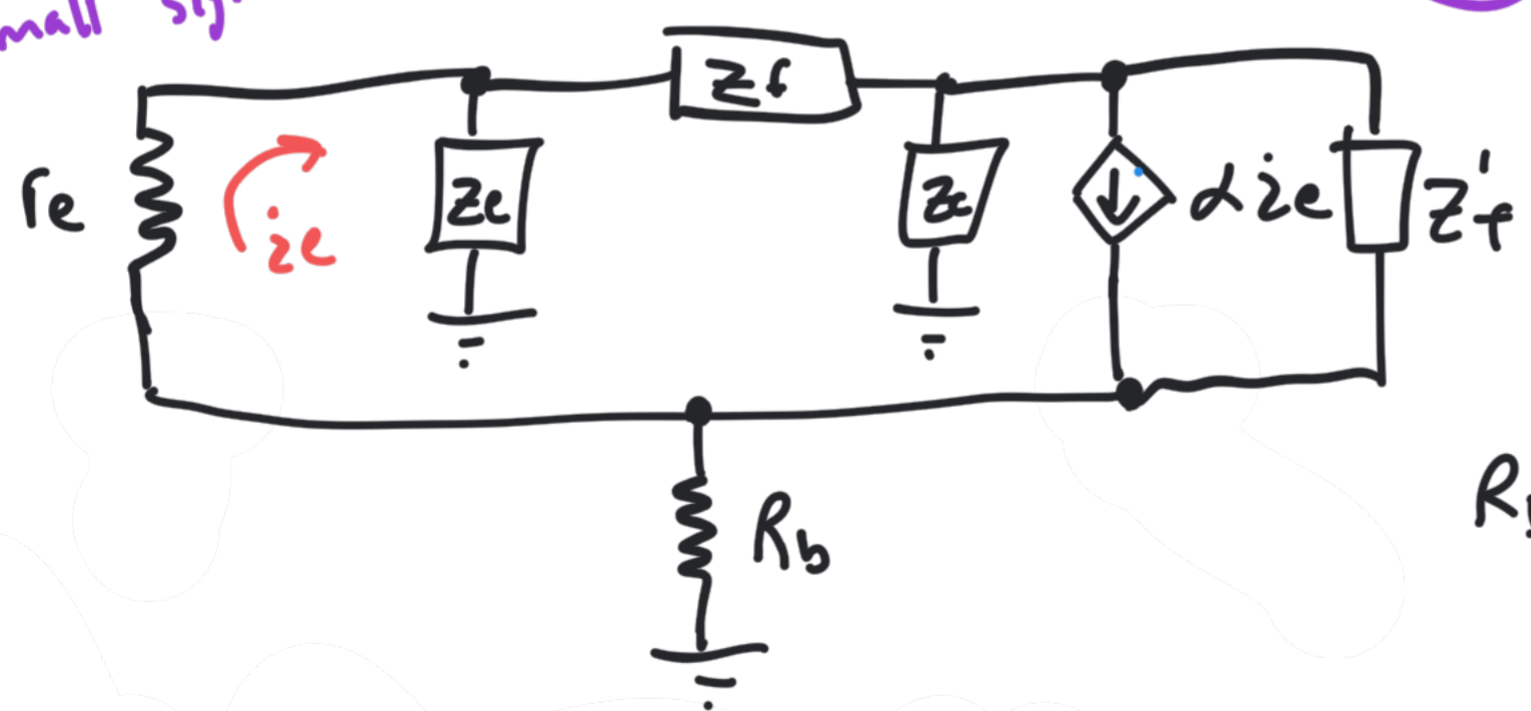



④ Find Return ratio R

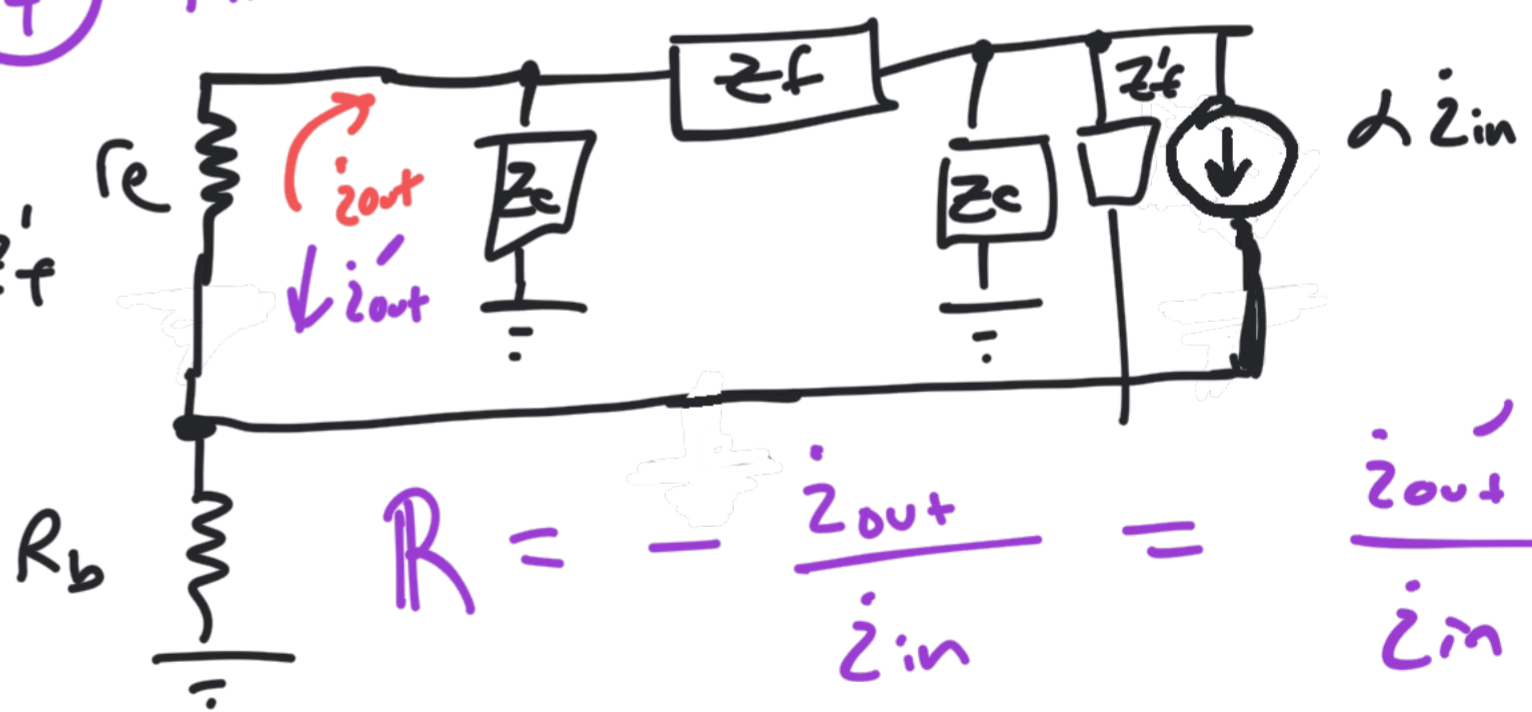

$$R = - \frac{i'_{out}}{i'_{in}} = \frac{i'_{out}}{i'_{in}}$$


circuit unstable if $|R| > 1$
 when $\angle R = 180^\circ + n \cdot 360^\circ$

Find Return ratio R



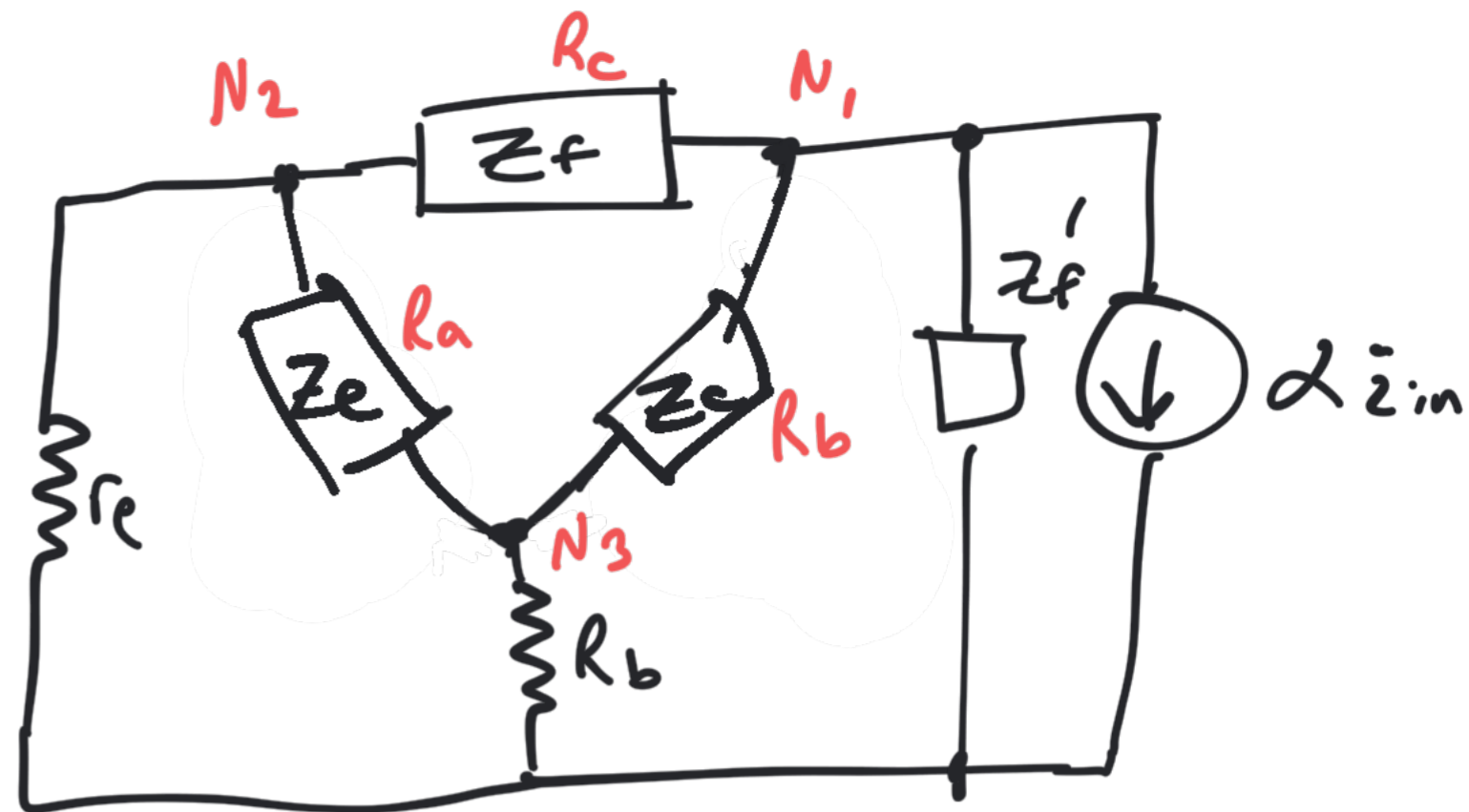
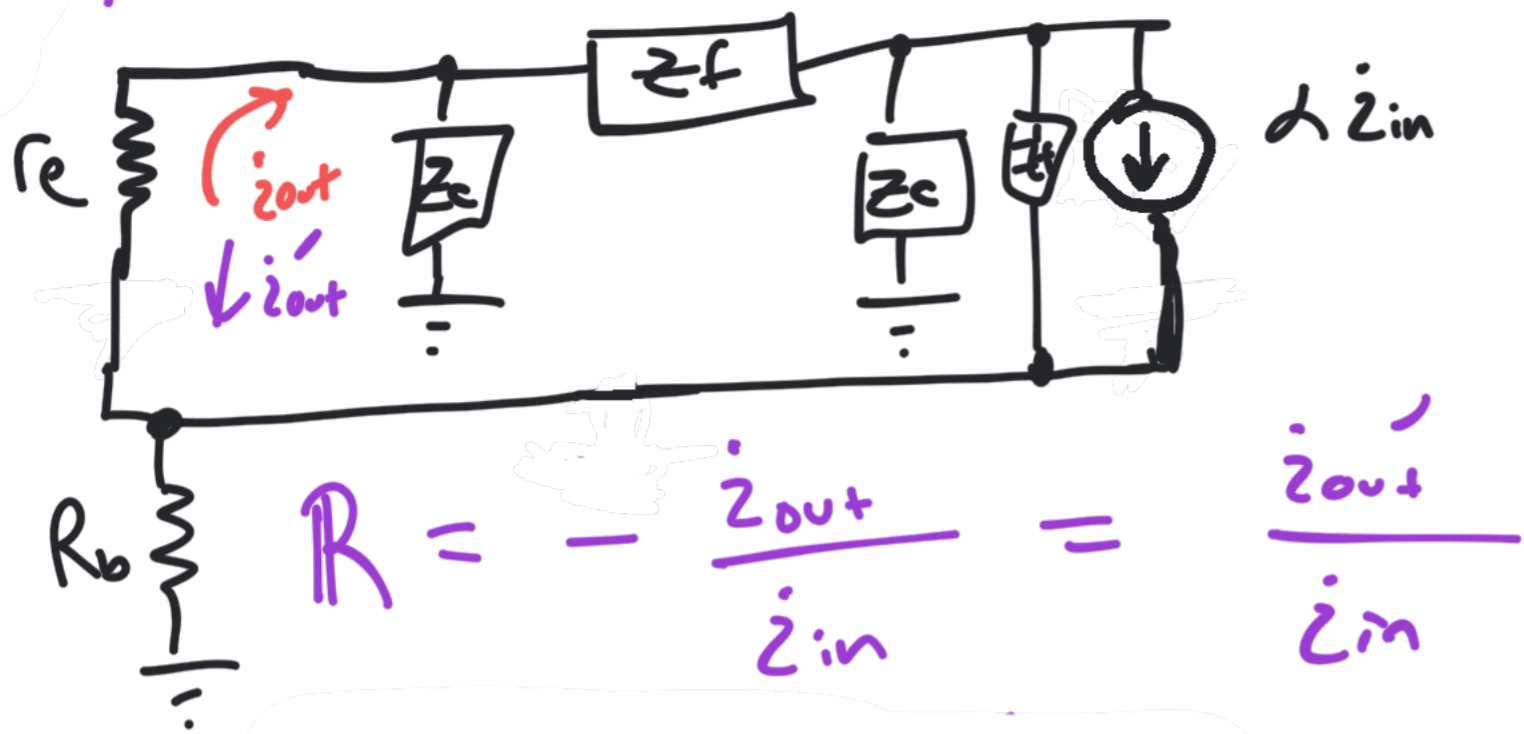



$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c} = \frac{Z_e Z_f}{Z_e + Z_f + Z_c}$$
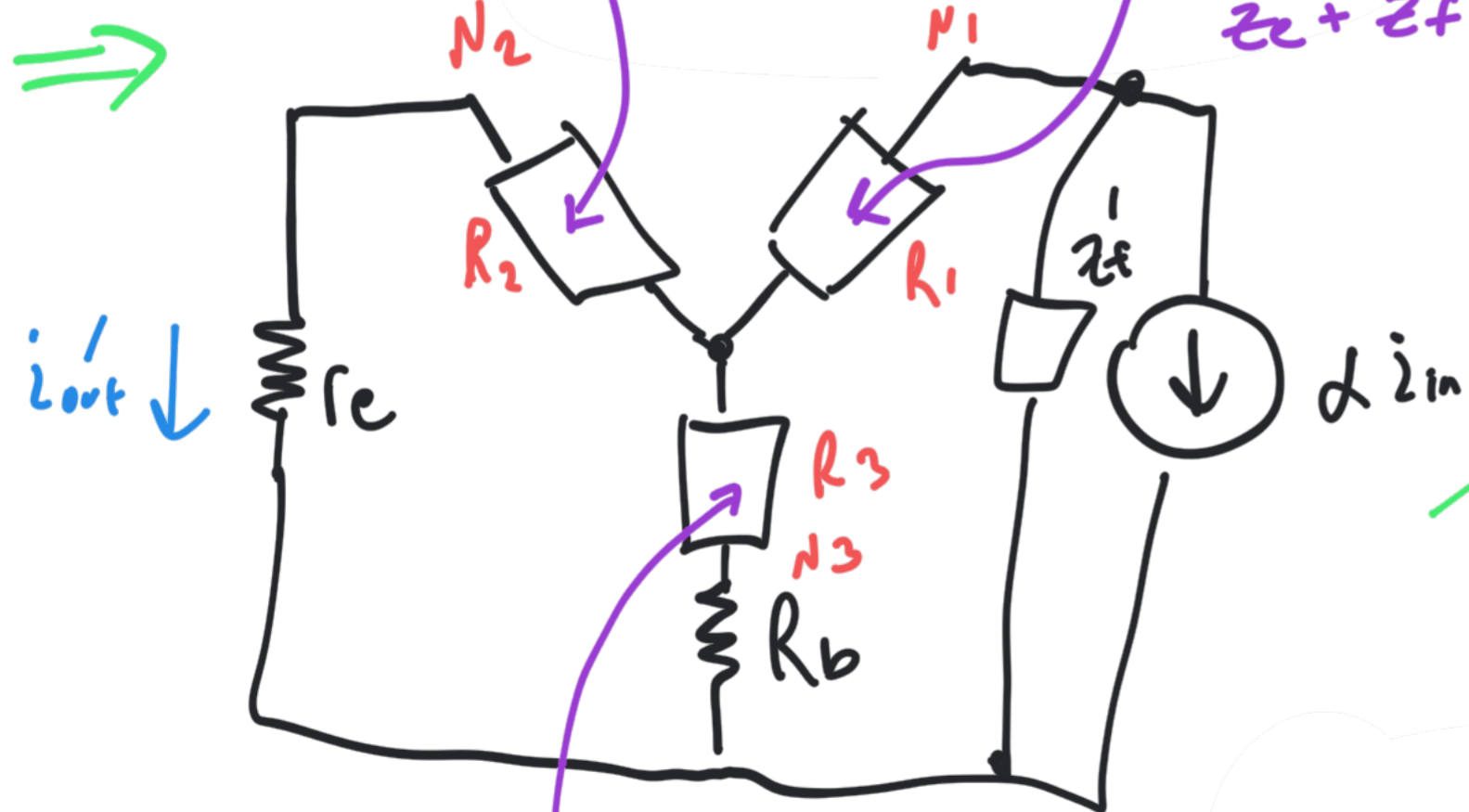
$$R_1 = \frac{Z_c Z_f}{Z_e + Z_f + Z_c}$$


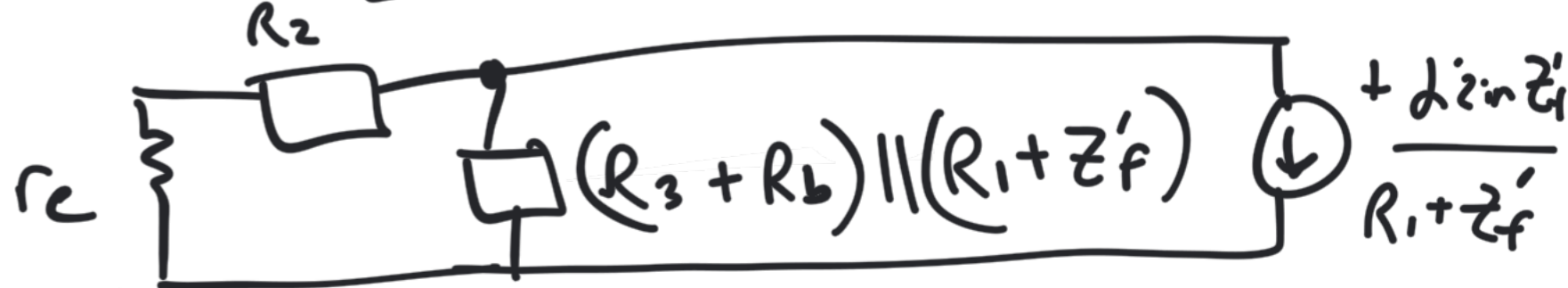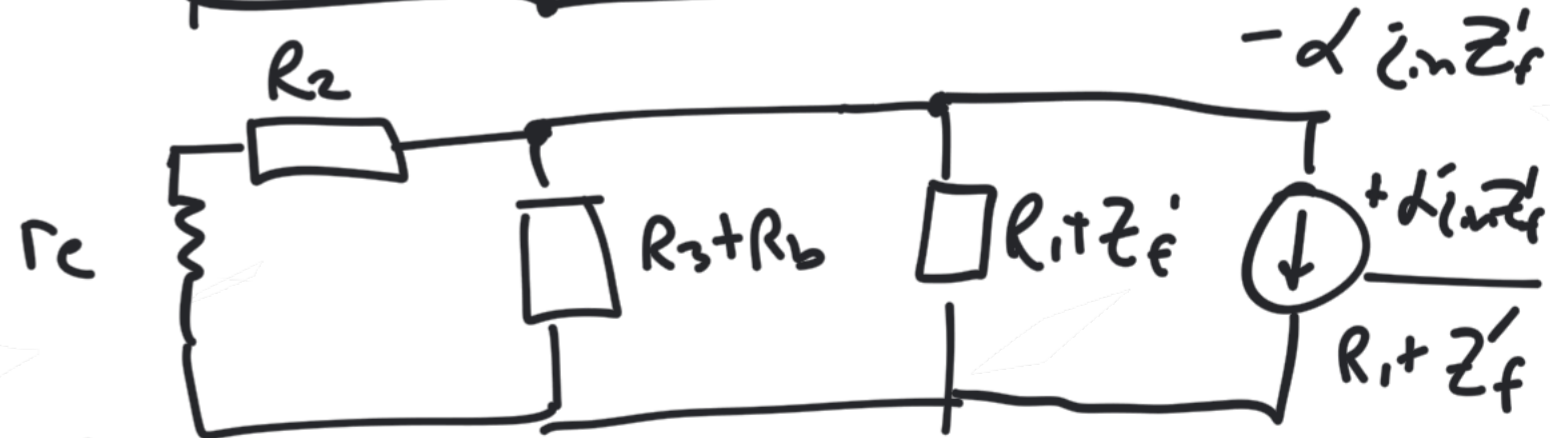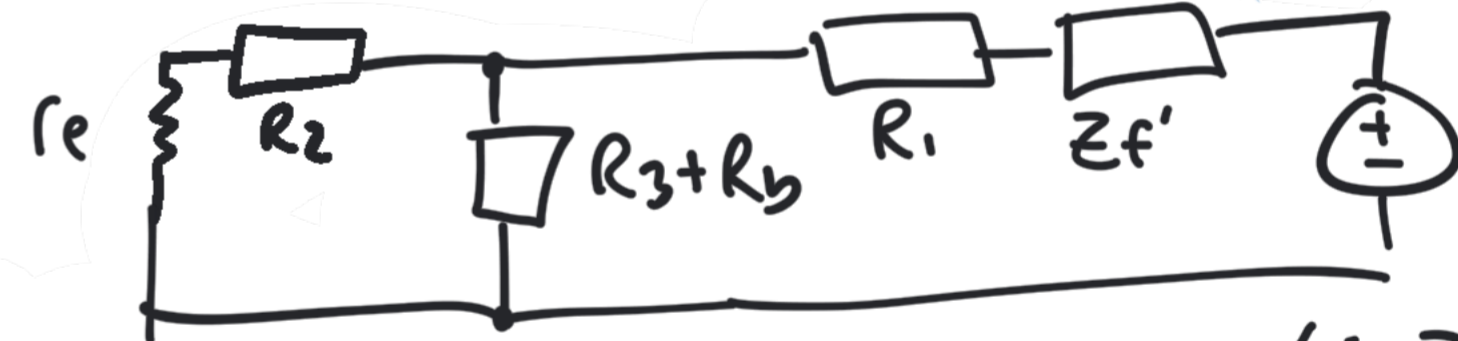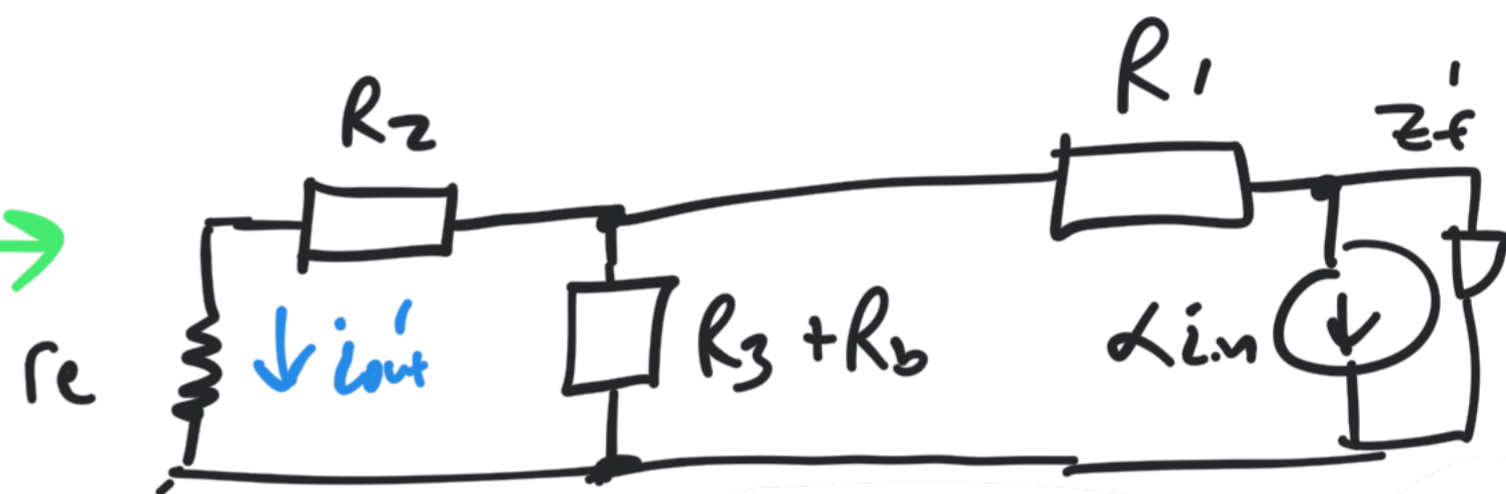
$$R_3 = \frac{Z_e Z_c}{Z_e + Z_f + Z_c}$$



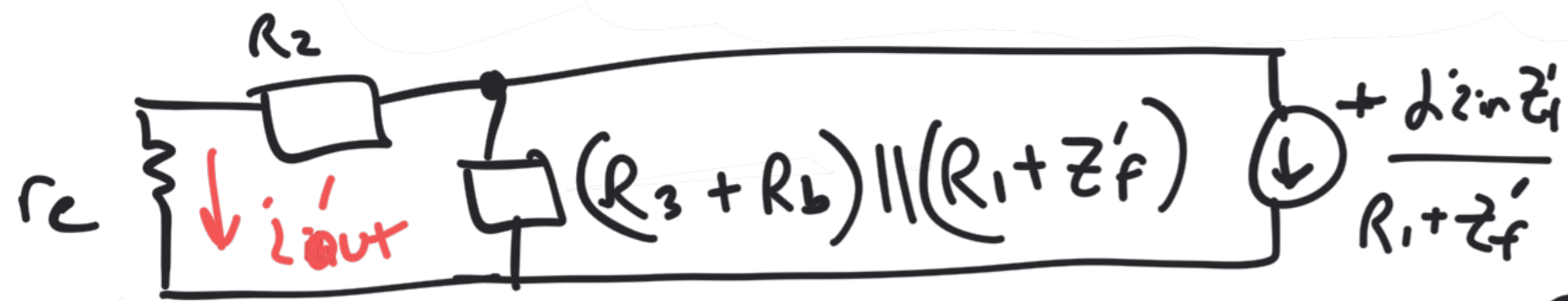

$$R = \frac{\dot{z}_{out}'}{i_{in}} = -\alpha \frac{z_f'}{R_1 + z_f'} \frac{(R_3 + R_b) \parallel (R_1 + z_f')}{r_e + R_2 + (R_3 + R_b) \parallel (R_1 + z_f')}$$

$$R = = -\alpha \frac{z_f'}{\cancel{R_1 + z_f'}} \frac{(R_3 + R_b) \cancel{(R_1 + z_f')}}{(r_e + R_2)(R_3 + R_b + R_1 + z_f') + (R_3 + R_b)(R_1 + z_f')}$$


$$\Sigma = z_e + z_c + z_f = -\alpha z_f' \frac{(R_3 + R_b)}{(R_3 + R_b)(r_e + R_2 + R_1 + z_f') + (r_e + R_2)(R_1 + z_f')}$$

$$= -\alpha z_f' \frac{(z_e z_c) \Sigma + R_b \Sigma^2}{(z_e z_c \Sigma + R_b \Sigma^2) \left(r_e + \frac{z_e z_f + z_c z_f}{\Sigma} + z_f' \right) + (r_e \Sigma^2 + R_b \Sigma) \left(\frac{z_c z_f}{\Sigma} + z_f' \right)}$$

Not sure where to go from here

Negative feedback comparison

Negative feedback amplifier

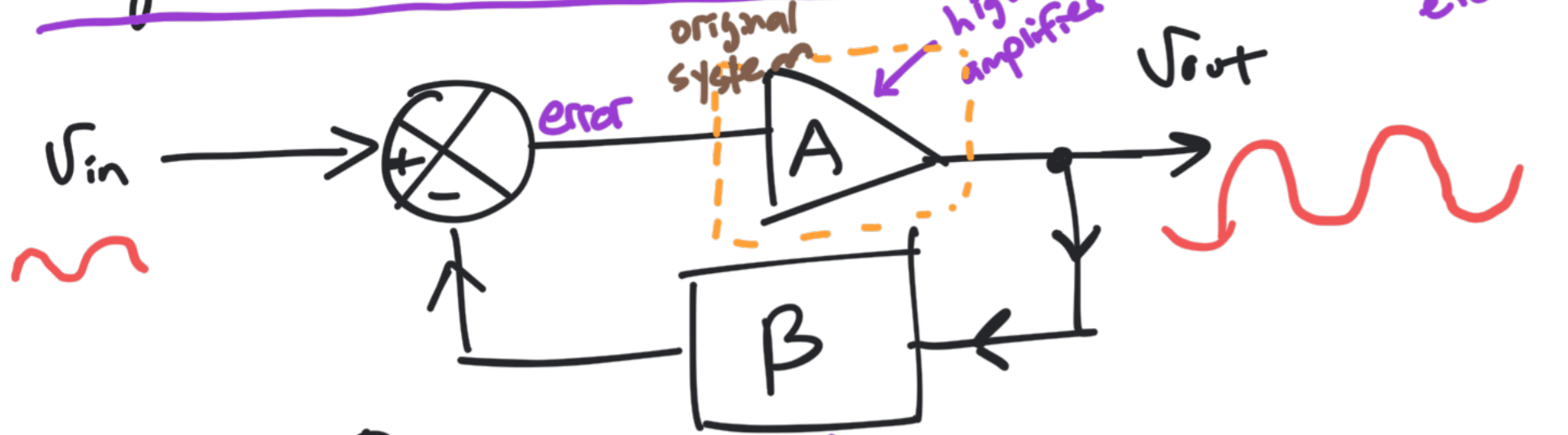

bottom line: Trade amplifier gain for linearity, less sensitivity to temp, etc. better freq response (flatter over Bd of amplified impedance, improving etc.)

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta}$$

loop gain

$$\approx \frac{1}{\beta} \text{ for } A\beta \gg 1$$

if error $\rightarrow 0$

$$V_{in} - \beta V_{out} = 0$$

$$\rightarrow V_{out} = \frac{1}{\beta} V_{in}$$


(stable gain!) independent of A!

advantages: noise/disturbance reduction of neg. feedback output follows input

advantages: linearity, const. freq response of neg. feedback (input/output impedance improvements... not shown)

bottom line: make Gc big so error is small and Vout tracks Vref

Negative feedback control system

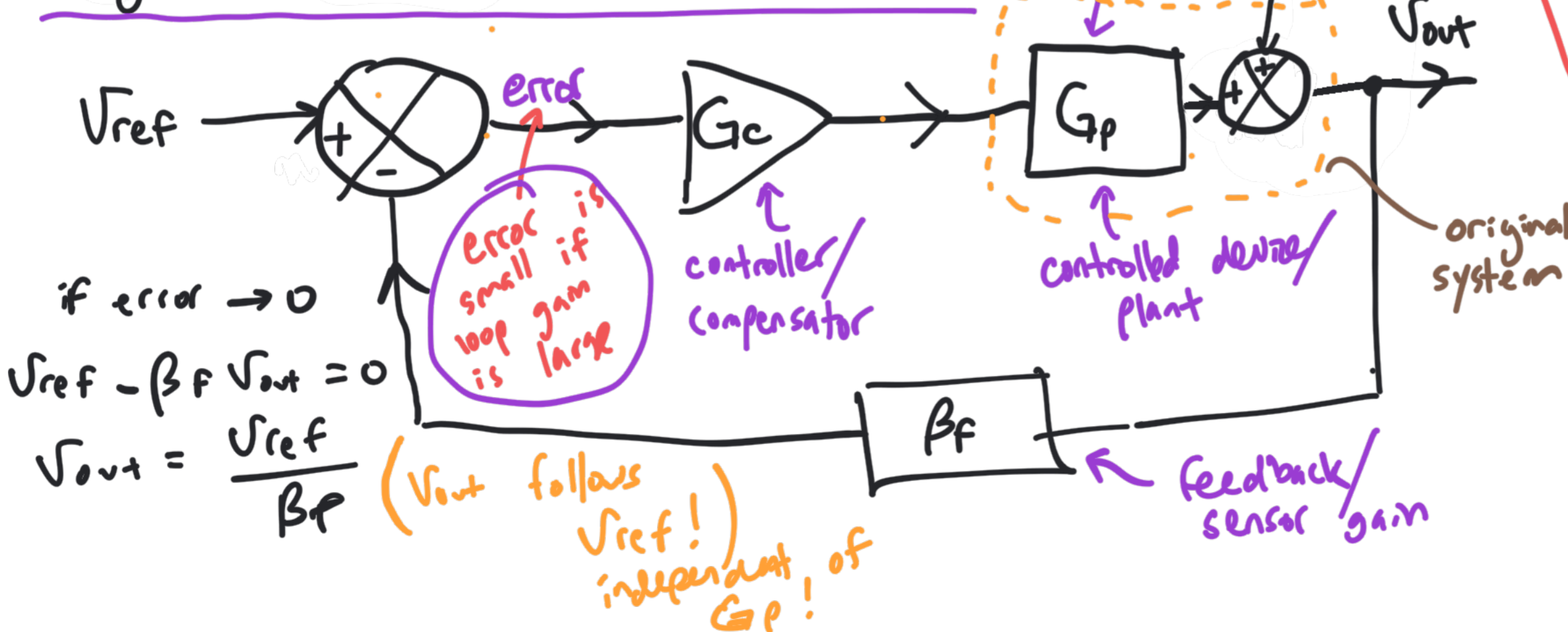

if error $\rightarrow 0$

$$V_{ref} - \beta_f V_{out} = 0$$

$$V_{out} = \frac{V_{ref}}{\beta_f}$$

(Vout follows Vref!) independent of Gp!

error is small if loop gain is large

$$\frac{V_{out}}{V_{ref}} = \frac{G_c G_p}{1 + G_c G_p \beta_f}$$

loop gain

$$\approx \frac{1}{\beta_f} \text{ for } G_c G_p \beta_f \gg 1$$

$$\frac{V_{out}}{V_{noise}} = \frac{1}{1 + G_c G_p \beta_f}$$

$$\approx 0 \text{ for } G_c G_p \beta_f \gg 1$$