

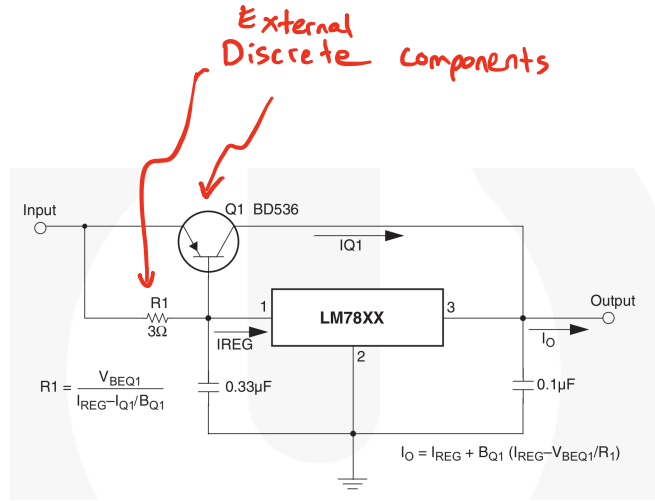


Fixed voltage regulator

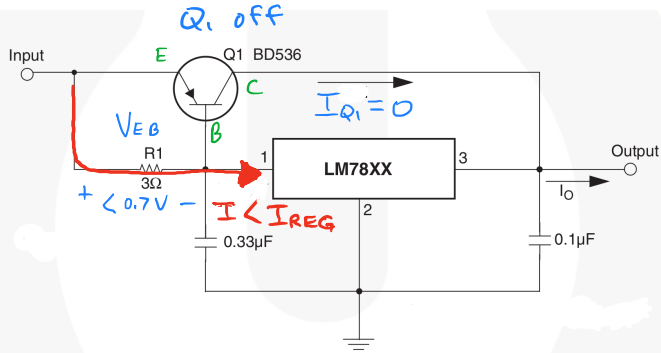


High-current fixed voltage regulator

Recall: For PNP transistor

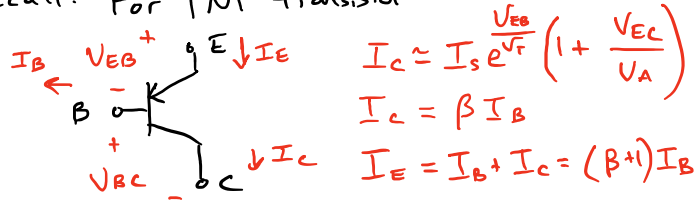

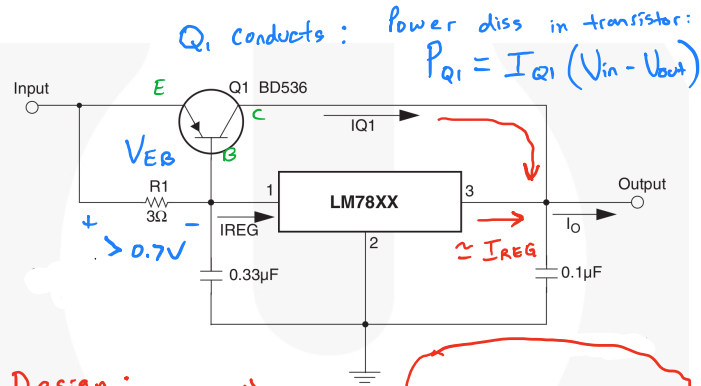I_{REG} = highest power that regulator can handle internally.



Design:

$\frac{V_{EB}}{R_1} = I_B + I_{REG} \rightarrow$

Choose:


$$R_1 = \frac{V_{EB}}{I_{REG}} \approx \frac{0.7V}{I_{REG}}$$

Notes



Q. Why didn't designers simply integrate Q_1 into IC itself?

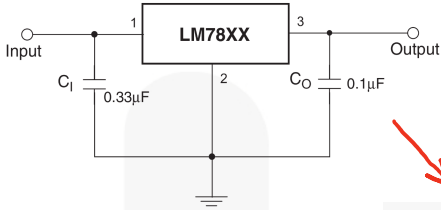A. Expense/bulk: For high current Q_1 may need to be a power transistor w/ its own heat sink.


R_1 acts as current sensor... It is small and therefore has negligible effect on circuit performance... It generates voltage which is proportional to current. When current reached a specified value such that the generated voltage is 0.7V the transistor turns on, and bypasses the excess current.



Fixed voltage regulator

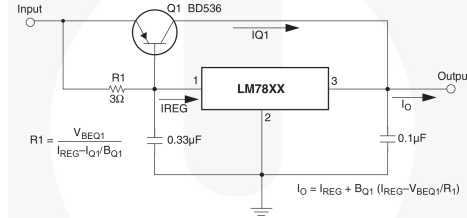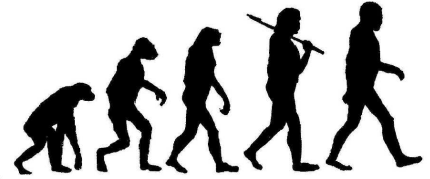


High output current

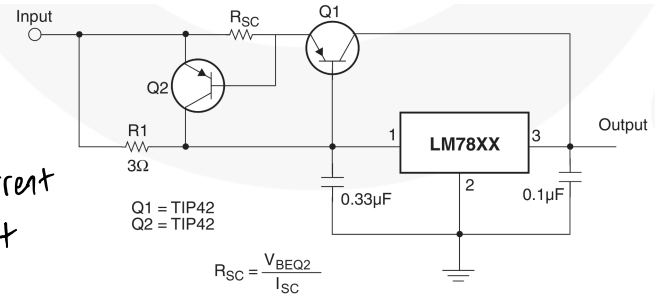


High output current
+ short circuit
protection


March 5, 2016

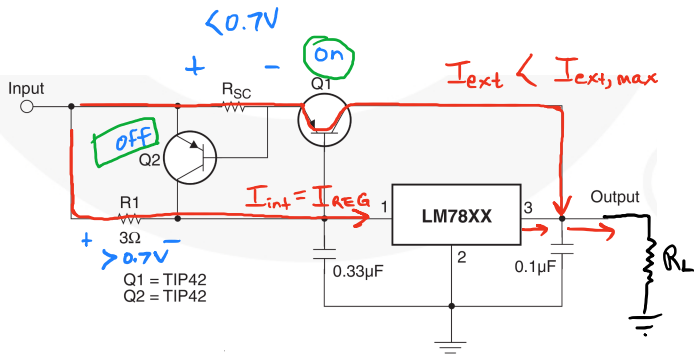
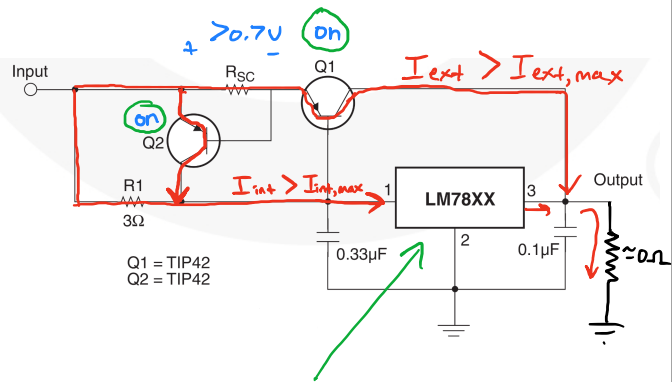
$$R_{sc} \approx \frac{0.7}{I_{ext,max}}$$




Internal regulator current is excessive, forcing the regulator into thermal shutdown.

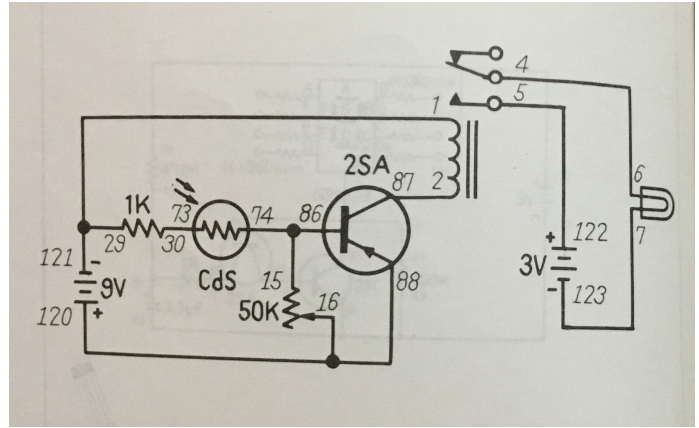


Experiment 78: Light controlled switch with CDS cell

March 6, 2016

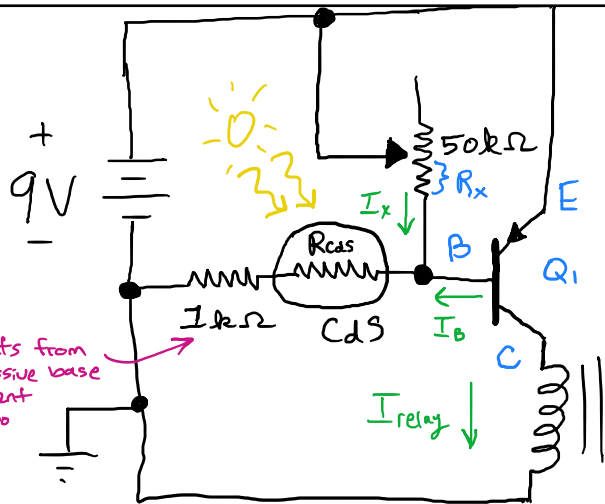

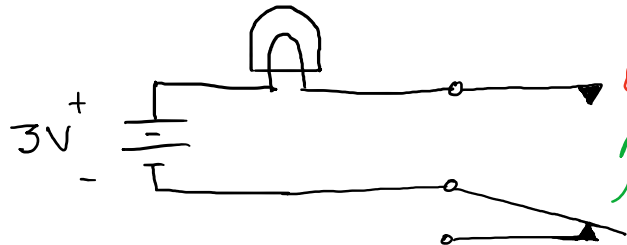Protects from excessive base current if too much light



$C_{ds} \approx \begin{cases} \infty \Omega & \leftarrow \text{Total Darkness} \\ \text{Somewhere in middle} & \leftarrow \text{Room lighting} \\ 100 - 200 \Omega & \leftarrow \text{Sun} \end{cases}$

Relay: $\begin{cases} |I_{\text{relay}}| < 40\text{mA} & \text{off} \\ |I_{\text{relay}}| \geq 40\text{mA} & \text{on} \end{cases}$

Circuit analysis


$Q_1 \text{ OFF: } I_x R_x < 0.7\text{V} \rightarrow \frac{9}{1\text{k}\Omega + R_x + R_{\text{Cds, dark}}} < 0.7\text{V}$
 ($I_{\text{relay}} = 0$)

$Q_1 \text{ on: } \frac{9}{1\text{k}\Omega + R_x + R_{\text{Cds, light}}} = 0.7\text{V} \rightarrow V_B = 8.3\text{V}$

$I_B = \frac{0.7\text{V}}{R_x} + \frac{8.3\text{V}}{1\text{k}\Omega + R_{\text{Cds, light}}}$


switches shut when $|I_{\text{relay}}| \geq 40\text{mA}$

$I_{\text{relay}} = \beta I_B$

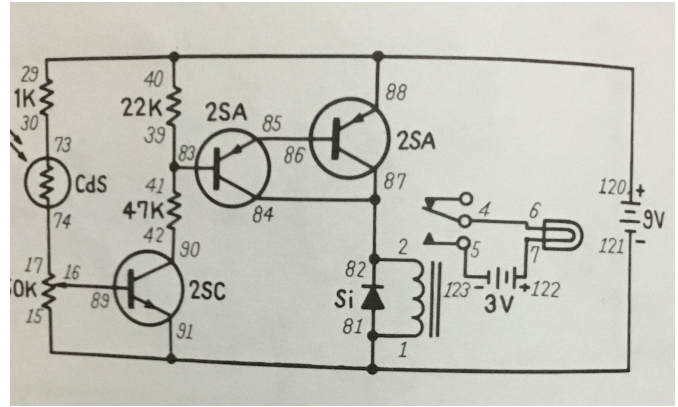

Experiment 80:
Sensitive Light
controlled switch with
CDS cell

March 7, 2016

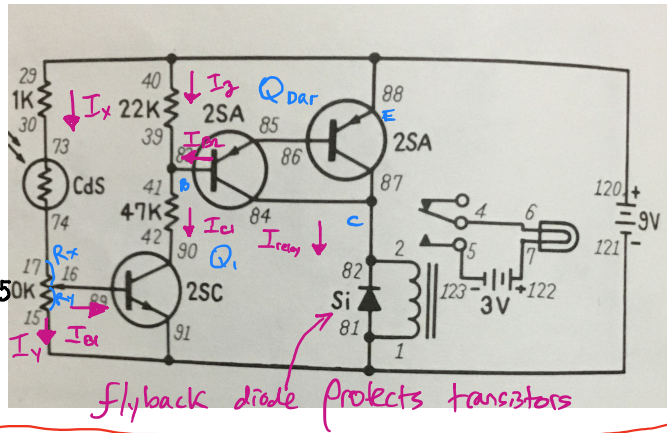

Circuit analysis

Assume Q_1 is off:

$$I_y R_y < 0.7V$$

$$I_y \approx I_x = \frac{9V}{1k\Omega + R_{cas} + 50k\Omega}$$

$\therefore Q_1$ is off when: R_y is adjustable!

$$R_{cas} > \frac{(9V)(R_y)}{0.7V} - 51k\Omega$$

R_{cas} is large in darkness!

When Q_1 is off, Q_{Dar} must also be off.

Assume Q_1 is on:

$$I_y R_y \approx 0.7V \rightarrow I_y = 0.7V / R_y$$

$$I_x = \frac{8.3V}{1k\Omega + R_{cas} + 50k\Omega - R_y}$$

$$I_{B1} = I_x - I_y \quad \leftarrow R_{cas} \downarrow \quad I_{B1} \uparrow$$

$$I_{C1} = \beta_1 I_{B1}$$

Assume Q_{Dar} is also on:

$$I_z = \frac{7.6V}{22k\Omega} \rightarrow I_{B2} = I_{C1} - I_z$$



$$I_{relay} = \beta_{dar} I_{B2} = \beta_{dar} (I_{C1} - I_z)$$

$\leftarrow \beta_{dar}$ is big!

Basic operation:




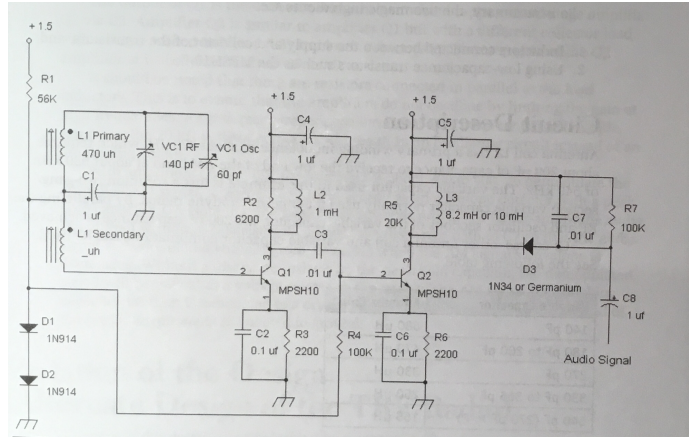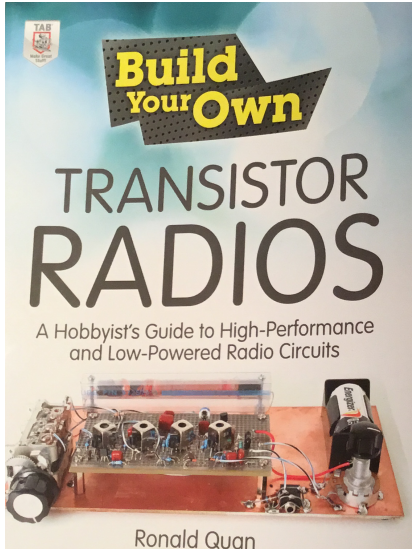$\uparrow R_{cas} \downarrow I_{B1} \uparrow I_{C1} \uparrow I_{relay} \uparrow$




Low powered tuned resonant frequency (TRF) AM radio receiver

Block diagram:

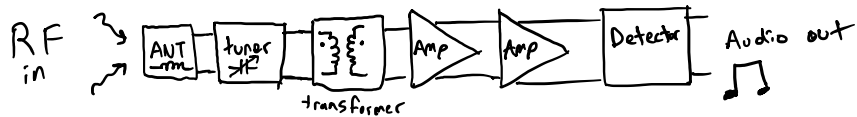

March 8, 2016

Analysis : PART 1

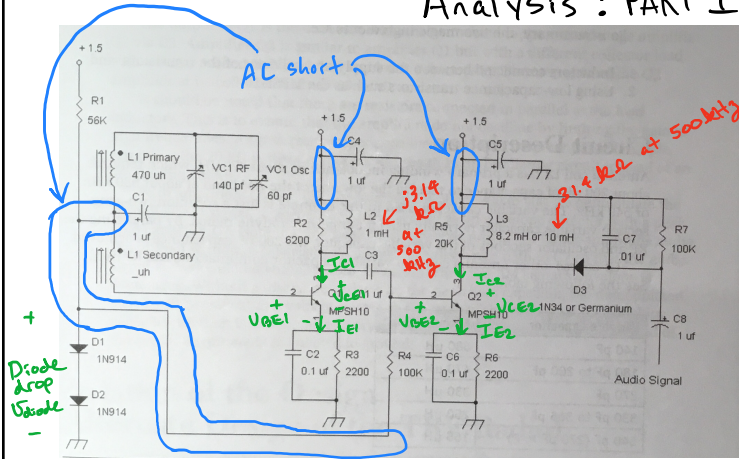

DC Quiescent Point - Assume Q_1 & Q_2 are in active region.

I_{C1} : $\sqrt{\approx I_{C1}}$
 $V_{diode} - V_{BE} \approx (I_{E1})(2200)$
 $\therefore I_{C1} = \frac{V_{diode} - V_{BE}}{2200}$

V_{CE1} :
 $V_{CE1} = 1.5V - (I_{E1})(2200)$
 $\therefore V_{CE1} = 1.5 - V_{diode} + V_{BE}$

I_{C2} :
 $V_{diode} - \frac{I_{C2} \cdot 100k}{\beta} - V_{BE2}$
 $\approx I_{C2} \cdot 2.2k$

V_{CE2} : $1.5V - (I_{E2})(2200)$
 $\therefore V_{CE2} = 1.5V - \left(\frac{V_{diode} - V_{BE2}}{2200 + \frac{100k\Omega}{\beta}} \right) \cdot 2200$

$\therefore I_{C2} = \frac{V_{diode} - V_{BE2}}{2200 + \frac{100k\Omega}{\beta}}$

Numerical Example

$V_{diode} = 0.76V$
 $V_{BE1} = V_{BE2} = 0.55V$
 $\beta = 100$


$I_{C1} = \frac{0.76 - 0.55}{2200} \approx 0.1mA$ DC
 $I_{C2} = \frac{0.76 - 0.55}{2200 + \frac{100k\Omega}{100}} \approx 0.07mA$ DC

$V_{CE1} = 1.5 - 0.76 + 0.55 \approx 1.3V$ DC
 $V_{CE2} \approx 1.36V$ DC


Amplifier 1:

AC EQUIVALENT (simplified)


ANALYSIS PART 2

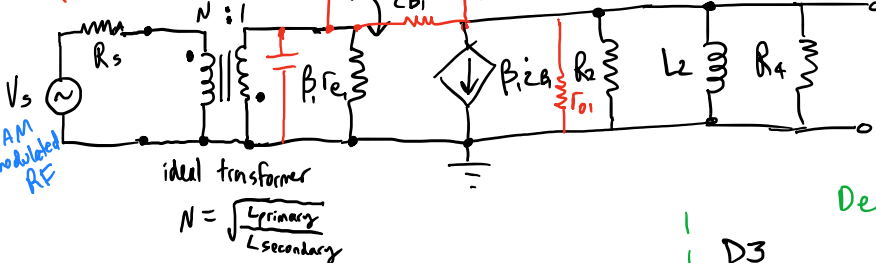

Amplifier 2:

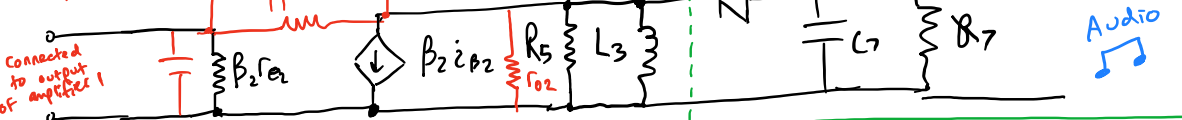

Simplified Equivalent circuit

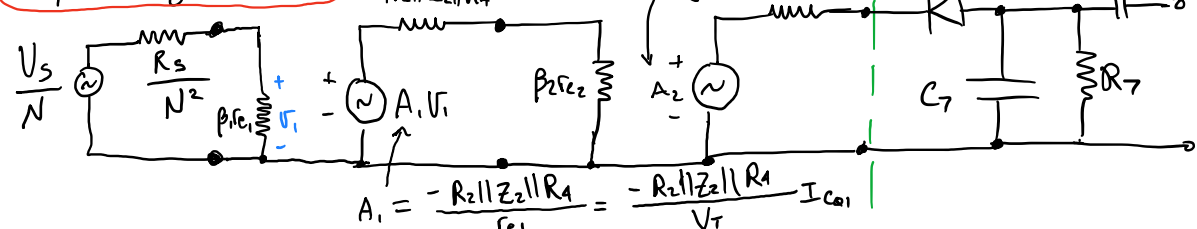

Numerical example

ANALYSIS
PART 3

$I_{CQ1} = 0.1 \text{ mA}$
 $I_{CQ2} = 0.07 \text{ mA}$

$f = 500 \text{ kHz}$
 $R_2 = 6.2 \text{ k}\Omega$
 $R_4 = 100 \text{ k}\Omega$

$\beta_2 r_{e2} = \beta_2 \frac{V_T}{I_{CQ2}} = (100) \frac{26}{0.07} = 37.14 \text{ k}\Omega$

$R_5 = 20 \text{ k}\Omega$ $Z_3 = j\omega L_3 = j 31.4 \text{ k}\Omega$

$Z_2 = j\omega L_2 = j 3.14 \text{ k}\Omega$

$R_5 \parallel Z_3 = 16.87 \text{ k}\Omega \angle 32.48^\circ$


$R_2 \parallel R_4 \parallel Z_2 \approx 2.76 \text{ k}\Omega \angle 62^\circ$

$\beta_1 = \beta_2 = 100$


$\beta_1 r_{e1} = \beta_1 \frac{V_T}{I_{CQ1}} = (100) \frac{26}{0.1} = 26 \text{ k}\Omega$

$A_1 = \frac{-2.76 \text{ k}\Omega \angle 62^\circ}{V_T} I_{CQ1} = -10.64 \angle 62^\circ$

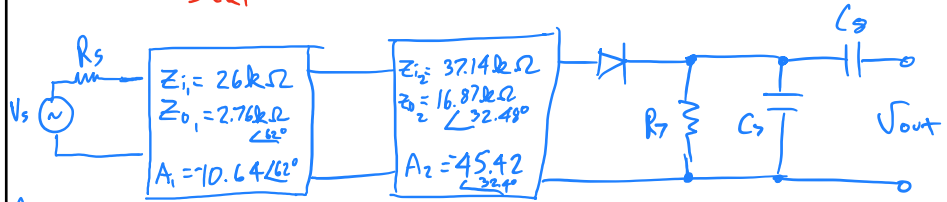$A_2 = \frac{-R_5 \parallel Z_3}{V_T} I_{CQ2} = -45.42 \angle 32.48^\circ$



Approximate:

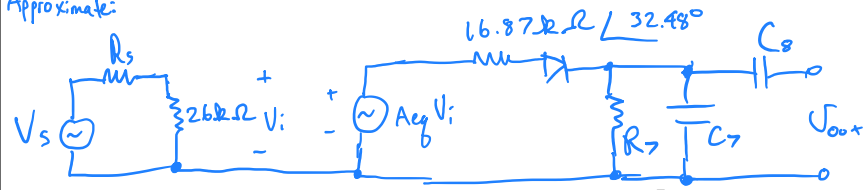


$A_{eq} = \frac{Z_{i2}}{Z_{o1} + Z_{i2}} A_1 A_2 \approx 469 \angle 91^\circ$


Large gain!
≈ 90° phase shift

Verified to be pretty accurate with LTspice.

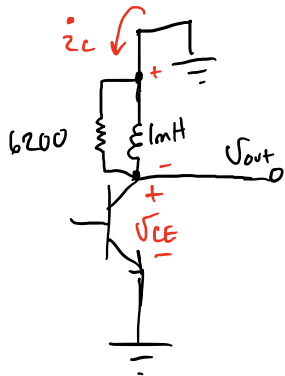Cut-off / Saturation : Eventually input will be so big that it will drive the BJT into cut-off or saturation. This causes the output to clip. Let's find the min/max values of V_{out} before clipping sets in.



First CE amplifier
AC equivalent

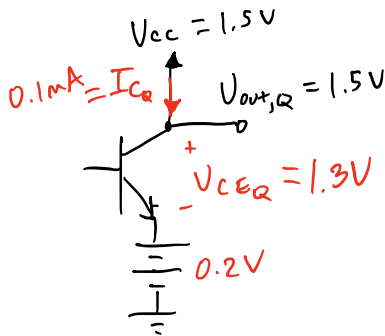

First CE amplifier
DC equivalent

total **SATURATION**

DC \downarrow $V_{CE} \approx 0.2V$ AC \leftarrow

$$V_{CE} = V_{CEQ} + \sqrt{V_{CE}}$$

$$V_{CE} = 1.3V + \sqrt{V_{CE}}$$

saturation: $V_{CE} \approx 0.2$ ← total V_{CE}

$$\rightarrow \sqrt{V_{CE}} = -1.1V$$

\therefore BJT saturates when $V_{CE} = \sqrt{V_{CE}} = -1.1V$


CUT-OFF $\leftarrow I_C \approx 0$

currents exactly cancel each other out \rightarrow


$$\frac{\sqrt{V_{CE}}}{Z_C} = I_{CQ} \rightarrow \sqrt{V_{CE}} = Z_C I_{CQ} = 0.28V$$

\therefore BJT is cut-off when $V_{CE} = \sqrt{V_{CE}} = 0.28V$

Antenna Equivalent Circuit

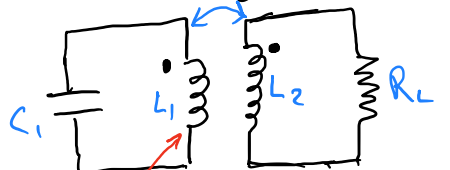


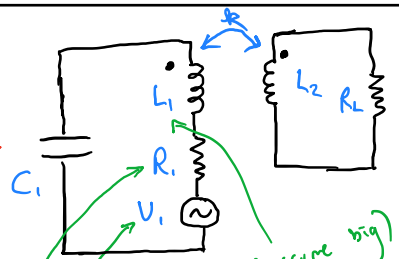antenna coil picking up RF
 $\omega_0 = \frac{1}{\sqrt{L_1 C_1}}$




ohmic + radiation resistance (small)
 (small)

resonates at ω_0

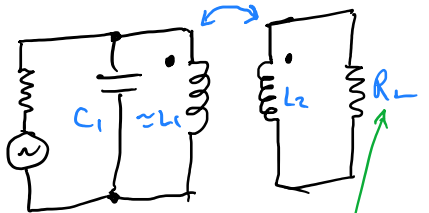


(really big)
 (big)

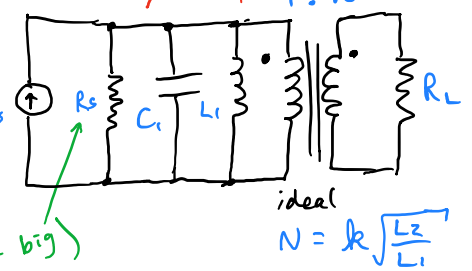

(small)
 (really big)

ideal
 $N = k \sqrt{\frac{L_2}{L_1}}$

Design notes

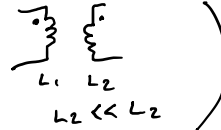- Inductive loading at collectors of Q_1 & Q_2 raises V_{CB} to reduce internal collector-to-base capacitances of transistors.
- Transistor was chosen to be low capacitor type
- Frequency adjusted by variable capacitor across antenna coil. Transformer step down chosen (i.e.  so that AC input impedance looking into Q_1 is stepped up to increase resonant Q of antenna coil (increase selectivity).
I guess this also increases sensitivity by providing a better impedance match to the coils large equivalent shunt resistance.
- Resistors are connected in parallel with collector inductors. This is to reduce gain at high frequencies. Author says this is needed to prevent oscillations. Remove the resistors and the thing oscillates.
- Germanium diode used as envelope detector.
- Detector cap C_7 is peak hold cap. R_7 gives discharge path. Without R_7 , the voltage would be pinned or "stuck" at a voltage related to peak of AM signal, resulting in gross "failure to follow" distortion.