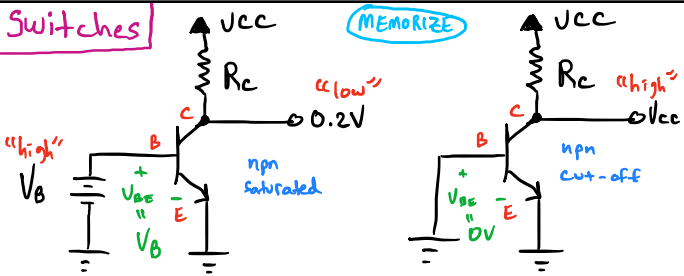



Switches

MEMORIZE



condition for saturation:
 $V_B > 0.7V$

nnp switch (no source/load impedance)

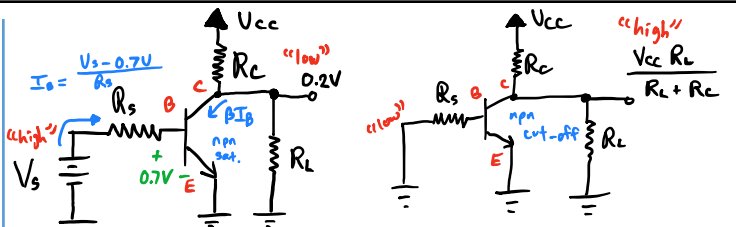

condition for saturation:


$$I_B = \frac{V_s - 0.7V}{R_s}$$

$$\frac{V_s - 0.7V}{R_s} \beta > \frac{V_{CC} - 0.2V}{R_C}$$

$$\Rightarrow V_s > V_{CC} \left(\frac{R_C}{\beta R_s} \right) + 0.7V$$


nnp switch (with source/load impedances)

MEMORIZE

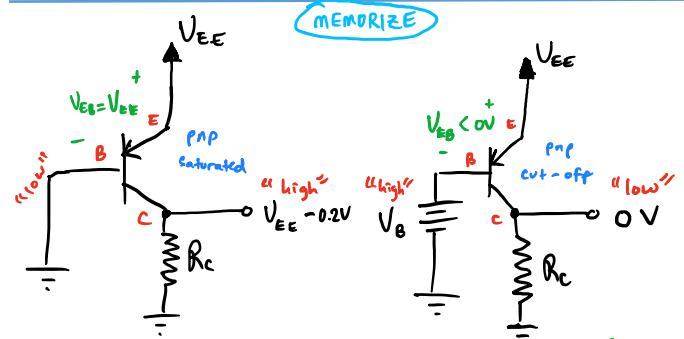

condition for cut-off:
 $V_B \geq V_{EE}$


pnp switch (simple)

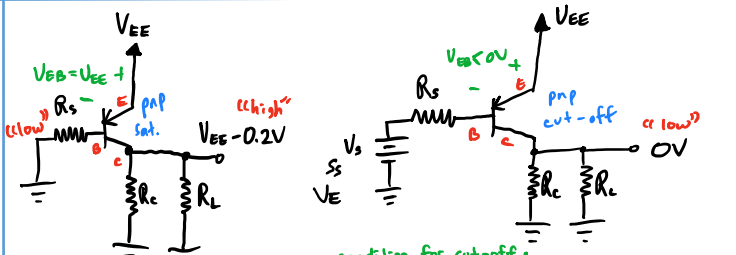

condition for cut-off:
 $V_s \geq V_{EE} - 0.7V$


pnp switch (with source/load impedances)

More switches

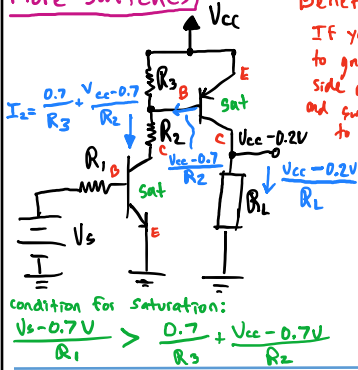


Benefit:

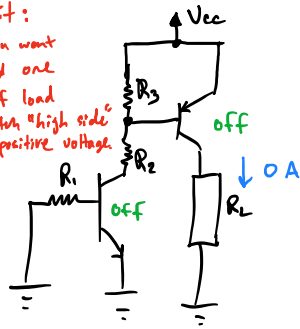IF you want to ground one side of load and switch "high side" to positive voltage.



Putting emitter follower in front of switch makes it easy for a low-current control signal to switch a high-current load.

Emitter follower

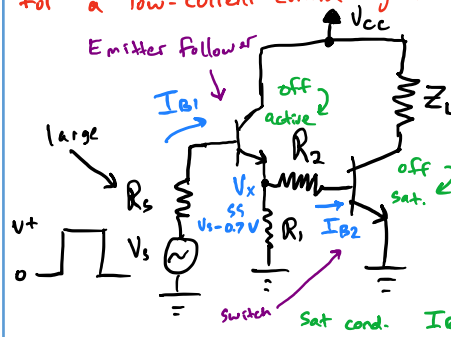

When $V_s = V^+$:

$$I_{B1} = \frac{V^+ - 0.7}{R_s + \beta R_1 + R_2}$$

$$\approx \frac{V^+ - 0.7V}{R_s + \beta R_2} \quad (R_1 \gg R_2)$$


$$V_x \approx V_s - 0.7V$$

$$I_{B2} \approx \frac{V_s - 1.4V}{R_2}$$


$I_{B2} > V_{cc}/Z_L$

Voltage followers
(Emitter followers)


MEMORIZE

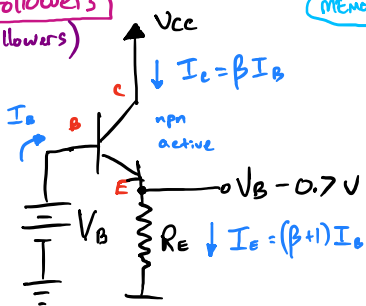

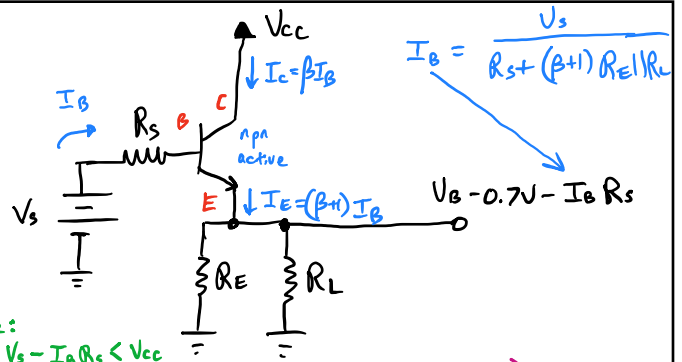
Assume: $V_B < V_{CC}$, $V_B > 0.7V$
nPN voltage follower (no source/load impedances)



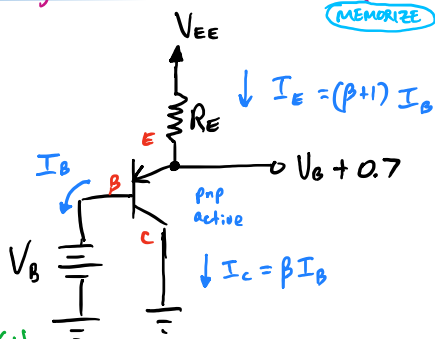Assume:
 $0.7V < V_s - I_B R_s < V_{CC}$
nPN voltage follower (with source/load impedances)




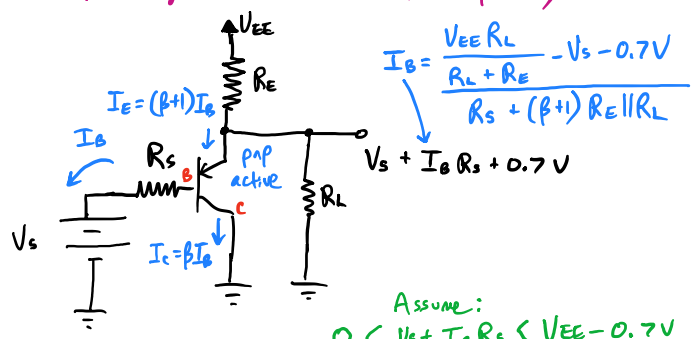Assume: $V_B < V_{EE}$
pNP voltage follower (no source/load impedances)



Assume:
 $0 < V_s + I_B R_s < V_{EE} - 0.7V$
pNP voltage follower (with source/load impedances)


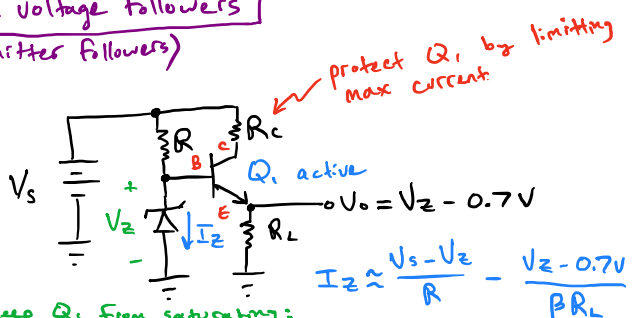
More voltage followers
(Emitter followers)





To keep Q_1 from saturating:
 $\frac{V_z - 0.7V}{R_L} < \frac{V_s}{R_c}$

Current sources





memorize

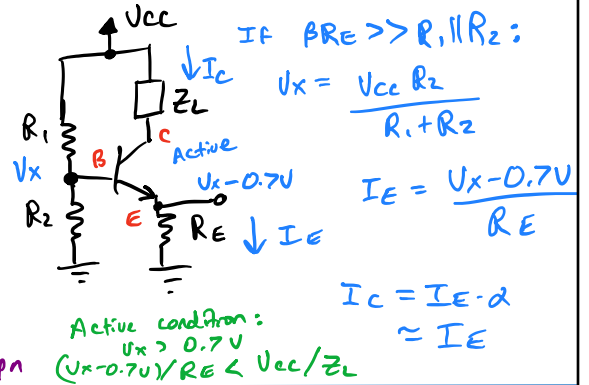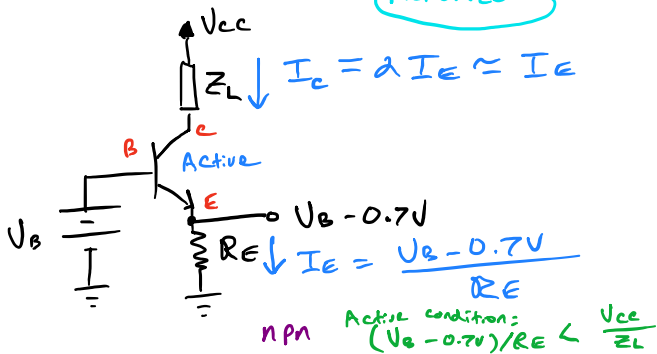





memorize

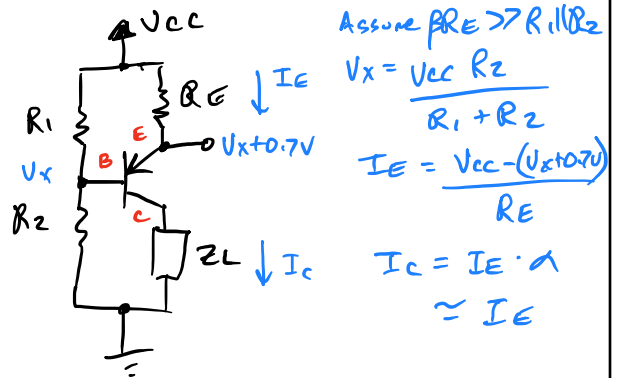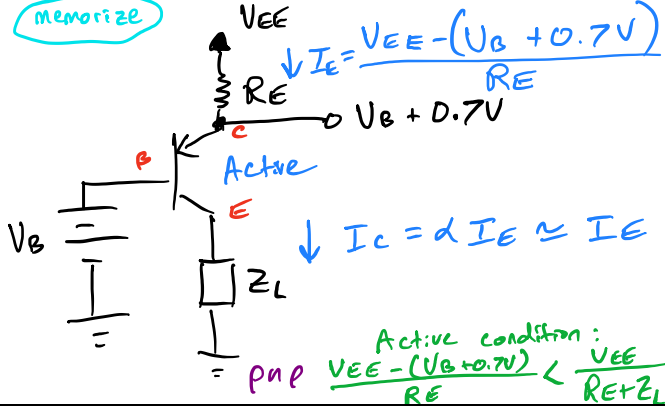

Common Emitter Amplifier

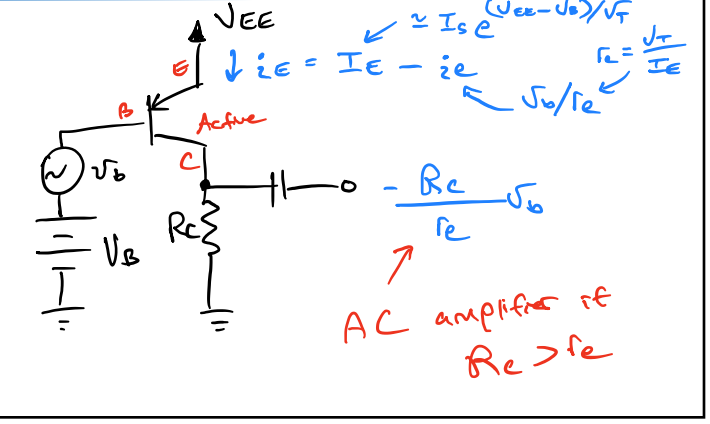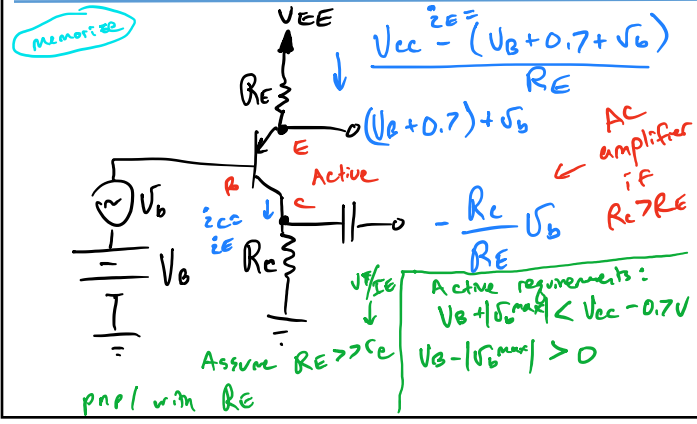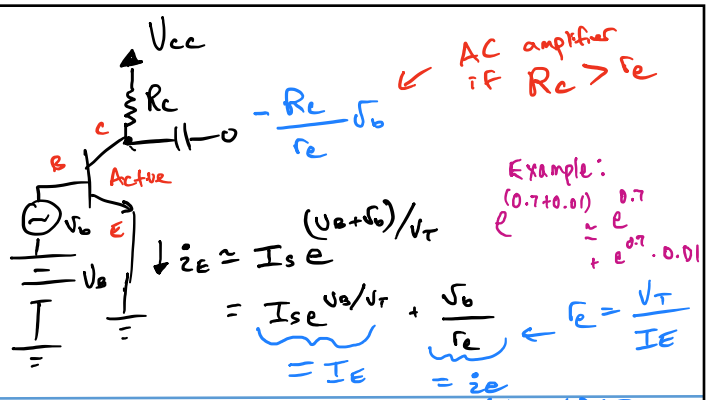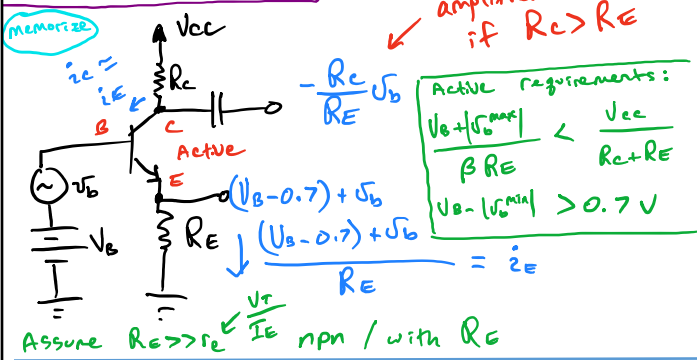

More common emitter amplifiers

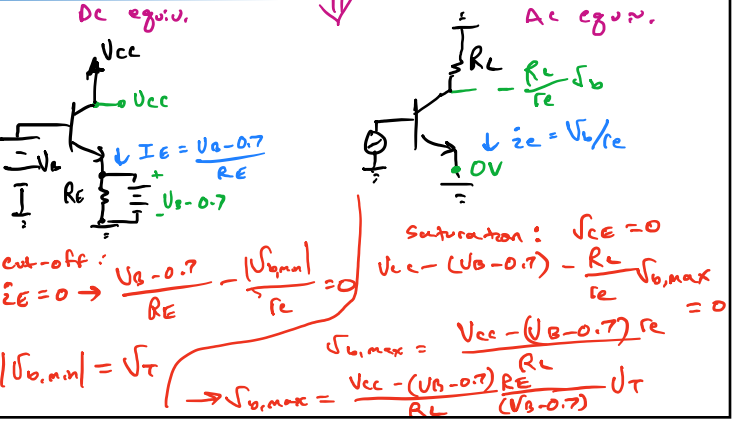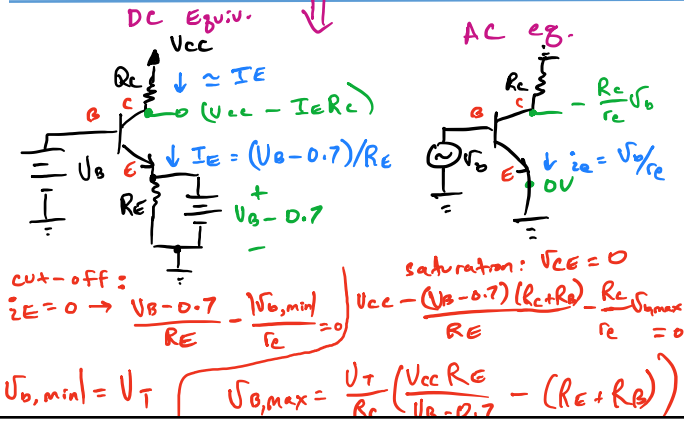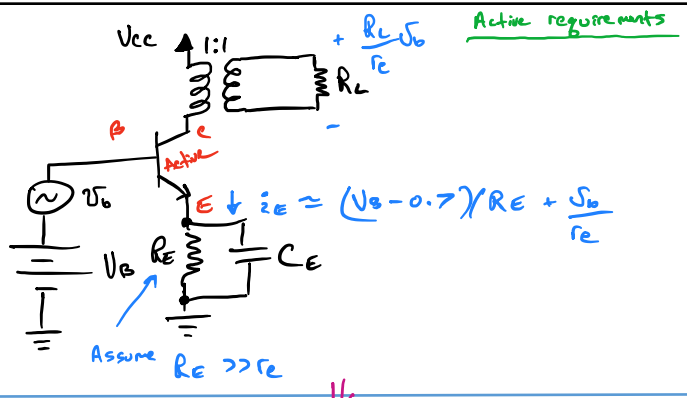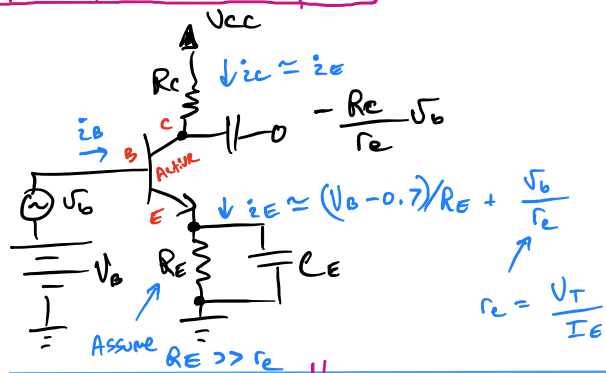

Current Mirror

ignoring Early Voltage

Recall: $i_B = \left(\frac{I_S}{\beta}\right) e^{V_{BE}/V_T}$

since $V_{BE1} = V_{BE2} \rightarrow i_{B1} = i_{B2} = i_B$

$i_{ref} = i_{c1} + i_{B1} + i_{B2}$

$\rightarrow i_{ref} = i_{c1} + 2i_B$

$i_{c1} = I_S e^{V_{EB1}/V_T} \left(1 + \frac{\sqrt{V_{EC1}}}{|V_A|}\right)$

$\sqrt{V_{EC1}} = 0.7V \ll |V_A|$

$\approx I_S e^{V_{EB1}/V_T} = \beta i_B$

\therefore


$\rightarrow i_{ref} = i_{c1} + 2i_B \rightarrow i_p = (2 + \beta) i_B$

$\rightarrow i_{ref} = \frac{V_{CC} - V_{EB}}{R_p}$

$\rightarrow i_B = \frac{i_{ref}}{2 + \beta}$


$\rightarrow i_{c2} = \beta i_B = \frac{\beta i_{ref}}{2 + \beta}$

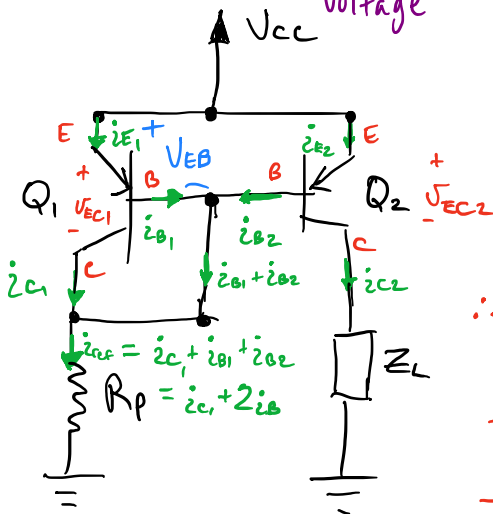$\rightarrow i_{c2} = \frac{i_{ref}}{\frac{2}{\beta} + 1}$



Current Mirror Taking into account

Early voltage

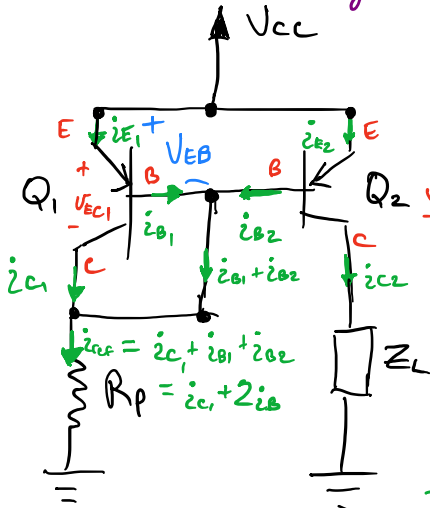

$$i_{ref} = i_{c1} + 2i_B \rightarrow i_C = (2 + \beta_0) i_B$$

$$\rightarrow i_{ref} = \frac{V_{CC} - V_{EB}}{R_p} \rightarrow i_B = \frac{i_{ref}}{2 + \beta_0}$$

$$i_{C2} = \beta_0 i_B \left(1 + \frac{V_{EC2}}{|V_A|}\right) = \beta_0 i_B \left(1 + \frac{V_{CC} - i_{C2} Z_L}{|V_A|}\right)$$

$$\rightarrow i_{C2} = \beta_0 i_B \left(1 + \frac{V_{CC}}{|V_A|}\right) = \left(\frac{1}{\frac{Z}{\beta_0} + 1}\right) i_{ref} \left(1 + \frac{V_{CC}}{|V_A|}\right)$$

$$i_{ref}' = \left(\frac{1}{\frac{Z}{\beta_0} + 1}\right) i_{ref}$$


$$= \frac{i_{ref} \left(1 + \frac{V_{CC}}{|V_A|}\right)}{1 + i_{ref}' \frac{Z_L}{|V_A|}} = \frac{Z_{out} i_{ref}'}{Z_{out} + Z_L}$$

$$Z_{out} = \frac{|V_A|}{i_{ref}'}$$


$$= \frac{|V_A| R_p}{V_{CC} - V_{EB}}$$



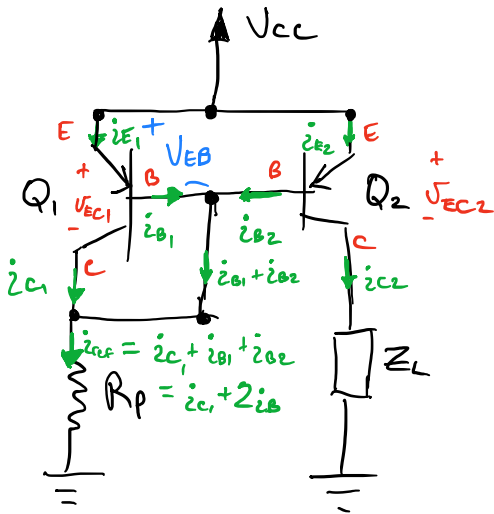Current Mirror (Taking into account the Early Effect) ... using AC small signal model to determine the output impedance.




AC small signal equivalent circuit:

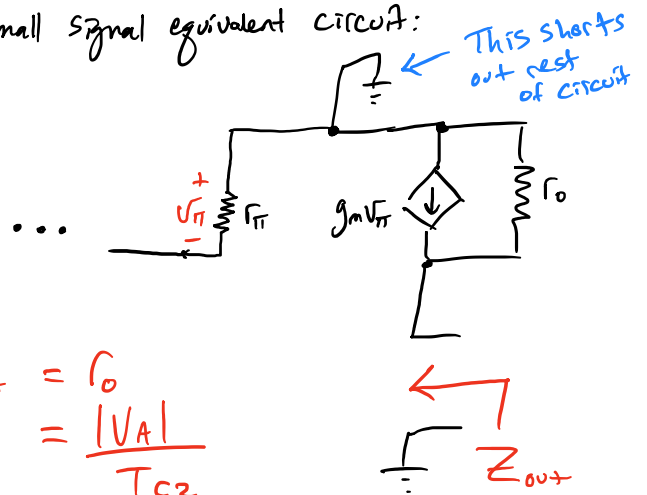


$$Z_{out} = r_o = \frac{|V_A|}{I_{C2}}$$

$$\approx \frac{|V_A|}{I_{ref}}$$

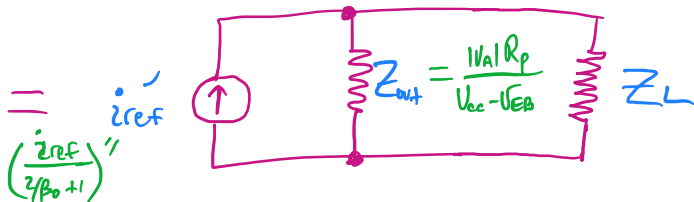

Different ways of analyzing common emitter analyzer...

Method 1: Assume $V_{BE} = \text{constant} \equiv V_{BE}$

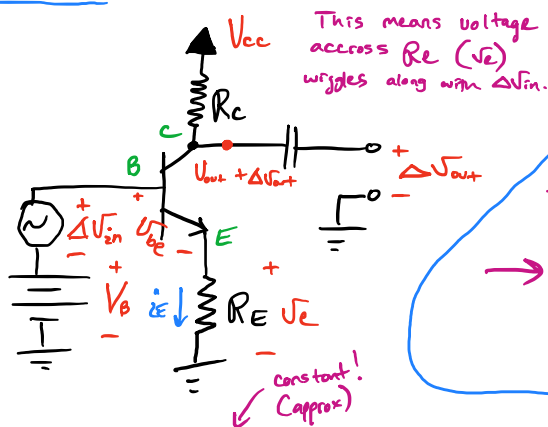

Method 2: Nonlinear long way...

$$i_c = \left(\frac{I_s}{\beta}\right) e^{V_{BE}/U_T} \quad (\text{ignore Early Effect})$$

$$(V_B + \Delta V_{in}) = V_{BE} + i_E R_E = V_{BE} + \alpha i_c R_E$$

$$\rightarrow V_B + \Delta V_{in} = V_{BE} + \alpha R_E I_s e^{V_{BE}/U_T}$$

solve for V_{BE}

$$\rightarrow V_{out} = (V_{CC} - i_c R_C) \quad \text{plug in}$$

$$= V_{CC} - (I_s e^{V_{BE}/U_T}) R_C$$

$$-V_B - \Delta V_{in} + V_{BE} + (I_E + \Delta i_E) R_E = 0$$


Equate AC and DC components:

$$I_E = (V_B - V_{BE}) / R_E$$


$$\Delta i_E = \Delta V_{in} / R_E \Rightarrow \Delta V_{out} = -\frac{R_C}{R_E} \frac{\Delta V_{in}}{\alpha} \approx -\frac{R_C}{R_E} \Delta V_{in}$$

$$\Delta i_c = \Delta i_E / \alpha$$

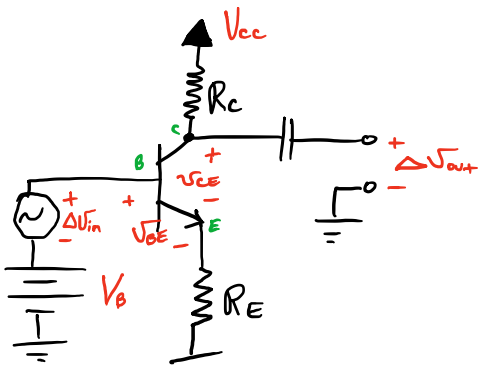Different ways of analyzing common emitter analyzer...
 method 3: Small signal model



Small signal:

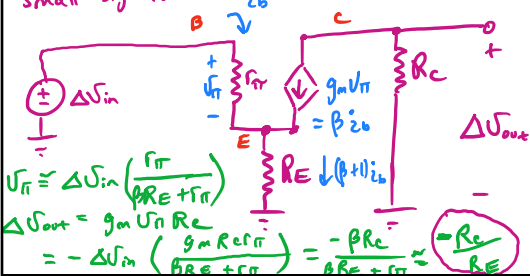

$$V_{BE} = V_{BE} + U_{be}$$

$$i_B = \frac{I_s}{\beta} e^{(V_{BE} + U_{be})/V_T} \approx I_B + \frac{d}{2V_{BE}} \left(\frac{I_s}{\beta} e^{V_{BE}/V_T} \right) U_{be}$$

$$= I_B + \frac{I_B}{V_T} U_{be}$$

$$\therefore i_B \approx I_B + \frac{1}{r_{\pi}} U_{be}, \quad r_{\pi} = V_T / I_B$$

$$i_c = \beta_0 i_B \left(1 + \frac{V_{CE}}{|V_A|} \right) = \beta_0 \left(I_B + \frac{1}{r_{\pi}} U_{be} \right) \left(1 + \frac{V_{CE} + U_{ce}}{V_A} \right)$$

$$= \beta_0 \left(I_B + \frac{I_B V_{CE}}{|V_A|} + \frac{I_B U_{ce}}{|V_A|} + \frac{1}{r_{\pi}} U_{be} + \frac{V_{CE} U_{ce}}{r_{\pi} V_A} + \frac{U_{be} U_{ce}}{|V_A| r_{\pi}} \right)$$

$$= \beta_0 I_B \left(1 + \frac{V_{CE}}{|V_A|} \right) + \frac{\beta_0 I_B U_{ce}}{|V_A|} + \frac{\beta_0 U_{be}}{r_{\pi}} + \frac{V_{CE} U_{be} \beta_0}{|V_A| r_{\pi}}$$


$$= I_c + \frac{V_{CE}}{r_o} + g_m U_{be}$$

$$r_o = \frac{|V_A|}{\beta_0 I_B} \approx \frac{|V_A|}{I_c} \quad g_m = \frac{\beta_0}{r_{\pi}} \left(1 + \frac{V_{CE}}{|V_A|} \right) = \frac{I_B \beta_0}{V_T} \left(1 + \frac{V_{CE}}{|V_A|} \right)$$

$$\therefore i_c = I_c + \frac{V_{ce}}{r_o} + g_m U_{be}, \quad r_o = |V_A| / I_c, \quad g_m = I_c / V_T$$


Different ways of analyzing common emitter analyzer...

Method 1: Looking at feedback

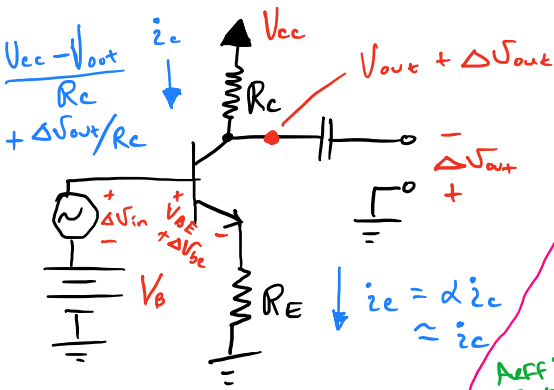

$$\Delta V_{be} = \Delta V_{in} - \frac{R_E}{R_C} \Delta V_{out}$$

Conventional Block Diagram: ΔV_{out}

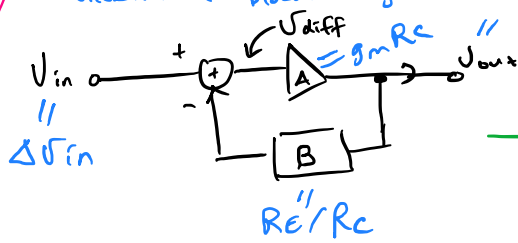

$$A(V_{in} - B V_{out}) = V_{out}$$

$$\rightarrow V_{out} = \frac{A}{1 + AB} V_{in}$$

$$\rightarrow V_{out} \approx \frac{V_{in}}{B} \quad (AB \gg 1)$$

Assume:

$$A_{eff} \Delta V_{be} = \Delta i_c = \Delta V_{out} / R_C$$

$$\rightarrow R_C A_{eff} \Delta V_{be} = \Delta V_{out} \quad \text{with } B \equiv R_E / R_C$$

$$A_{eff} (\Delta V_{in} - B \Delta V_{out}) = \Delta V_{out}$$

$$\rightarrow \Delta V_{out} = \frac{A_{eff}}{1 + A_{eff} B} \approx \frac{1}{B} = \frac{R_C}{R_E}$$



A_{eff} is the small signal gain:

$$A_{eff} = g_m = I_C / V_T$$

Summary of feedback point of View for common Emitter Amplifier.

ignoring Early Effect: only small signals shown

Main Equations:

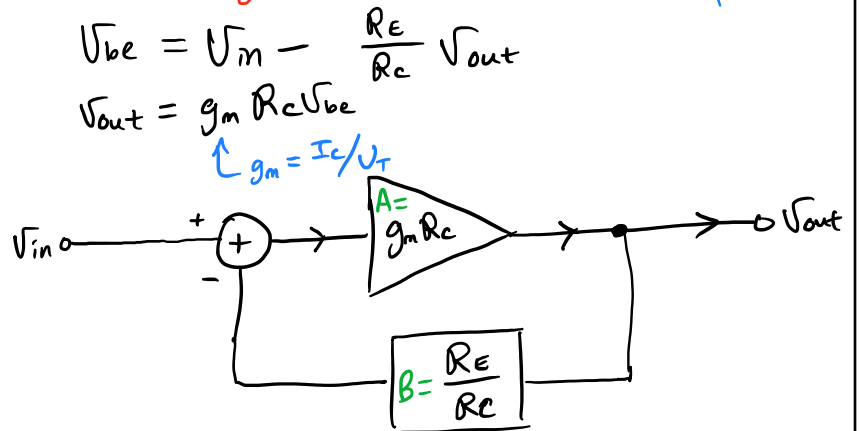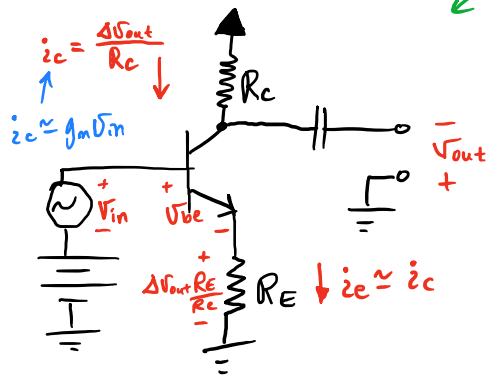

$$V_{out} = \frac{A}{1 + AB} V_{in}$$

where: $A = g_m R_c$ and $B = \frac{R_E}{R_c}$