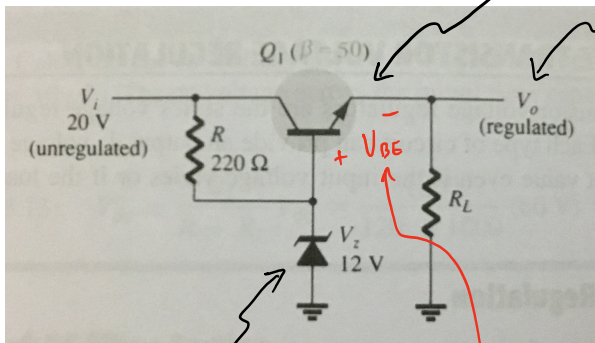


Simple series Voltage regulator circuit.


Note: It's in the emitter follower configuration




reference voltage

Comparator voltage causes Q_1 to conduct more or less...

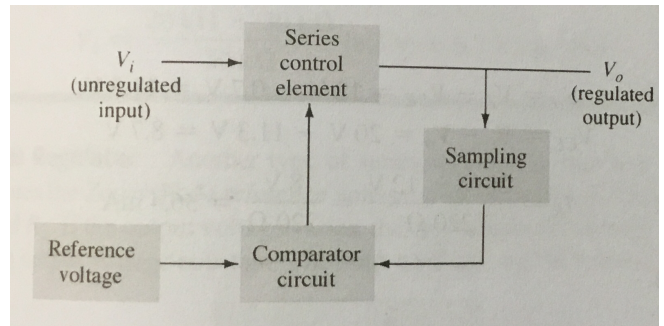series control element
sample output = output



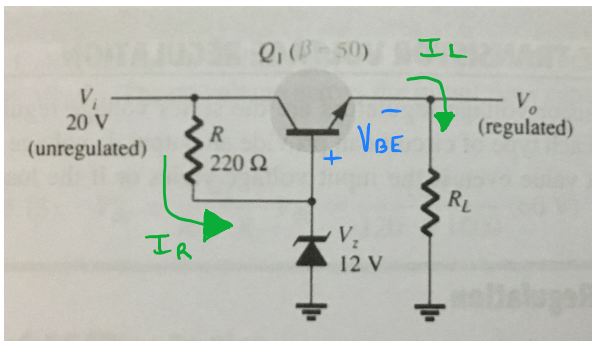

Basic operation (feedback describing regulating operation)

$R_L \downarrow \rightarrow V_o \downarrow \rightarrow V_{BE} \uparrow \rightarrow I_L \uparrow \rightarrow V_o \uparrow$
 assume current through resistor stays momentarily constant
 feedback

$$I_L = I_E = \alpha I_S e^{V_{BE}/V_T}$$

Benefit: Zener current is voltage pretty constant w/ changing loads.

Disadvantage: V_o limited to V_z values...

$$\frac{12 - V_{BE}}{R_L} = \alpha I_S e^{V_{BE}/V_T}$$

This is the equation to solve!

Analysis

$$V_o = 12 - V_{BE} \approx 12 - 0.7 = 11.3 \text{ V}$$


$$V_{CE} = V_i - V_o = 20 - 11.3 \text{ V} = 8.7 \text{ V}$$

$$I_R = \frac{20 - 12}{220} = 36.4 \text{ mA}$$


$$\text{If } R_L = 1 \text{ k}\Omega \rightarrow I_L = \frac{11.3 \text{ V}}{1 \text{ k}\Omega} = 11.3 \text{ mA}$$

$$I_B = I_C / \beta = \frac{11.3 \text{ mA}}{50} = 226 \mu\text{A} \rightarrow I_Z = I_R - I_B = 36.4 \text{ mA} - 226 \mu\text{A} = 36 \text{ mA}$$


$$I_L = I_E \approx I_C$$

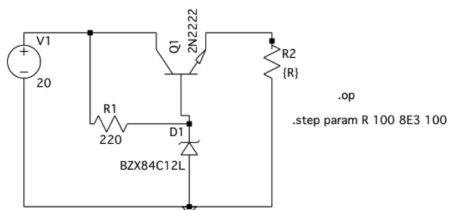

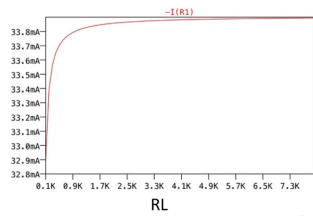Current through R1 as a function of load resistance RL





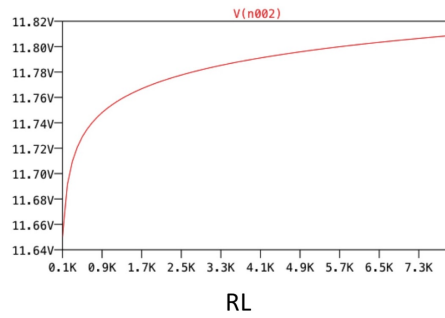
Output voltage as a function of load resistance RL



Zener diode voltage as a function of load resistance RL

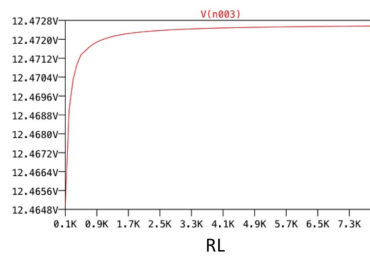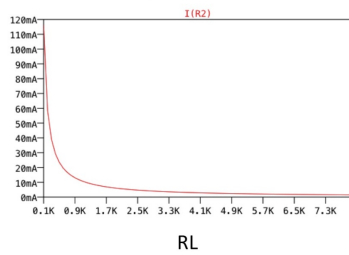
Output current as a function of load resistance RL



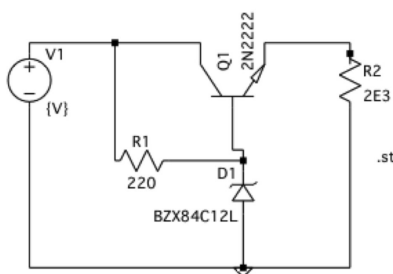


.op
 .step param V 15 40 1


Output voltage as a function of Vin


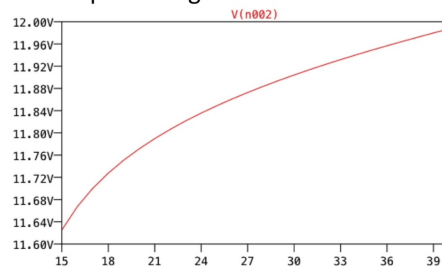


Zener voltage as a function of Vin

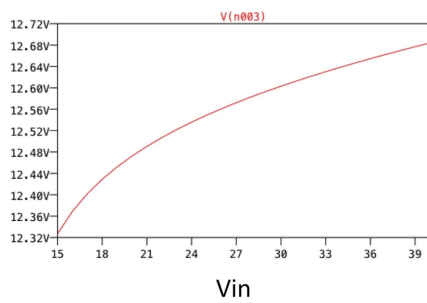


Current through R1 as a function Vin

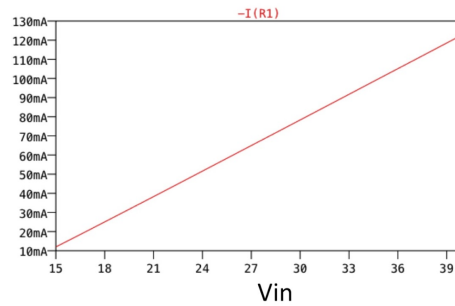

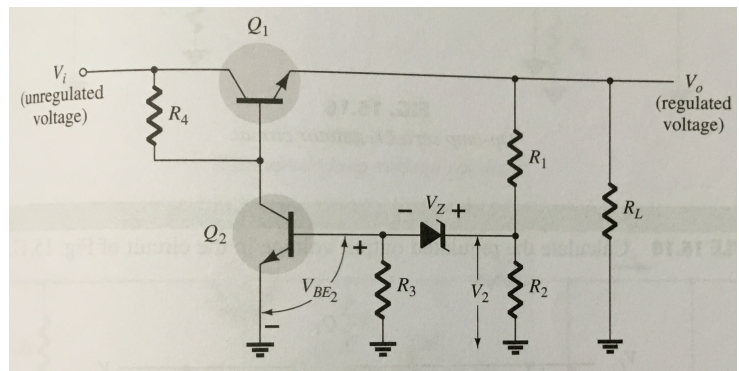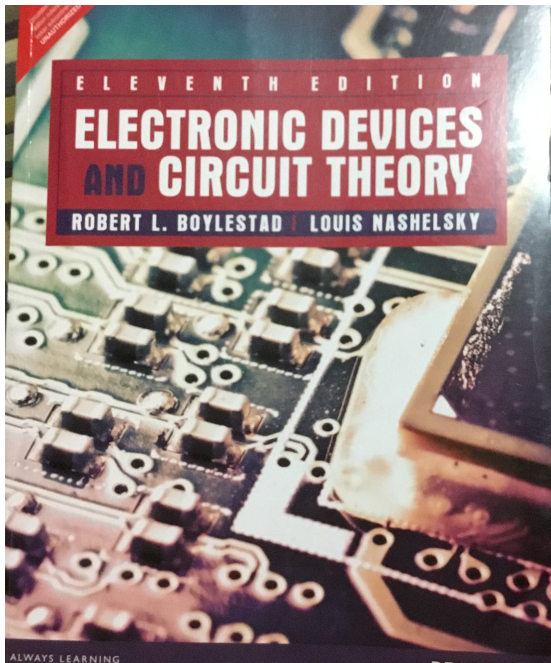


"Improved" series voltage regulator

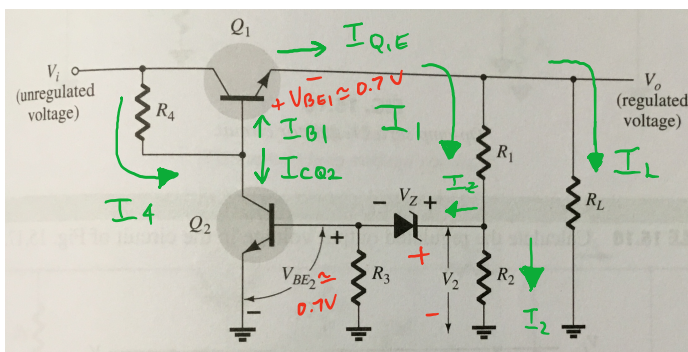The only improvement I really see over previous regulator is that V_o is set by V_Z and R_1 & R_2 ... so you can set V_o to any arbitrary value (not just those determined by V_Z)



Arrow analysis:

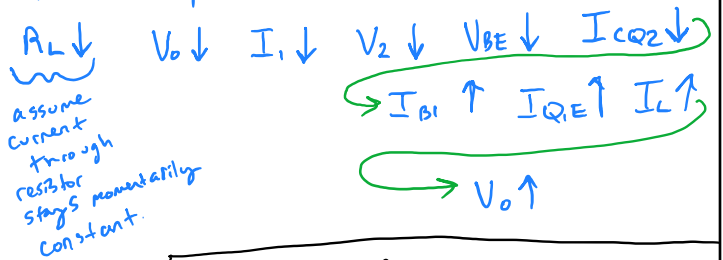

Example: $R_1 = 20k\Omega$, $R_2 = 30k\Omega$, $V_Z = 8.3V$


$$V_2 = V_{BE2} + V_Z \approx 9V$$


$$9V = V_o \frac{R_2}{R_2 + R_1}$$

$$V_o = \frac{(9)(R_2 + R_1)}{R_2}$$

$$= \frac{9.50k}{30k} = 15V$$

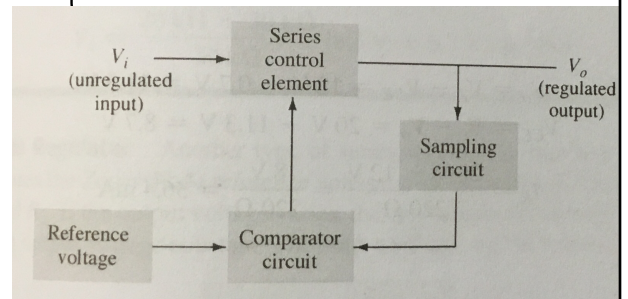After many Spice simulations, I see that this circuit is very dependent on resistor values! If R_4 or R_3 are too small then the system will not work...



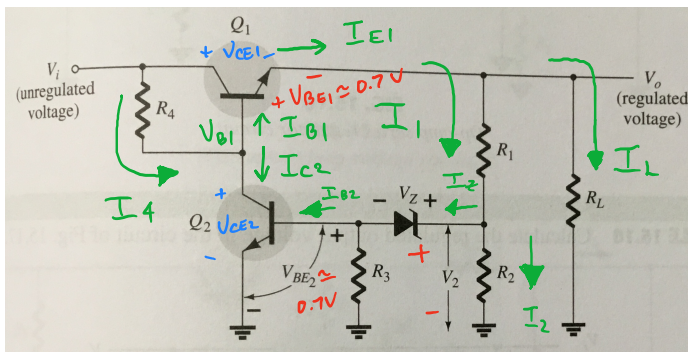

Assumptions

• Q_1 & Q_2 are in active region

- $V_{BE1} \approx 0.7V$ $V_{CE1} > 0.2V$
- $V_{BE2} \approx 0.7V$ $V_{CE2} > 0.2V$
- $I_{E1} \approx \beta I_{B1}$ $V_{B1} \approx V_o + 0.7V$
- $I_{E2} \approx \beta_2 I_{B2}$

Assume I_{B1} stays same

Another arrow analysis (start w/ input)

$$V_i \uparrow \quad I_4 \uparrow \quad I_{C2} \uparrow \quad I_{B2} \uparrow$$

$$V_{BE2} \uparrow \quad I_2 \uparrow$$

since $I_2 \ll I_1, I_2$

nothing else changes!


so V_o stays the same which agrees w/ assumption that I_{B1} stays the same.

• $I_2 \ll I_1, I_2$

$$\therefore \frac{0.7}{R_3} + \frac{I_{C2}}{\beta} \ll \frac{V_2 + 0.7}{R_2}$$


$$\Rightarrow \frac{0.7}{R_3} + \frac{(V_i - V_{B1})}{\beta R_4} \ll \frac{V_2 + 0.7}{R_2}$$

Scratch

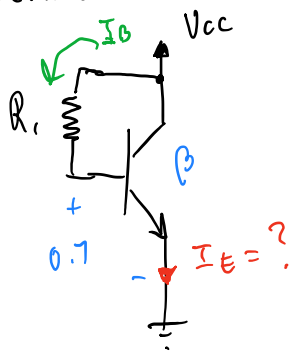

$$\frac{V_{cc} - 0.7}{R_1} = I_B \approx \frac{I_E}{\beta}$$


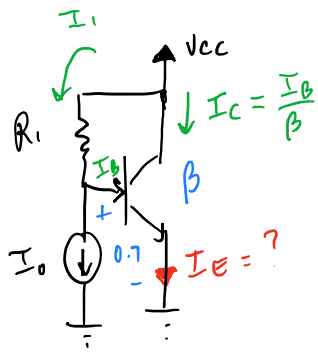
$$\rightarrow I_E = \frac{\beta}{R_1} (V_{cc} - 0.7)$$




$$I_1 = I_B + I_o$$

$$\frac{V_{cc} - 0.7}{R_1} = I_E + I_o$$

?

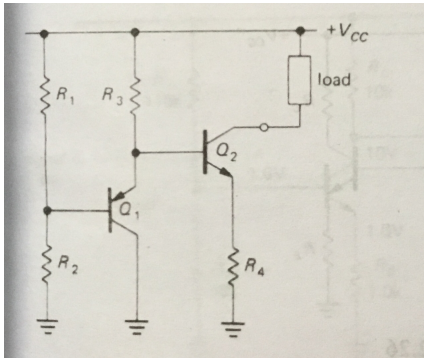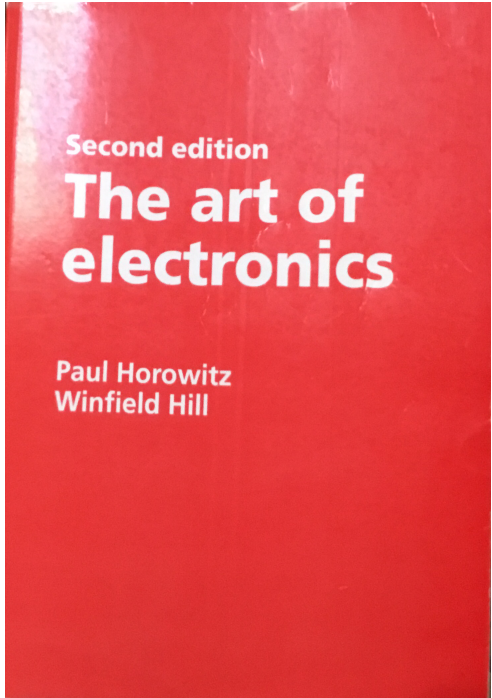

Temperature compensated current source

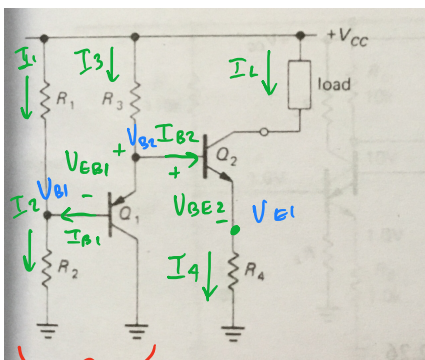

Emitter follows

- The basic idea: supply constant current through load.
- problem this circuit tries to fix: β and V_{BE}

change w/ temperature w/ changes w/ load
 current $V_{BE} \rightarrow (-2mV/^\circ C)$ $V_{BE} \rightarrow (-0.0001 \Delta V_{CE})$
temp dependence Early effect

Analysis:

$$I_1 + I_{B1} = I_2 \approx 0 \text{ for } R_3 \beta \gg R_1$$

$$\frac{V_{CC} - V_{CE1}}{R_1} + \frac{V_{CC} - (V_{BE1} + V_{BE2})}{R_3 \beta} = I_2$$

$$\frac{R_2}{R_2 + R_1} V_{CC}$$



A change in V_{BE1} is counteracted by an opposite change in V_{BE2} .

$$\rightarrow V_{BE1} \approx \text{constant} = \frac{R_2}{R_2 + R_1} V_{CC}$$


$$\rightarrow V_{BE2} = V_{BE1} + V_{CE1}$$

$$\rightarrow V_{CE1} = V_{BE1} + V_{BE2} - V_{BE1} \rightarrow$$
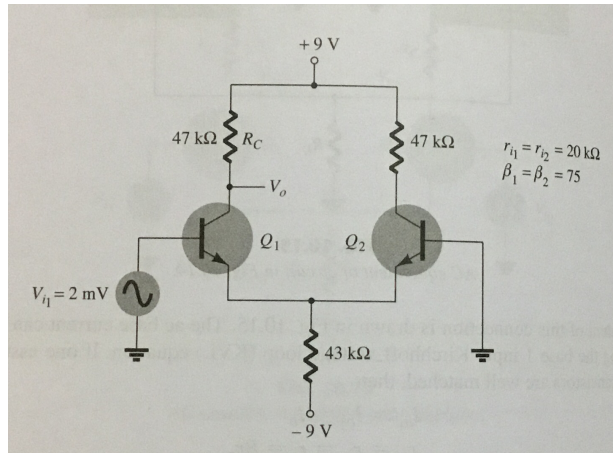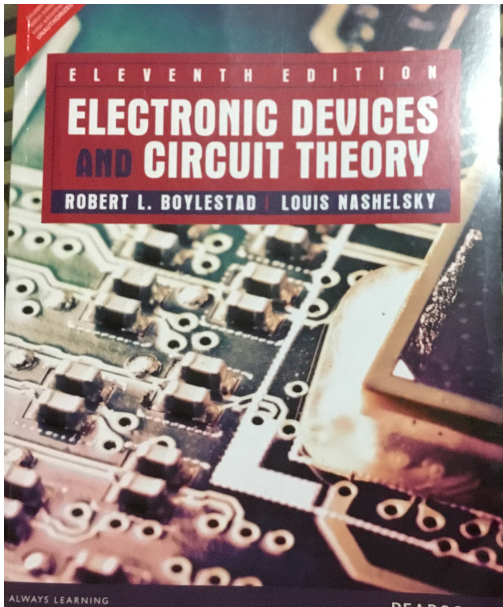
$$I_4 = \frac{V_{BE1} + V_{BE2} - V_{BE1}}{R_4}$$




Differential amplifier circuit

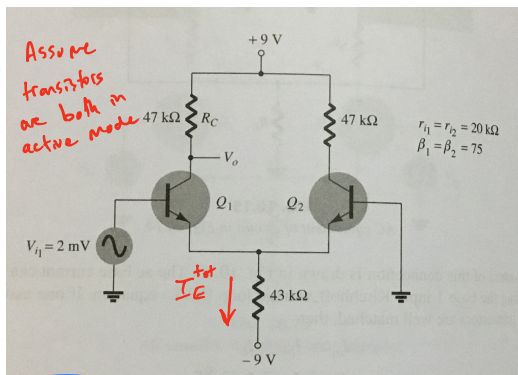

Goal: Find V_o

Even odd mode analysis

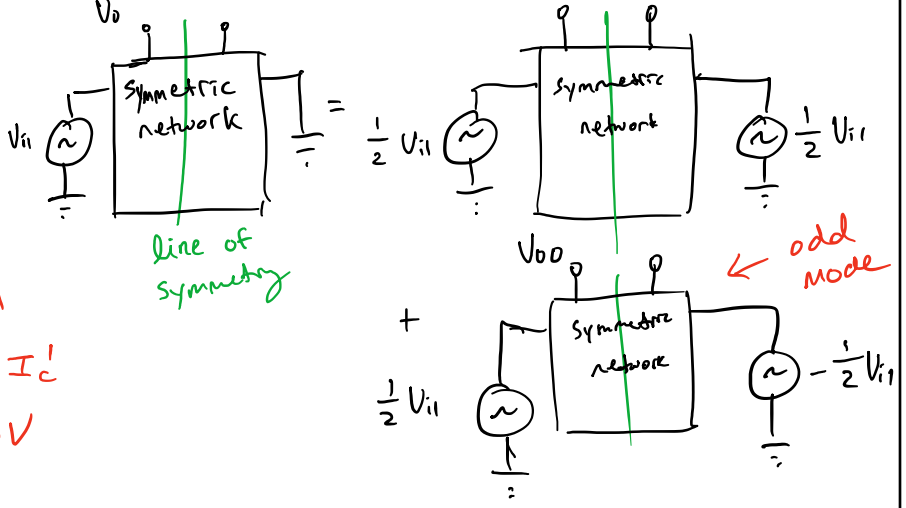


DC Bias: $I_E^{tot} = \frac{9 - 0.7}{43 \text{ k}\Omega} = 193 \mu\text{A}$


$\therefore I_E' = I_E^{tot} / 2 = 96.5 \mu\text{A} \approx I_C'$

$V_{ce} = \frac{V_{cc} - I_C'}{47 \text{ k}\Omega} = 4.5 \text{V}$

Total output = $V_{oe} + V_{oo}$

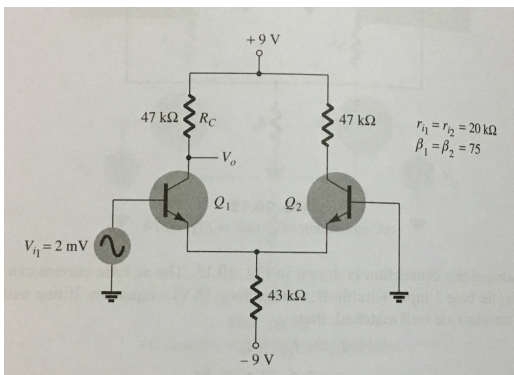


Odd mode (AC eg)


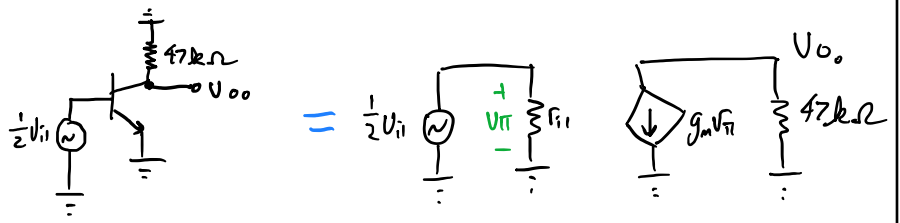


$$g_m = \frac{q I_c}{kT} = \frac{I_c}{26 \text{ mV}}$$
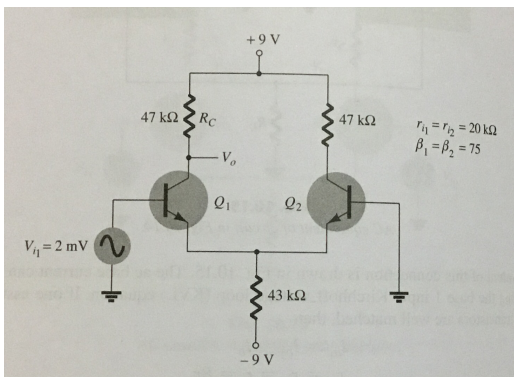
$$\begin{aligned} \therefore V_{o0} &= -\frac{1}{2} V_{i1} g_m 47 \text{ k}\Omega = \frac{96.5 \mu\text{A}}{26 \text{ mV}} \\ &= \left(-\frac{1}{2}\right) (2 \text{ mV}) (0.0037) (47 \times 10^3) = 0.0037 \\ &= -173.9 \text{ mV} \approx -0.175 \text{ V} \end{aligned}$$



even mode (AC eg)

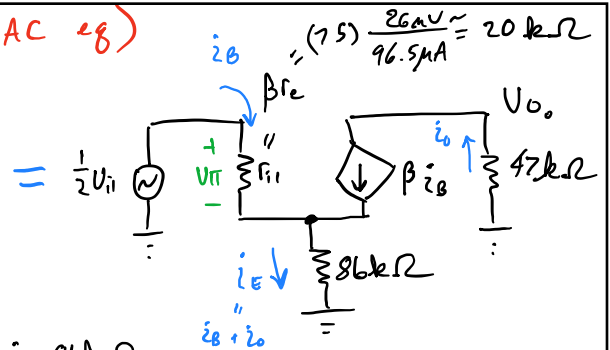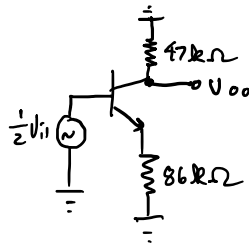

$$\begin{aligned} \frac{1}{2} V_{i1} &= i_B r_{i1} + i_E 86k\Omega \\ &= i_B r_{i1} + (i_B + i_o) 86k\Omega = i_B r_{i1} + i_B (1 + \beta) 86k\Omega \\ &= i_B (r_{i1} + 1 + \beta 86k\Omega) \approx i_B \beta 86k\Omega \end{aligned}$$

$$\rightarrow i_B = \frac{\frac{1}{2} V_{i1}}{(86k\Omega)\beta} \rightarrow i_o = \frac{\frac{1}{2} V_{i1}}{(86k\Omega)}$$

$$\rightarrow V_{o0} = -i_o 47k\Omega = -\frac{47k\Omega}{(86k\Omega)} \frac{1}{2} V_{i1} = \left(-\frac{1}{4}\right) (2mV)$$

$$= -0.5mV$$

Since $V_{o_e} \ll V_{o_0}$


$$\rightarrow V_o \approx V_{o_0}$$

$$\rightarrow V_o = -0.175V = -175\mu V$$


Large signal models

Forward-active: $V_{BE} > 0, V_{BC} < 0, V_{CE} > 0$


Three equivalent large signal models

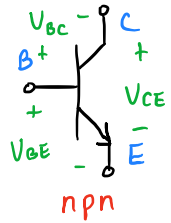

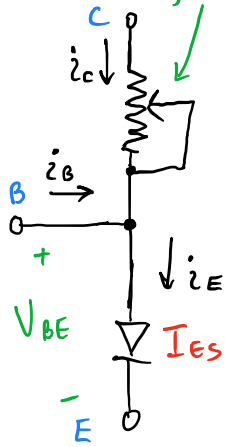
resistor automatically adjusts to keep $i_c = \beta i_b$



=


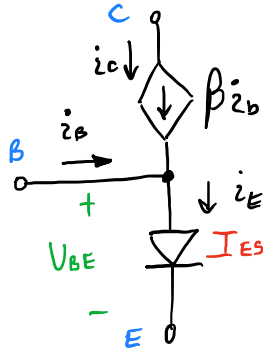


=

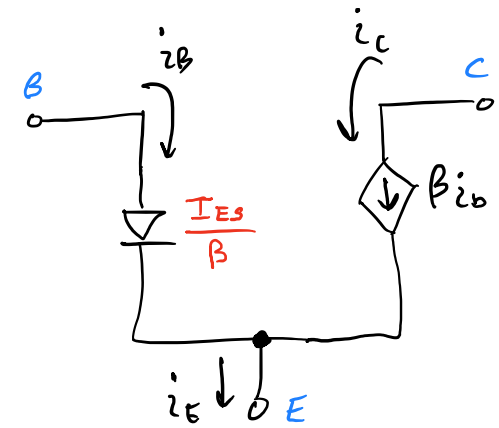

Large signal models

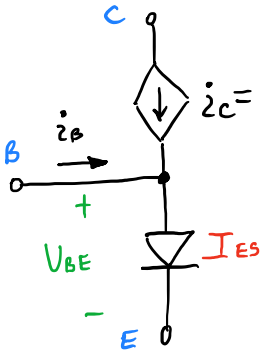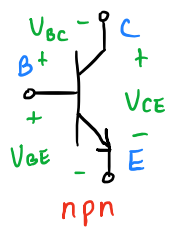Forward-active: $V_{BE} > 0, V_{BC} < 0, V_{CE} > 0$



$$i_c = \beta i_b = \alpha i_e = \alpha I_{ES} (e^{V_{BE}/V_T} - 1)$$

$$\alpha I_{ES} \equiv I_S$$

$V_T =$ thermal voltage $\frac{kT}{q} \approx 26 \text{ mV @ } 300\text{K}$

$I_{ES} =$ reverse saturation current of base-emitter diode (on order of 10^{-15} to 10^{-12} amperes).


This determines the voltage drop across diode (e.g. 0.3V, 0.65V, etc.)

So we can view α as a CCES or a VCCS!


Very simple Ebers-Moll model in forward-active mode (ignores early voltage)

Small signal: $V_{BE} = V_{BE} + v_{be}$

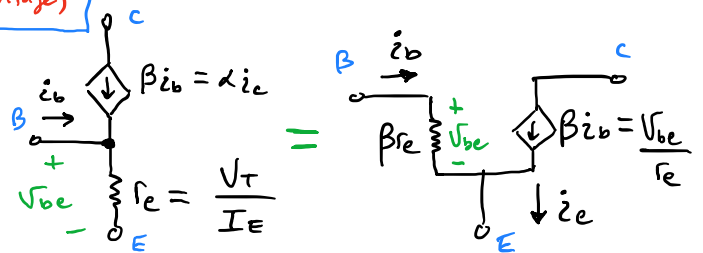instantaneous total \uparrow quiescent large signal \uparrow incremental small signal (wiggle)




$$r_e = \frac{V_T}{I_E}$$

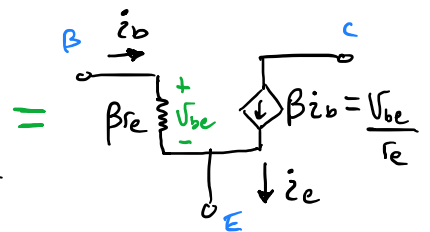


Useful basic BJT configurations for analog electronics design

Switching

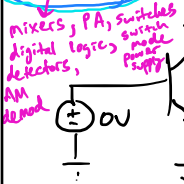


Cut-off
(BJT acts as open)

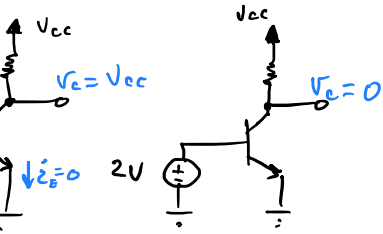


Saturation
(BJT acts as short)

Current source

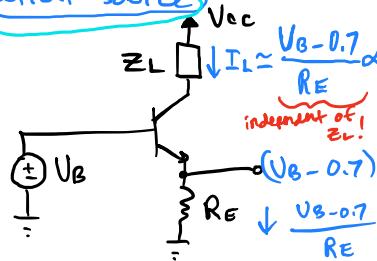


active mode

Amplifier 3

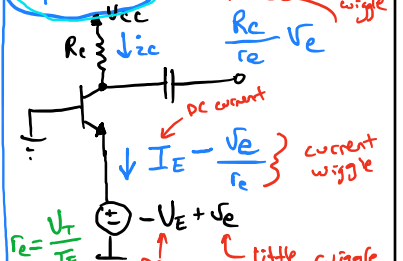

active mode


Voltage follower

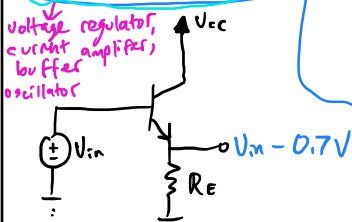

active mode


voltage amplifier oscillators

Amplifier 1

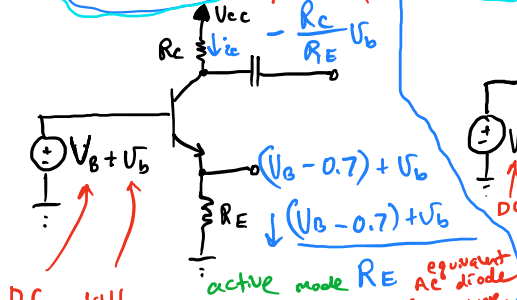

active mode RE
(Assume $RE \gg r_e$)

Amplifier 2

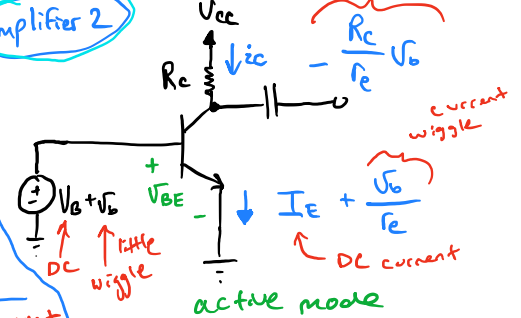

active mode

$$r_e = \frac{V_T}{I_E}$$